




# DC Bridges-II

---

KELVIN DOUBLE BRIDGE AND  
BRIDGES WITH STRAIN GAUGE  
AND TEMPERATURE SENSORS
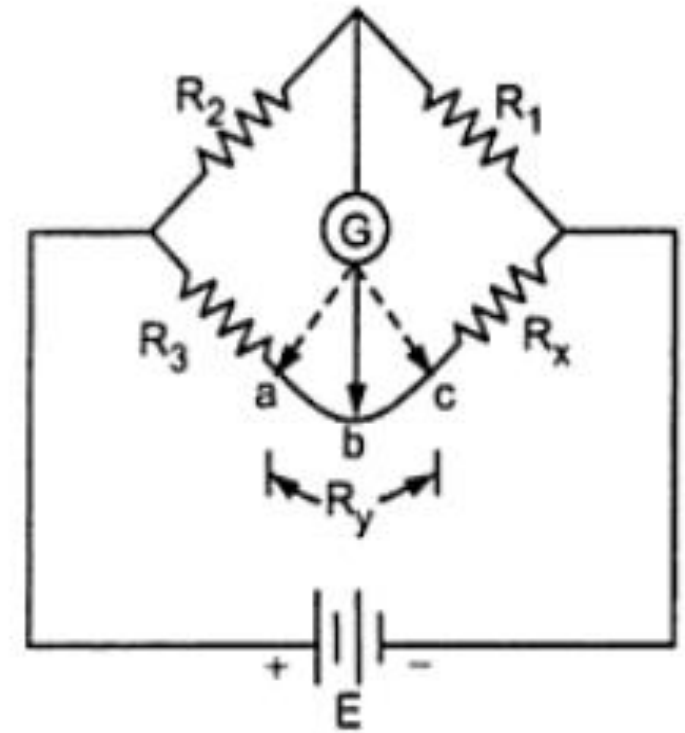
# DC BRIDGES – KELVIN DOUBLE BRIDGE

- ❑ It is used to solve the problem of connecting leads.
- ❑ It has two balanced ratio and can measure small resistance ( $0.0001\Omega$ ) with error 0.1%
- ❑ Kelvin bridge is a modified version of the Wheatstone bridge.
- ❑ The purpose of the modification is to eliminate the effects of contact, and lead resistance when measuring unknown low resistances.
- ❑ Resistors in the range of approximately 1microhm to 1ohm may be measured with a high degree of accuracy using a bridge called the *Kelvin bridge*



# Contd..

---

The resistance  $R_y$  is the resistance from  $R_3$  to  $R_x$ .

Where  $R_x$  is Unknown resistance

$$R_{cb}/R_{ab} = R_1/R_2 \quad (1)$$


Bridge in Balance form is

$$R_2 R_x = R_1 R_3 \quad (2)$$

$R_3$  is changed to  $R_3 + R_{ab}$  and  $R_x$  is changed to  $R_x + R_{cb}$

Modify equation (2) as
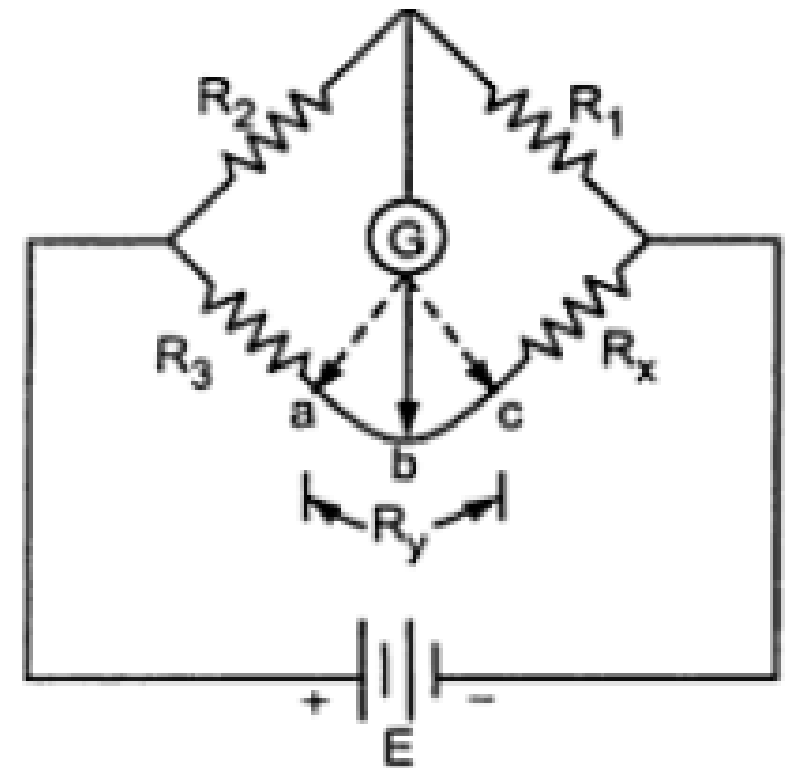
$$R_2 (R_x + R_{cb}) = R_1 (R_3 + R_{ab}) \quad (3)$$



# Contd..

---

$$(R_x + R_{cb}) = \frac{R_1}{R_2} (R_3 + R_{ab}) \quad (4)$$

$$\frac{R_{cb} + R_{ab}}{R_{ab}} = \frac{R_1 + R_2}{R_2}$$

but  $R_{cb} + R_{ab} = R_y$

Now 
$$\frac{R_{cb}}{R_{ab}} = \frac{R_1}{R_2}$$

$$\frac{R_y}{R_{ab}} = \frac{R_1 + R_2}{R_2}$$

$$\frac{R_{cb}}{R_{ab}} + 1 = \frac{R_1}{R_2} + 1$$

$$R_{ab} = \frac{R_2 R_y}{R_1 + R_2}$$

# Contd..

---

Similarly

$$R_{cb} = \frac{R_1 R_y}{R_1 + R_2}$$

$$(R_x + R_{cb}) = \frac{R_1}{R_2} (R_3 + R_{ab}) \quad (4)$$

Substitute value of  $R_{cb}$  and  $R_{ab}$  in eq (4)

$$R_x + \frac{R_1 R_y}{R_1 + R_2} = \frac{R_1}{R_2} \left( R_3 + \frac{R_2 R_y}{R_1 + R_2} \right)$$

$$R_x = \frac{R_1 R_3}{R_2}$$



# BRIDGE AMPLIFIER WITH STRAIN GAUGE

Gauge factor,  $G_F$

$$G_F = \frac{\Delta R/R_0}{\Delta L/L} = \frac{\Delta R/R_0}{\varepsilon}$$

$$R_3 = R_0 + \Delta R = R_0 (1 + \Delta R/R_0)$$

$$R_3 = R_0 (1 + G_F \varepsilon)$$

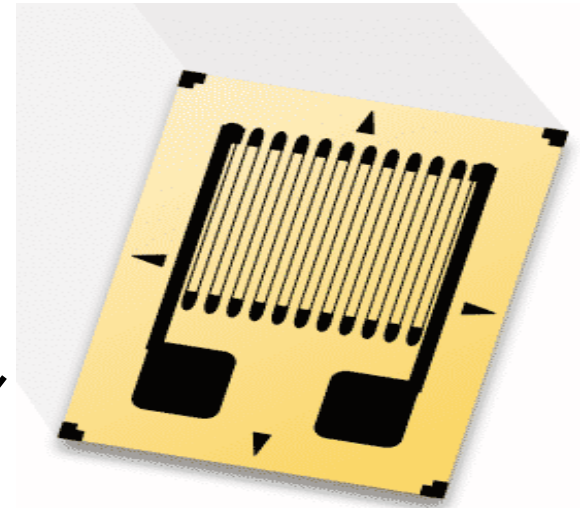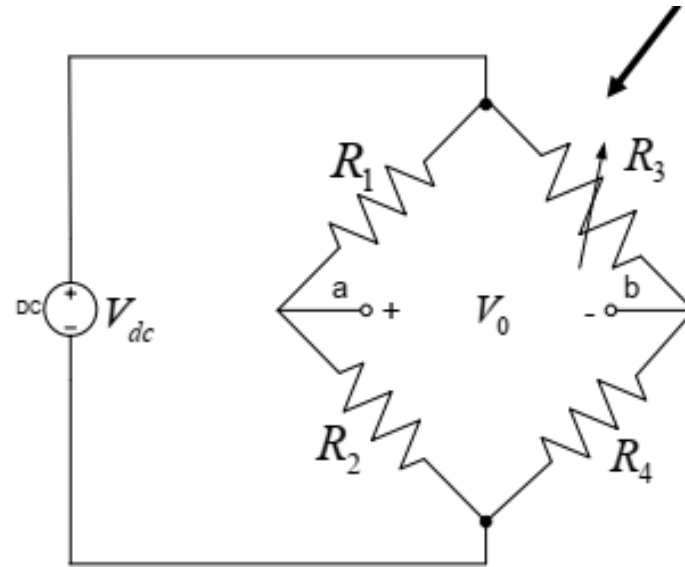

# Measurement of strain


---

$$V_0 = V_{dc} \left[ \frac{R_2}{R_1 + R_2} - \frac{R_4}{R_3 + R_4} \right]$$

$$\text{but } R_3 = R_0(1 + G_F \varepsilon)$$

$$V_0 = V_{dc} \left[ \frac{R_2}{R_1 + R_2} - \frac{R_4}{R_0(1 + G_F \varepsilon) + R_4} \right]$$

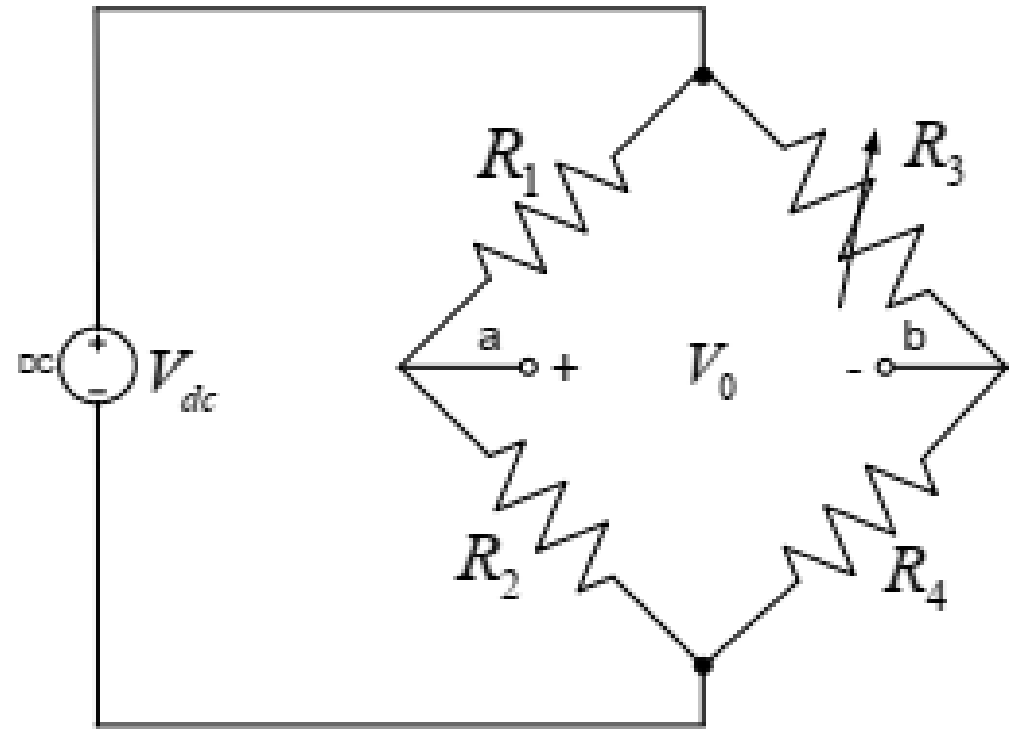
$$\varepsilon = \frac{R_4}{G_F R_0} \left[ \frac{1}{\left( \frac{R_2}{R_1 + R_2} - \frac{V_0}{V_{dc}} \right)} - 1 \right] - \frac{1}{G_F}$$


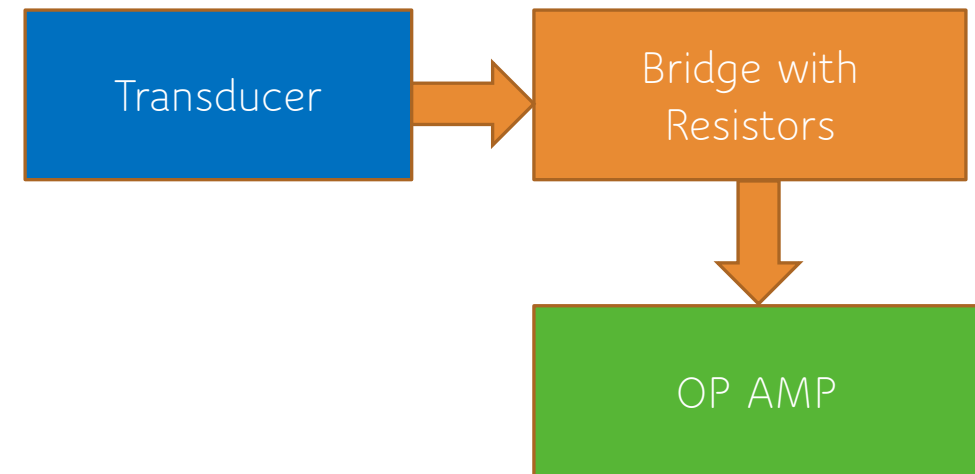
# BASIC BRIDGE AMPLIFIER

---

- ❑ A Basic bridge amplifier consists of an Op Amp, four resistors and a transducer.
- ❑ The transducer is a device that converts a non-electrical quantity to an electrical one or vice versa.
- ❑ A strain gauge is also a transducer whose resistance changes with the strain.
- ❑ **Photoconductive cells** are light-sensitive resistors in which resistance decreases with an increase in light intensity. When illuminated, it is another type of transducer.





# CIRCUIT ANALYSIS

The resistance of transducer is represented by

$$R_{transducer} = R_{ref} + \Delta R \quad (1)$$


$\Delta R$ =amount of change in R.

A thermistor has resistance of  $10,000\Omega$  at temperature of  $25^\circ\text{C}$ .

A temperature change of  $26^\circ\text{C}$  results in resistance of  $9573\Omega$ .


So using equation (1)

$$\Delta R = -427\Omega$$

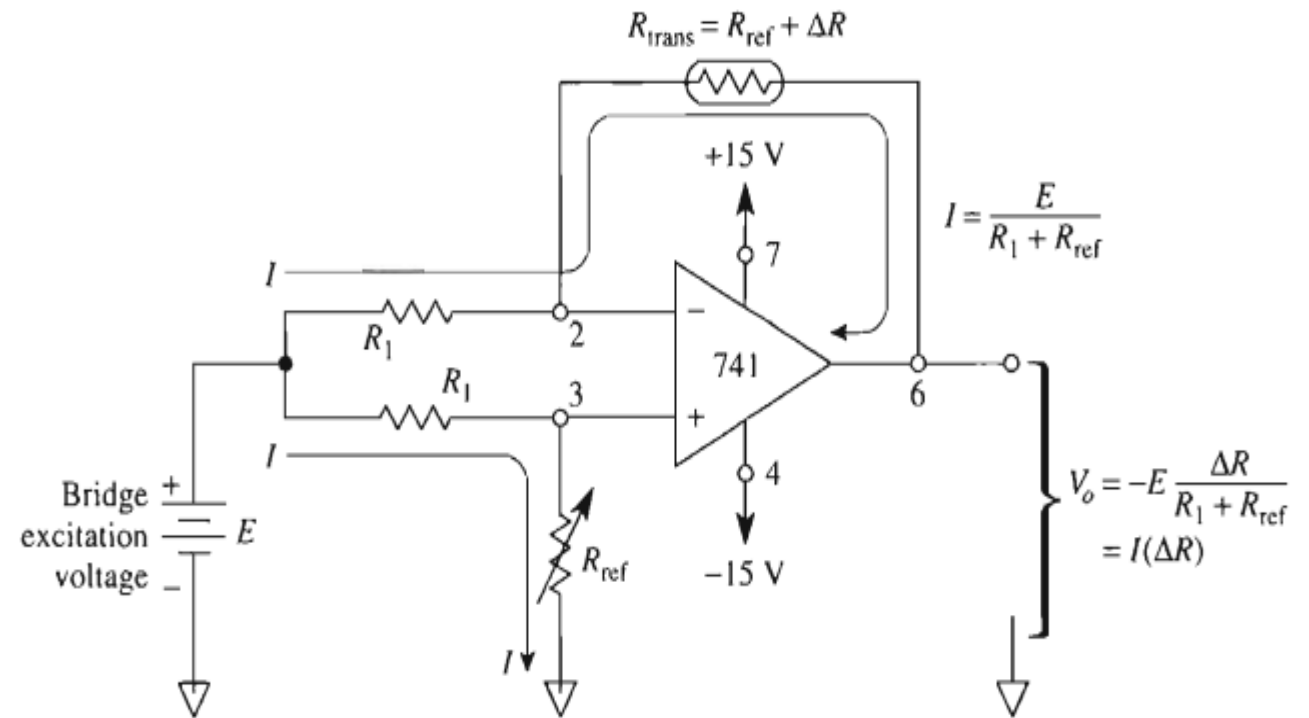
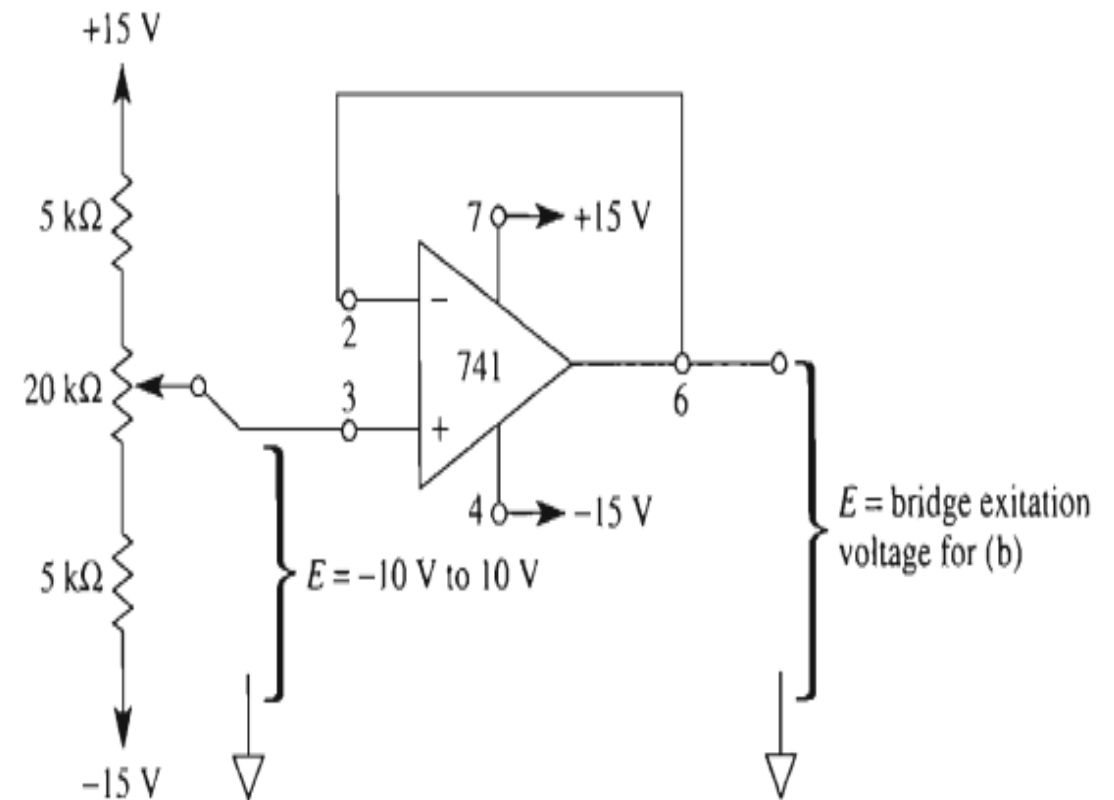
# Contd..

- ❑ This Bridge amplifier requires a stable dc or ac supply  $E$ .
- ❑ The power supply should have small internal resistance than  $R$ .
- ❑ So a specific circuit is used for generating of the stable power supply in which voltage divider circuit is used together with op amp.
- ❑ The OP amp act as voltage follower and  $E$  can be adjusted between  $+10$  and  $-10$  V.



# Temperature measurement with Thermistor

---

Step1 Select any thermistor such as 701033 or UUA41J1

Step2 Connect this to one arm of the bridge amplifier.

Step 3 Select the reference temperature. e.g. 20 degree C

Step 4 At reference temperature the voltage should be zero and calculate the resistance at this value.

Step 4 Predict the voltage temperature characteristics and calculate the I and V for each



# Sensitivity of Wheatstone Bridge

let for unbalance  $R$  is changed to  $R + \Delta R$

$$e = E_{AD} - E_{AB} = I_2 (R + \Delta R) - I_1 P$$


$$= \frac{E}{R + \Delta R + S} (R + \Delta R) - \frac{E}{P + Q} P$$

$$= E \left[ \frac{R + \Delta R}{R + \Delta R + S} - \frac{P}{P + Q} \right]$$

As  $\frac{P}{Q} = \frac{R}{S}$  or  $\frac{P}{P + Q} = \frac{R}{R + S}$

$$= E \left[ \frac{R + \Delta R}{R + \Delta R + S} - \frac{R}{R + S} \right] = \frac{ER}{R + S} \left[ \frac{1 + \frac{\Delta R}{R}}{1 + \frac{\Delta R}{R + S}} - 1 \right]$$
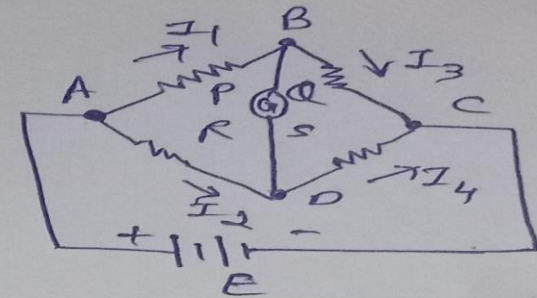
$$= \frac{ER}{R + S} \left[ \left( 1 + \frac{\Delta R}{R} \right) \left( 1 - \frac{\Delta R}{R + S} + \frac{(\Delta R)^2}{(R + S)^2} - \dots \right) - 1 \right]$$



Contd..

$$= \frac{ES\Delta R}{(R+S)^2}$$

Let  $S_V$  be voltage sensitivity of galvanometer

Galvanometer Deflection  $Q = S_V e = S_V \frac{ES\Delta R}{(R+S)^2}$

Let  $S_B$  is bridge sensitivity  $\rightarrow$  It is deflection of galvanometer per unit fractional change in unknown resistance

$$S_B = \frac{Q}{\frac{\Delta R}{R}} = \frac{S_V E S R}{(R+S)^2}$$



Contd..

$$S_B = \frac{S_V E}{\frac{(R+S)^2}{RS}} = \frac{S_V E}{\left(\frac{R}{S} + 2 + \frac{S}{R}\right)} = \frac{S_V E}{\frac{P}{Q} + 2 + \frac{Q}{P}}$$

For bridge with unity arm resistance

$$R = S = P = Q$$


$$S_B = \frac{S_V E}{1+2+1} = \frac{S_V E}{4}$$

$$R_{th} = \frac{RS}{R+S} + \frac{PQ}{P+Q}$$

$$\text{If } P=Q=R=S$$

$$R_{th} = \frac{R \cdot R}{R+R} + \frac{R \cdot R}{R+R} = \frac{R^2}{2R} + \frac{R^2}{2R} = \frac{2R(R)}{2R} = R$$
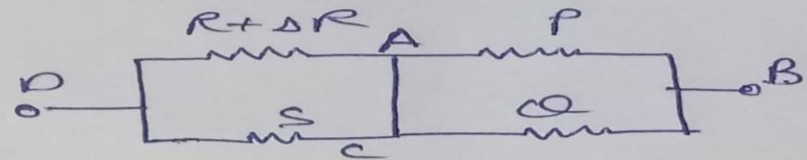
$$E_{th} = E \left[ \frac{R+\Delta R}{R+\Delta R+S} - \frac{P}{P+Q} \right] = E \left[ \frac{R+\Delta R}{2R+\Delta R} - \frac{1}{2} \right]$$



Contd..

$$I_g = \frac{E_{th}}{R_{th} + R_g}$$

$$= \frac{E \frac{\Delta R}{4R}}{R_{th} + R_g}$$

deflection  $\leftarrow$


$$\odot = \frac{S_v E S R}{(R + S)^2}$$

$$S_v = \frac{S_i}{R_{th} + R_g} \rightarrow \text{Current Sensitivity of galvanometer}$$

$$\odot = \frac{S_i E S R}{(R + S)^2 (R_{th} + R_g)}$$

For  $R = 0 = R = S$
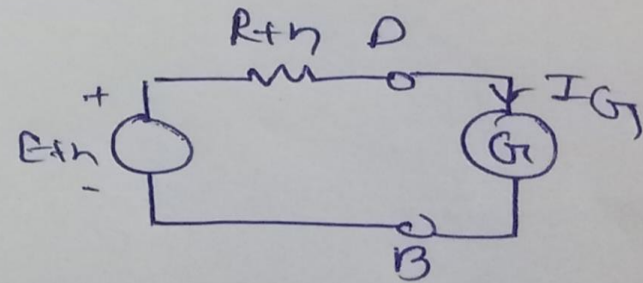
$$\odot = \frac{S_i E \Delta R}{4R(R_{th} + R_g)} \quad S_B = \frac{S_i E}{4(R_{th} + R_g)}$$



# References

---

[Kalsi H S](#), [Electronic instrumentation](#), Tata McGraw-Hill Education, 2004

[E.O. Doebelin](#), [Measurement System](#), Tata McGraw-Hill Education, 2013.

A.K Sawhney,, [Electrical and Electronics Measurements](#).