



# Active Filters

---

**Bandpass & Low Pass Butterworth Filters**
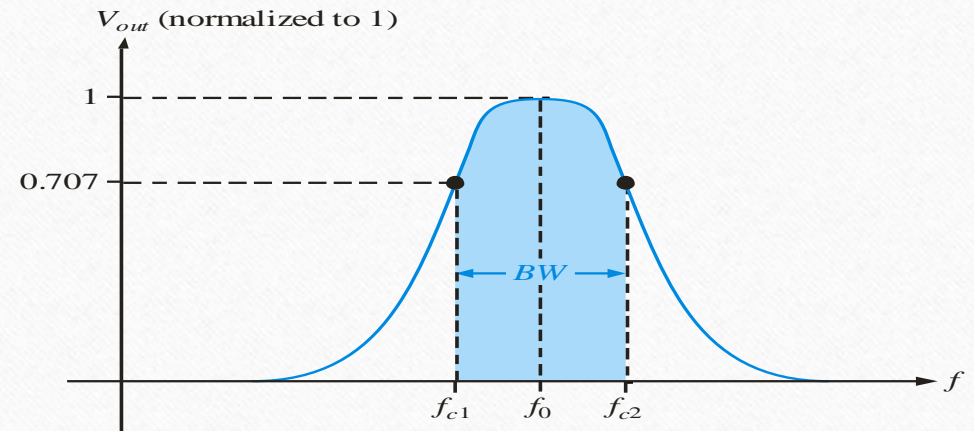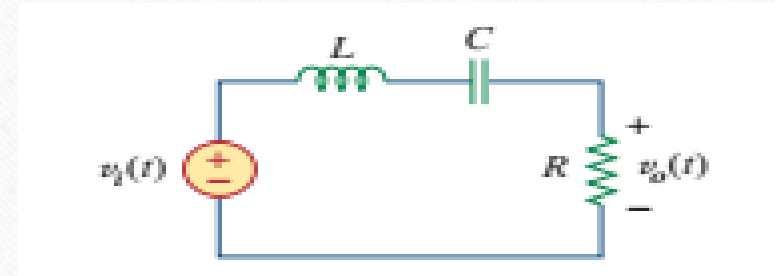
# The Band-Pass Filter

- A **band-pass filter** passes all frequencies between two critical frequencies.
- The **bandwidth** is defined as the difference between the two critical frequencies  $f_{c1}$  and  $f_{c2}$ .
- $\text{Bandwidth} = f_{c2} - f_{c1}$
- $\text{Centre freq} = (f_{c2} \times f_{c1})^{0.5}$
- The simplest band-pass filter is an *RLC* circuit.







## Contd..

- A band-pass filter that will have a gain  $K$  over the required range of frequencies.
- By cascading a unity-gain low-pass filter, a unity-gain high-pass filter, and an inverter with gain  $-R_f/R_i$ .
- Band pass filters are known generally as second-order filters, (two-pole) because they have “two” reactive component, the capacitors, within their circuit design.

$$f_c = \frac{1}{2\pi RC} \text{ Hz}$$

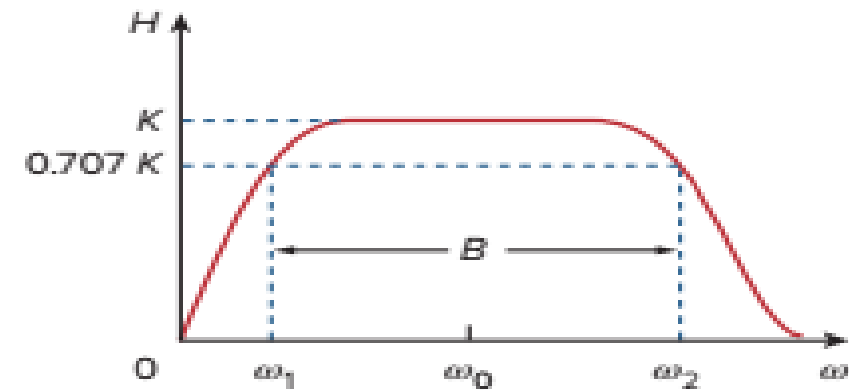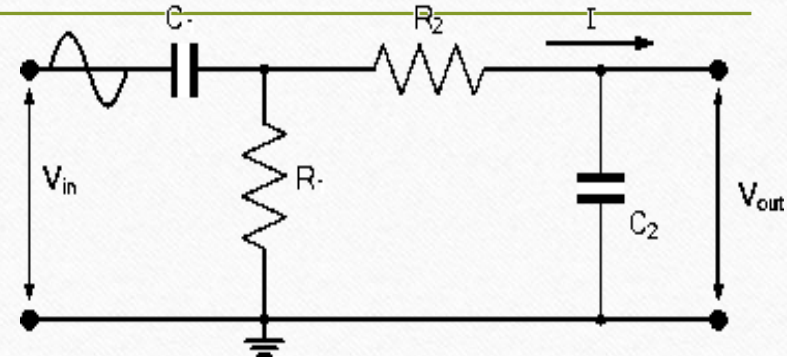


# Contd..

$$\mathbf{H}(\omega) = \frac{\mathbf{V}_o}{\mathbf{V}_i} = \left( -\frac{1}{1 + j\omega C_1 R} \right) \left( -\frac{j\omega C_2 R}{1 + j\omega C_2 R} \right) \left( -\frac{R_f}{R_i} \right)$$

$$= -\frac{R_f}{R_i} \frac{1}{1 + j\omega C_1 R} \frac{j\omega C_2 R}{1 + j\omega C_2 R}$$

The upper and lower cut off frequency is given by
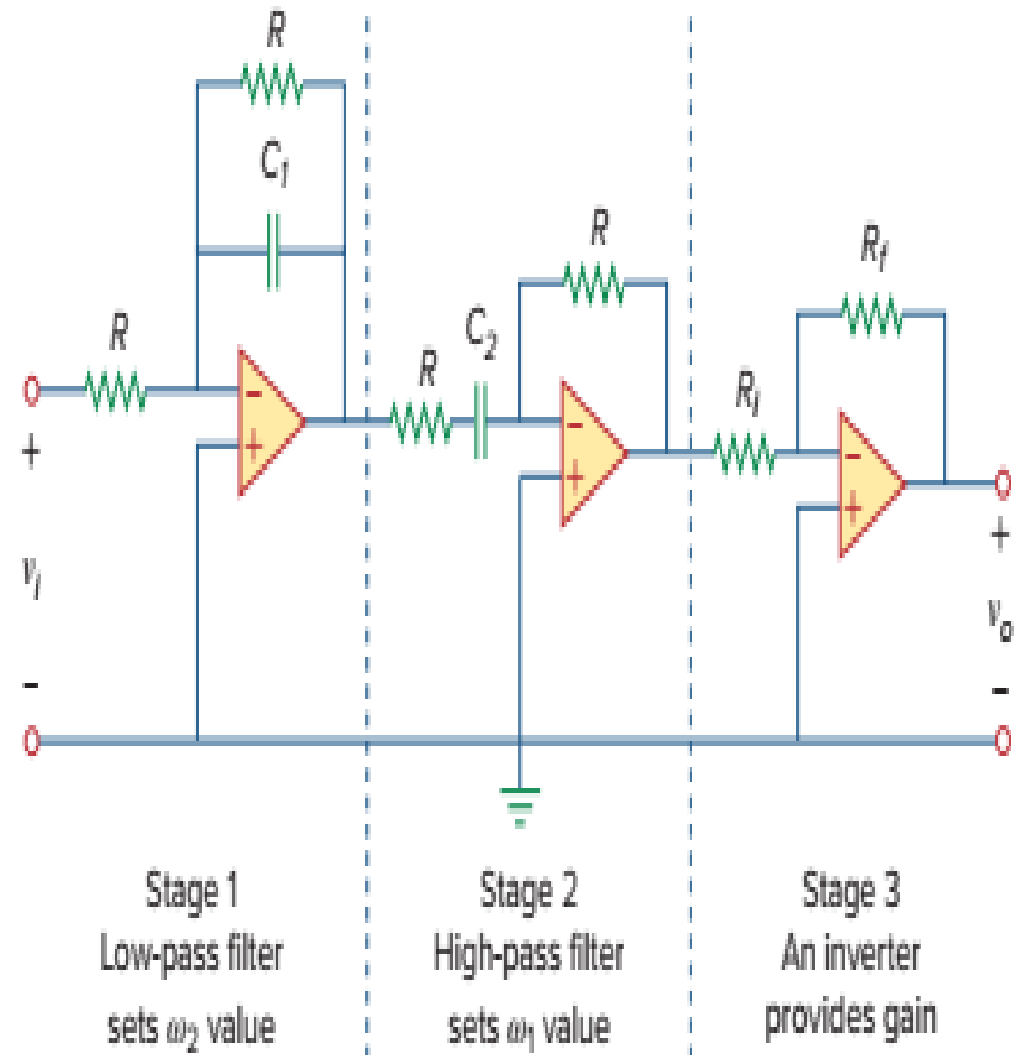
$$\omega_2 = \frac{1}{RC_1} \quad \omega_1 = \frac{1}{RC_2}$$



## Contd..

- The bandwidth, quality factor can be calculated as

$$\omega_0 = \sqrt{\omega_1 \omega_2}$$

$$B = \omega_2 - \omega_1$$

$$Q = \frac{\omega_0}{B}$$

- Pass band gain be calculated by

$$H(\omega) = -\frac{R_f}{R_i} \frac{j\omega/\omega_1}{(1 + j\omega/\omega_1)(1 + j\omega/\omega_2)} = -\frac{R_f}{R_i} \frac{j\omega\omega_2}{(\omega_1 + j\omega)(\omega_2 + j\omega)}$$

$$|H(\omega_0)| = \left| \frac{R_f}{R_i} \frac{j\omega_0\omega_2}{(\omega_1 + j\omega_0)(\omega_2 + j\omega_0)} \right| = \frac{R_f}{R_i} \frac{\omega_2}{\omega_1 + \omega_2}$$

$$K = \frac{R_f}{R_i} \frac{\omega_2}{\omega_1 + \omega_2}$$



# Butterworth Filter

---

- Flat response in the pass band & stop band and called flat-flat filter .
- The Butterworth filter has frequency response as flat as mathematically possible, hence it is also called as a maximally flat magnitude filter (from 0Hz to cut-off frequency at -3dB without any ripples).
- The quality factor for this type is just  $Q=0.707$  and thus, all high frequencies above the cut-off point band rolls down to zero at 20dB per decade or 6dB per octave in the stop band.

# Transfer Function

**The transfer function provides a basis for determining important system response characteristics**

**The transfer function is a rational function in the complex variable  $s = \sigma + j\omega$ , that is**

$$H(s) = \frac{b_m s^m + b_{m-1} s^{m-1} + \dots + b_1 s + b_0}{a_n s^n + a_{n-1} s^{n-1} + \dots + a_1 s + a_0}$$

$$H(s) = \frac{N(s)}{D(s)} = K \frac{(s - z_1)(s - z_2) \dots (s - z_{m-1})(s - z_m)}{(s - p_1)(s - p_2) \dots (s - p_{n-1})(s - p_n)}$$


**$z_i$ 's are the roots of the equation  $N(s) = 0$ , and are defined to be the system zeros, and the  $p_i$ 's are the roots of the equation  $D(s) = 0$ , and are defined to be the system poles.**

**$N(s) = 0$ ; Zeros.  $D(s) = 0$ ; Poles.**



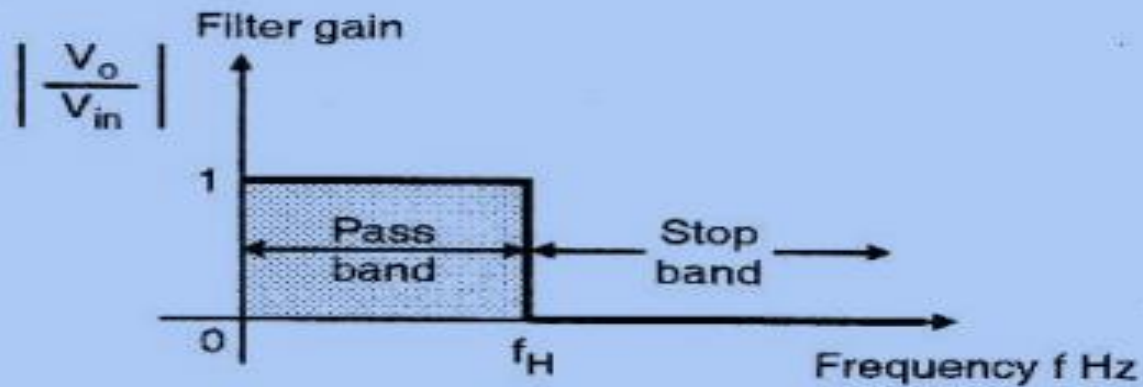
# FREQUENCY RESPONSE OF FILTERS

- Gain of a filter is given as,  $G=V_o/V_{in}$ .
- Ideal & practical frequency responses of different types of filters are shown below.



(a) Ideal low-pass filter

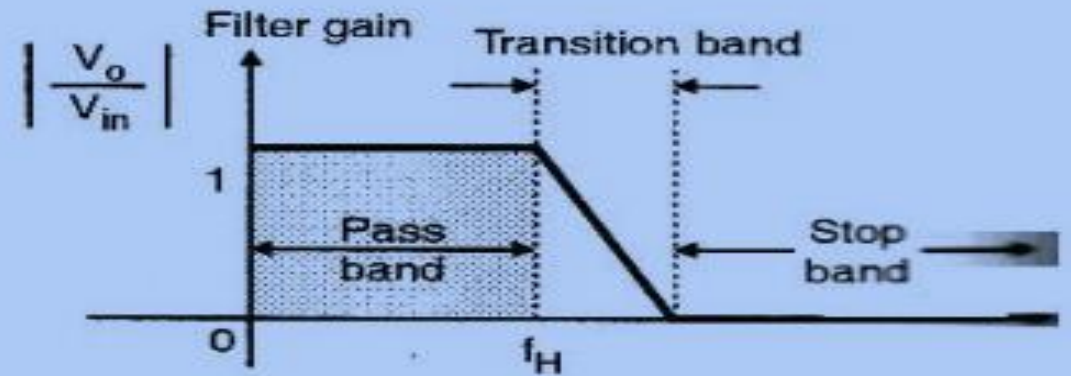


(b) Practical low-pass filter




# First Order Low-Pass Butterworth Filter

- In 1st. order LPF which is also known as *one pole LPF*.
- RC values decide the cut-off frequency of the filter.
- Resistors  $R_1$  &  $R_F$  will decide its gain in pass band.
- As the OP-AMP is used in the non-inverting configuration, the closed loop gain of the filter is given by

$$A_{VF} = 1 + \frac{R_F}{R_1}$$

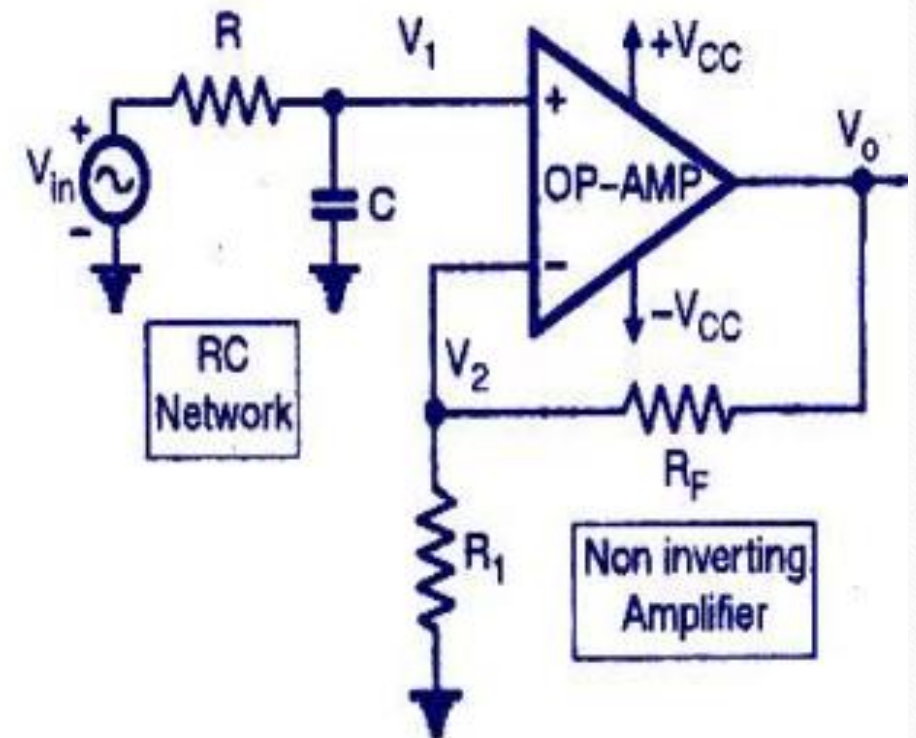

# Mathematical Analysis

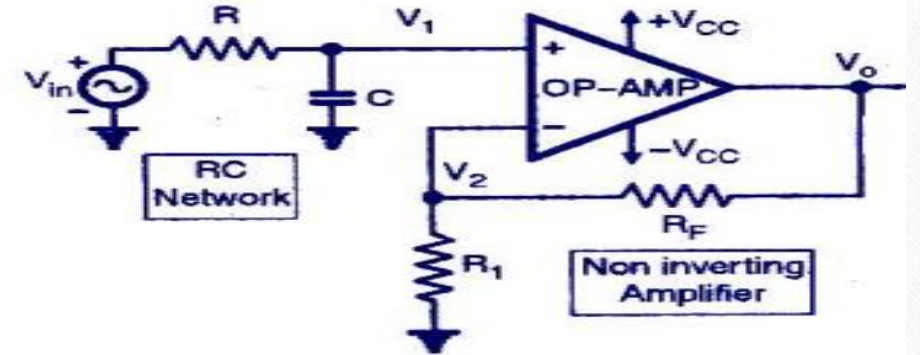

- The Voltage at non inverting input is

$$v_1 = \frac{-jX_c}{R - jX_c} V_{in} = \frac{V_{in}}{1 + j2\pi fCR}$$

$$V_{out} = \left(1 + \frac{R_F}{R_1}\right) v_1 = \left(1 + \frac{R_F}{R_1}\right) \frac{V_{in}}{1 + j2\pi fCR}$$

$$\frac{V_{out}}{V_{in}} = \frac{A_F}{1 + j2\pi fCR}$$

$$\text{where } A_F = \left(1 + \frac{R_F}{R_1}\right)$$

- is a Pass band gain of filter

- Substitute

$$f_H = \frac{1}{2\pi RC} \quad \frac{V_{out}}{V_{in}} = \frac{A_F}{1 + j \frac{f}{f_H}}$$

- The gain magnitude can be calculated using

$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{A_F}{\sqrt{1 + \left(\frac{f}{f_H}\right)^2}}$$

- The phase angle is

$$\phi = -\tan^{-1} \left( \frac{f}{f_H} \right)$$



# DESIGN PROCEDURE

---

- *Step1: Choose the cut-off frequency  $f_H$*   
*Step2: Select a value of 'C'  $\leq 1\mu F$  (Approximately between .001 &  $0.1\mu F$ )*  
*Step3: Calculate the value of R using*

$$R = \frac{1}{2\pi f_H C}$$

- *Step4: Select resistors  $R_1$  &  $R_2$  depending on the desired pass band gain.*

$$A_{VF} = 1 + \frac{R_F}{R_1}$$



*Q1. For a first order Butterworth LPF, calculate the cut –off frequency if  $R=10Kohm$  &  $C=0.001\mu F$ . Also calculate the pass band voltage gain if  $R_1=10Kohm$  and  $R_F=100Kohm$*


---

$$f_H = \frac{1}{2\pi RC} = \frac{1}{2\pi \times 10 \times 10^3 \times 0.001 \times 10^{-6}} = 15.915 KHz$$

$$A_{VF} = 1 + \frac{R_F}{R_1} \quad 1 + 100K/10K = 11$$
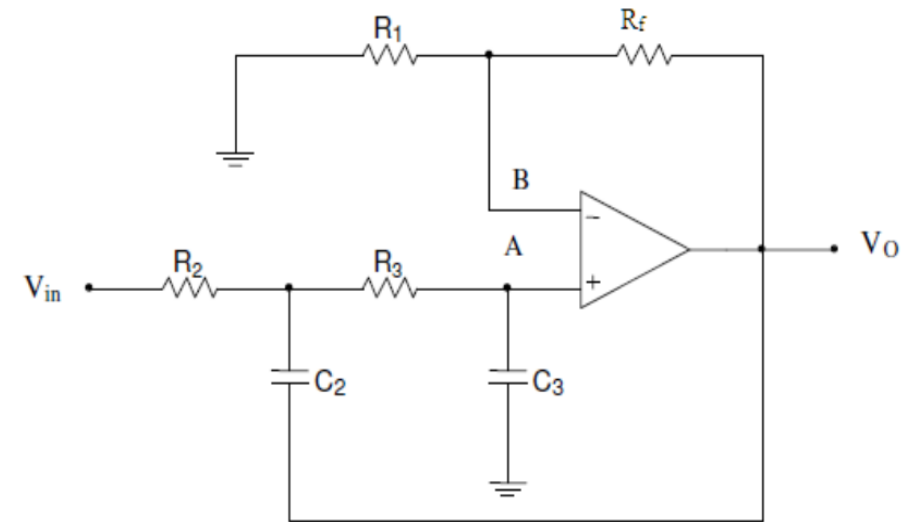
# 2<sup>nd</sup> Order Low-Pass Butterworth Filter

- As the order of the filter increase the gain roll off also increases.
- Hence for a second order filter the roll off will be - 40dB / decade.
- Hence the gain reduces sharply compared to first ordered filters.
- A first order filter can be converted to a second order by using an additional RC network as shown in the figure.
- The closed loop gain  $A_f$  must be 1.586 for Butterworth response.



$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{A_F}{\sqrt{1 + \left( \frac{f}{f_H} \right)^4}} \quad f_H = \frac{1}{2\pi \sqrt{R_2 R_3 C_2 C_3}}$$

# References

---

- *Coughlin, R.F., Operational Amplifiers and Linear Integrated Circuits, Pearson Education (2006).*
- *Gayakwad, R.A., Op-Amp and Linear Integrated Circuits, Pearson Education (2002).*
- *Franco, S., Design with Operational Amplifier and Analog Integrated circuit, McGraw Hill (2016).*
- *Terrell, D., Op Amps Design Application and Troubleshooting, Newness (1996).*