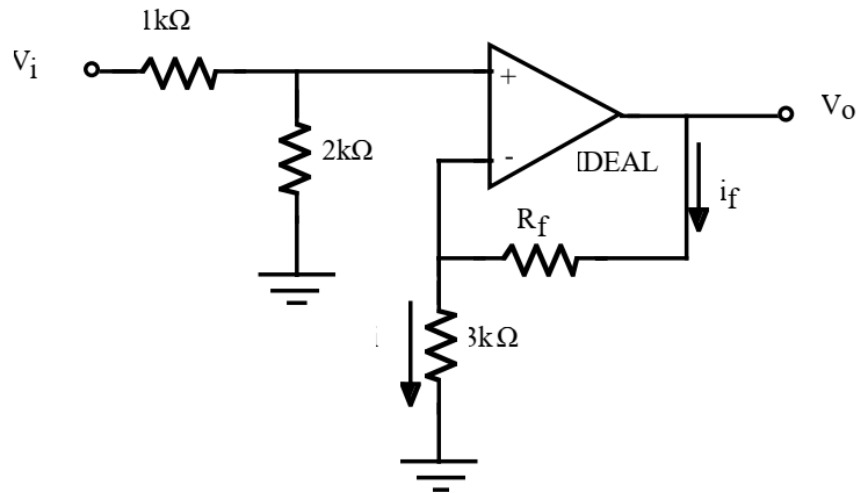


## Tutorial Sheet


---

Q1. For the ideal op amp shown, what should be the value of resistor  $R_f$  to obtain a gain of 5?



**Answer : 19.5 k $\Omega$**

Sol 1.

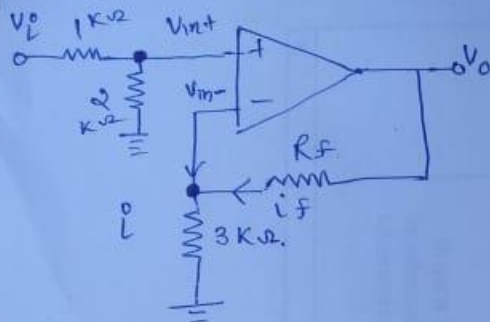

Find  $V_{in+}$

Apply voltage divider rule

$$V_{in+} = \frac{2}{2+1} \times V_i = \frac{2}{3} V_i$$

Now using virtual concept

$$V_{in+} = V_{in-} = \frac{2}{3} V_i$$

Now Consider a feedback loop

$$i = i_f$$

$$\frac{V_{in-} - 0}{3} = \frac{V_o - V_{in-}}{R_f}$$

$$\frac{\frac{2}{3} V_i}{3} = \frac{V_o - \frac{2}{3} V_i}{R_f}$$

$$\text{But } V_o = 5V_i$$

$$\frac{2}{9} V_i = \frac{5V_i - \frac{2}{3} V_i}{R_f}$$


$$\frac{2}{9} V_i = \frac{15V_i - 2V_i}{3R_f}$$

$$\frac{2}{9} V_i = \frac{13V_i}{3R_f}$$

$$R_f = \frac{13 \times 9}{2 \times 8}$$

$$= \frac{39}{2} = 19.5 \text{ k}\Omega$$

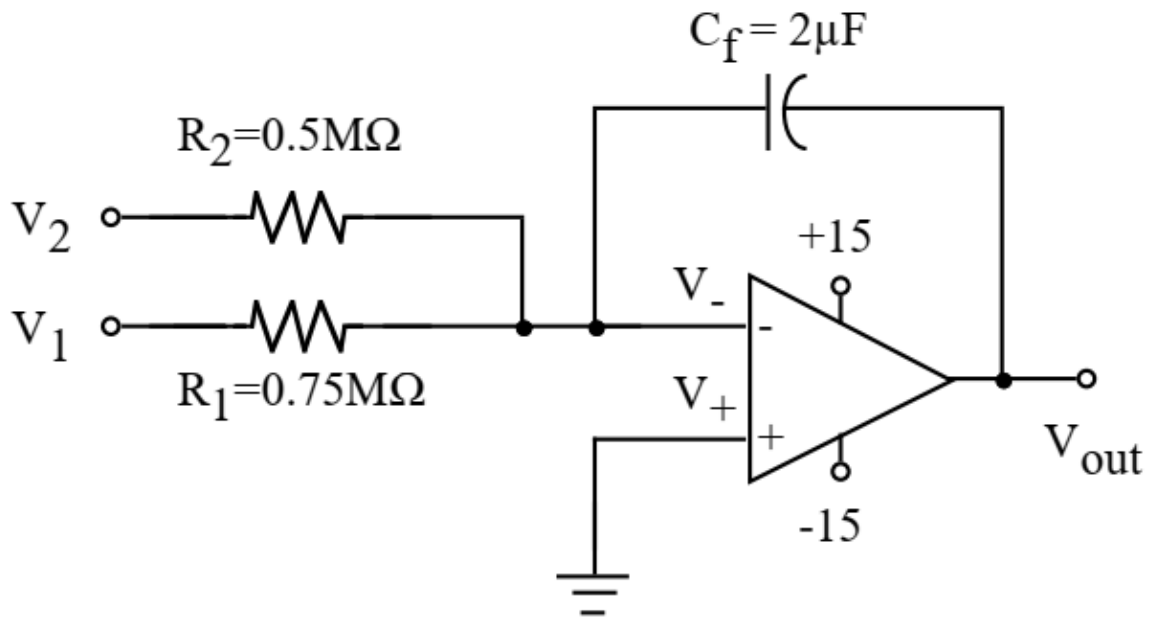**Q2.** For the circuit shown below,  $V_1 = 10\sin(200t)$  and  $V_2 = 15\sin(200t)$ . What is  $V_{out}$ ? The op amp is ideal with infinite gain.



**Answer :**  $(\frac{3}{40} + \frac{1}{30}) \cos(200t)$

Sol 2

Apply KCL at inverting point.

$$\frac{V_2 - 0}{R_2} + \frac{V_1 - 0}{R_1} = 0 - \frac{V_{out}}{j\omega C}$$

$$\frac{V_2}{R_2} + \frac{V_1}{R_1} + j\omega C V_{out} = 0$$

$$V_{out} = -\frac{V_2}{R_2 j\omega C} - \frac{V_1}{j\omega C R_1}$$

$$\sin(200t) = \cos(200t - 90^\circ) \rightarrow 1 \angle -90^\circ = -j$$

$$V_{out} = \frac{-j15}{j(200)(2 \times 10^6)(0.5 \times 10^{-6})} - \frac{(-j10)}{j(200)(2 \times 10^6)(0.75 \times 10^{-6})}$$

$$= \frac{3}{40} + \frac{1}{30}$$

$$V_{out} = \left( \frac{3}{40} + \frac{1}{30} \right) \cos(200t)$$

Q3. Find the cut off frequency for low pass active filter for given specifications:  
Resistor(R) = 1kohm and capacitor (C) = 1μF.

**Answer : 159Hz**


Solution

$$f_c = \frac{1}{2\pi RC} \text{ Hz}$$

Q4. The maximum gain of the low pass filter is 100dB. Find the gain at the critical frequency.  
**Answer : 97 dB**

Solution 3 db gain at  $f_c$

So  $100-3=97$  db

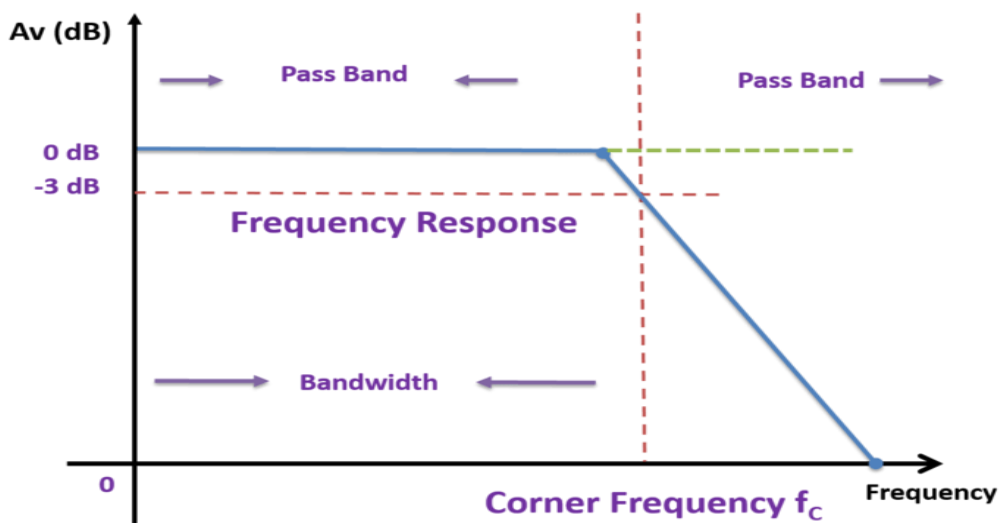

Q5. Design a non inverting amplifier that has a voltage gain of 10 using an ideal op amp. The input signal lie in the range from -1 V to 1 V. Use 5 % tolerance discrete resistors for the feedback network.

**Answer :** The values of resistances are restricted in the range 100Ω.. 1MΩ.

$$A_{CL} = 1 + (R_f / R_2) = V_{out}/V_{in} = 10 = 1 + R_f/2$$

