

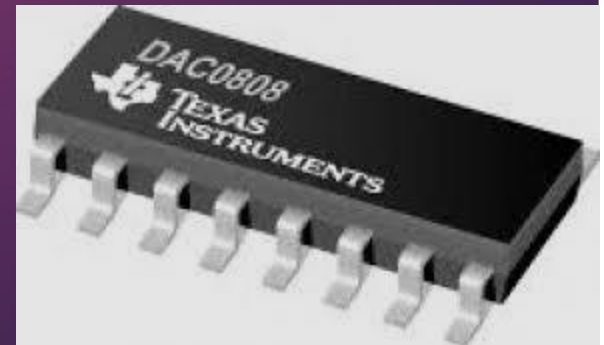


# Digital to Analog Converters (DAC)

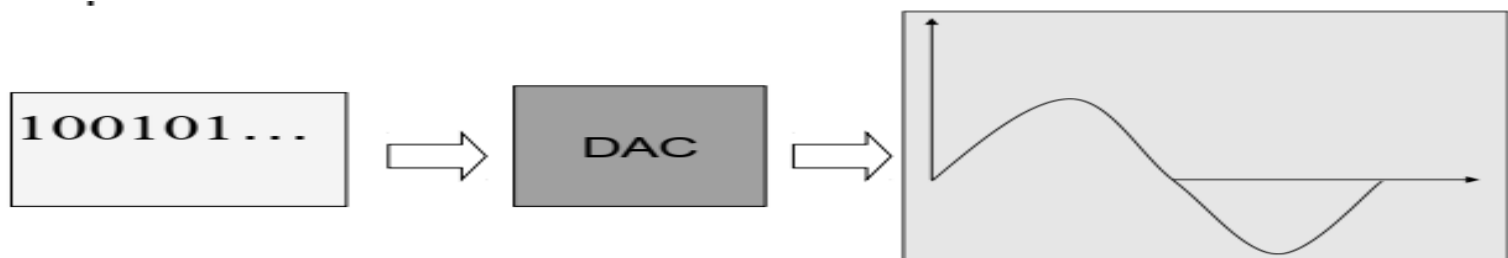
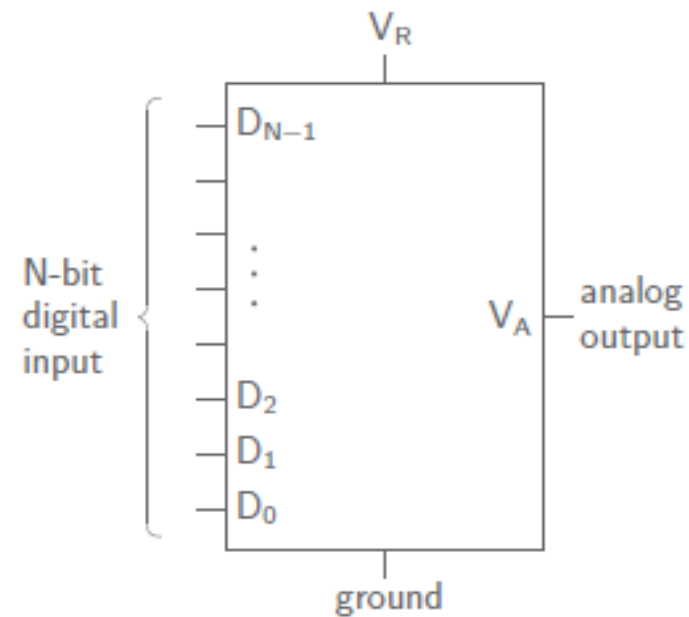
# Introduction

- ▶ Digital to analog converter translates a digital signal into an analog signal to represent a physical quantity.
- ▶ A n-bit DAC has n input lines to have  $2^n$  input combination and an analog output line.
- ▶ A digital-to-analog converter (DAC) takes a digital code as its input and produces an analog voltage or current as its output.
- ▶ This analog output is proportional to the digital input.




Contd..

0 1 1 1 0 0 1 1 0 1 1 1 1 1 1 1 0 0 1 1 0 0 1



D/A  
conversion

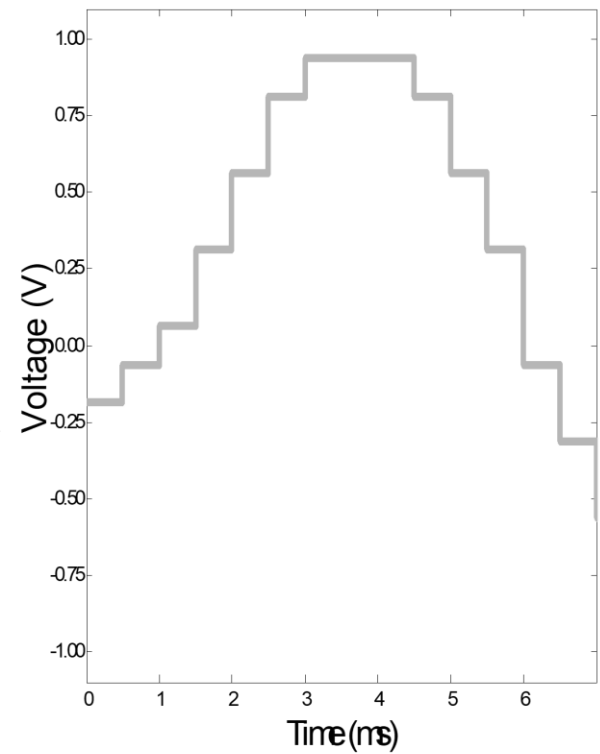


# Digital to Analog Basic Operation

- ▶ The conversion of the digital signal into an analog one is performed by an electronic circuit.
- ▶ The input is received in a binary form and the output yielded is in the form of an electrical current or voltage that manifests as an analog presentation.
- ▶ The digital data that is being used as an input can be produced by an FPGA, or any other microprocessor or microcontroller.
- ▶ One of the most commonly seen and used applications of a digital to analog converter is that is music players.
- ▶ These devices take in streams and waves of digital data and then convert them into analog audio signals.
- ▶ A DAC is defined by certain parameters and its capability pertaining to these specific parameters determines the application they are best suited for. These parameters include resolution and frequency.
- ▶ Where the audio output would require a high resolution but low frequency type of converter, a video or visual output will require high frequency and low resolution.
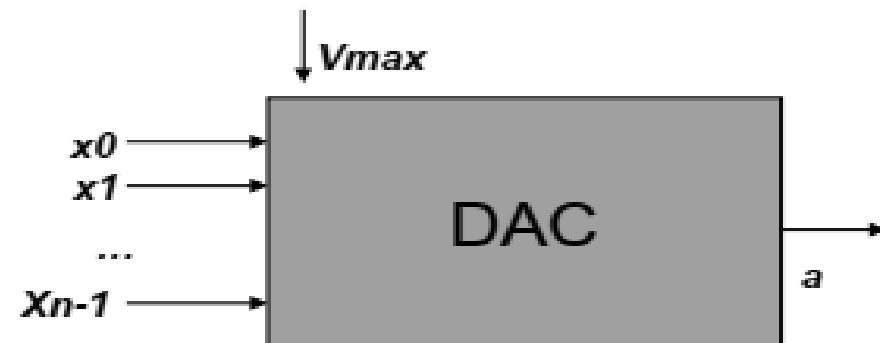
# Principle

- ▶ Digital transforming the computer's binary output into an analog representation of the binary data .  
and 1's (1's typically = 5.0 volts) in 0's
- ▶  $n$  digital inputs for digital encoding
- ▶ analog input for  $V_{max}$
- ▶ Analog output




# Contd..

- ▶ Digital input  $D_{in}$  is defined as  $n$  bit digital word such as  

$$D_{in} = D_0 \times 2^{-n} + D_1 \times 2^{-(n-1)} + D_2 \times 2^{-(n-2)} + \dots + D_{n-1} \times 2^{-1}$$
- ▶ Where  $D_i$  is binary digit and equals 1 or 0.
- ▶  $D_0$  is defined as least significant bit and  $D_{N-1}$  is most significant bit.
- ▶ The analog output signal  $V_{out}$  is related to digital input signal.
- ▶  $D_{in}$  through analog voltage reference  $V_{ref}$ .
- ▶ The relation between these three signals is

$$V_{out} = V_{ref} \times D_{in}$$

$$V_{LSB} = V_{ref} / 2^n$$

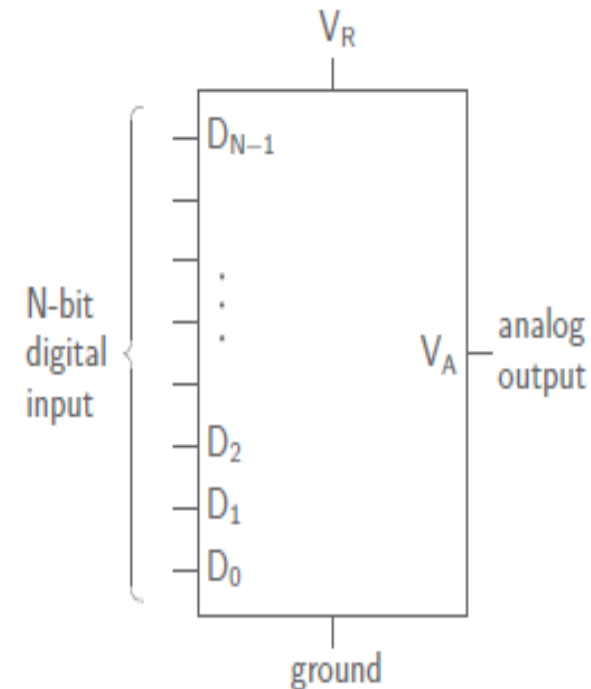

# DAC CHARACTERISTICS

- ▶ **Resolution** -Resolution is the amount of variance in output voltage for every change of the LSB in the digital input.
- ▶ Just as with ADCs, there are several common ways of specifying a DAC's resolution:
- ▶ Number of bits,  $n$  , Number of output codes =  $2^n$ , and Number of steps in the output =  $2^n - 1$
- ▶ **Percentage resolution** =  $1 / (2^n - 1)$ , expressed as a percentage
- ▶ Step size, =  $V_{ref} / (2^n - 1)$
- ▶ Percentage Resolution=step size/Full scale output
- ▶ Example: For 5 bit binary network, if full scale maximum output is 10 Volt, then resolution would be  $=1/32 * 10 = 0.3125$  Volt


## Contd..

- ▶ **Accuracy**- is represented in form of full scale error and linearity error.
- ▶ **Full scale error**- is deviation of DAC output from ideal or expected value.
- ▶ **Linearity error**-is maximum deviation in step size of 1 V.
- ▶ **Offset error**-often called 'zero-scale' error, indicates how well the actual transfer function matches the ideal transfer function at a single point.
- ▶ **Gain error**-is difference in slope between ideal DAC output gain and actual gain.



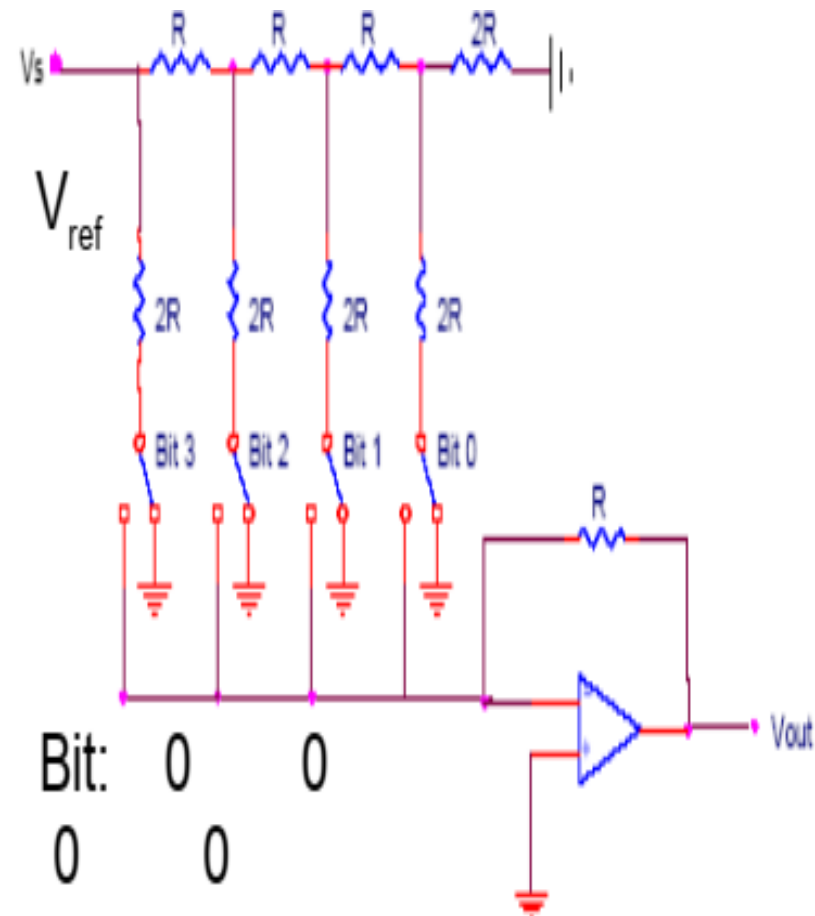
# R-2R ladder network

- ▶ An enhancement of the binary-weighted resistor DAC is the R-2R ladder network.
- ▶ This type of DAC utilizes Thevenin's theorem in arriving at the desired output voltages.
- ▶ The R-2R network consists of resistors with only two values - R and  $2xR$ .
- ▶ If each input is supplied either 0 volts or reference voltage, the output voltage will be an analog equivalent of the binary value of the three bits.



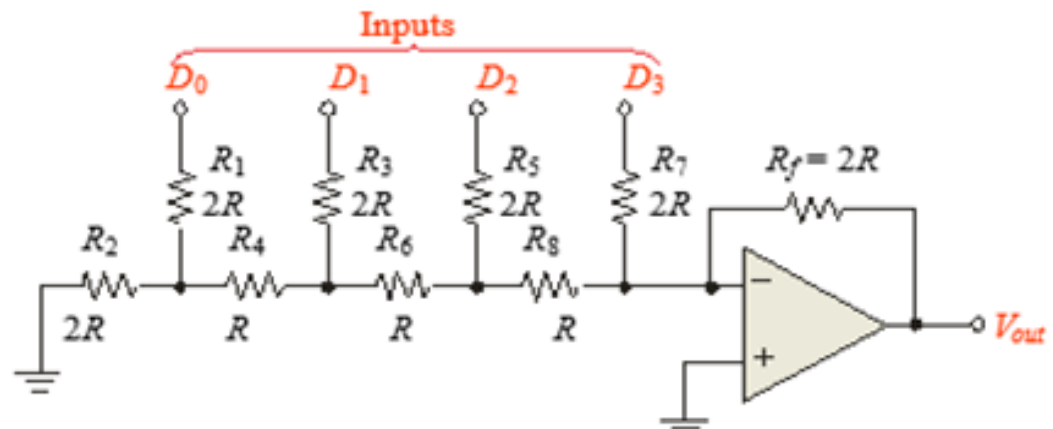
# Working

- ▶ The  $R$ - $2R$  ladder requires only two values of resistors.
- ▶ By calculating a Thevenin equivalent circuit for each input, the output is proportional to the binary weight of inputs that are HIGH.
- ▶ Each input that is HIGH contributes to the output:  $V_{out} = -\frac{V_s}{2^{n-i}}$
- ▶ where  $V_s$  = input HIGH level voltage,  $n$  = number of bits and  $i$  = bit number
- ▶ For accuracy, the resistors must be precise ratios, which is easily done in integrated circuits.





# 3 BIT DAC

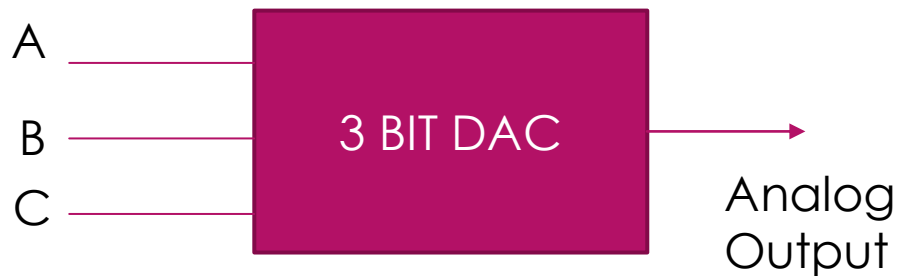


Digital Input			
C	B	A	Analog Output (in Volts)
0	0	0	0
0	0	1	1
0	1	0	2
0	1	1	3
1	0	0	4
1	0	1	5
1	1	0	6
1	1	1	7

# Working

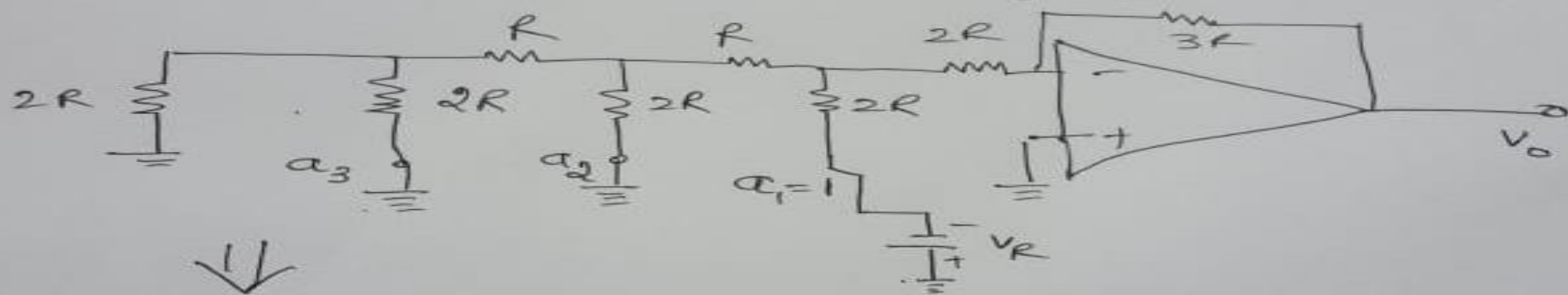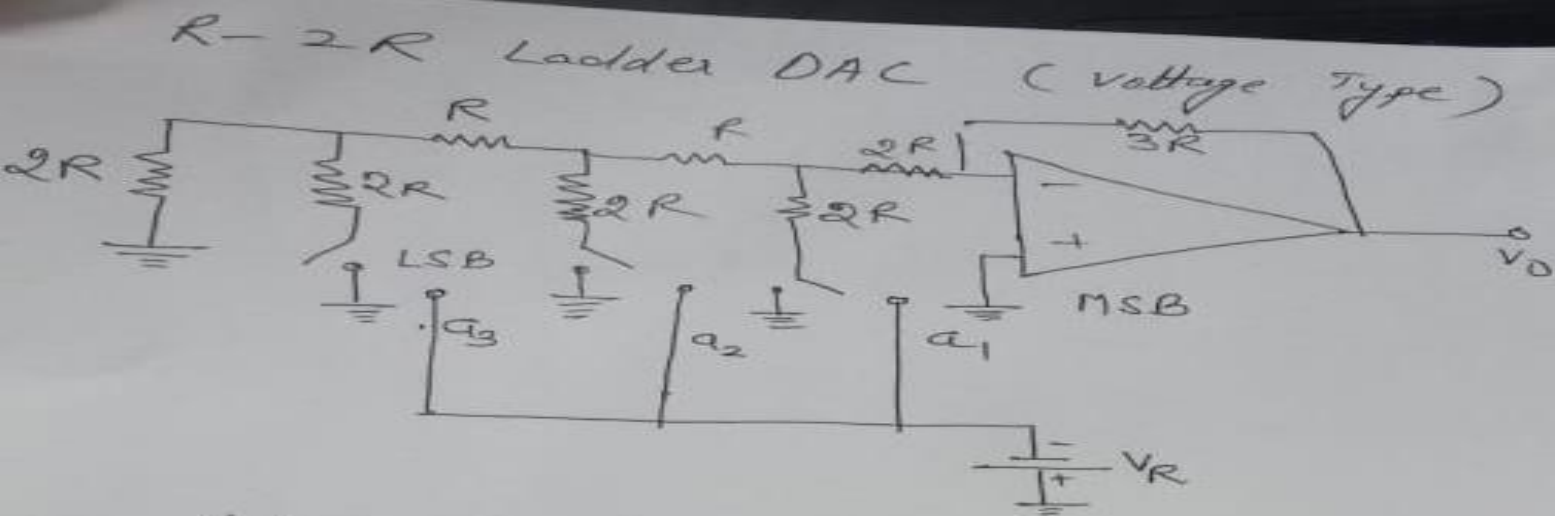


Contd..

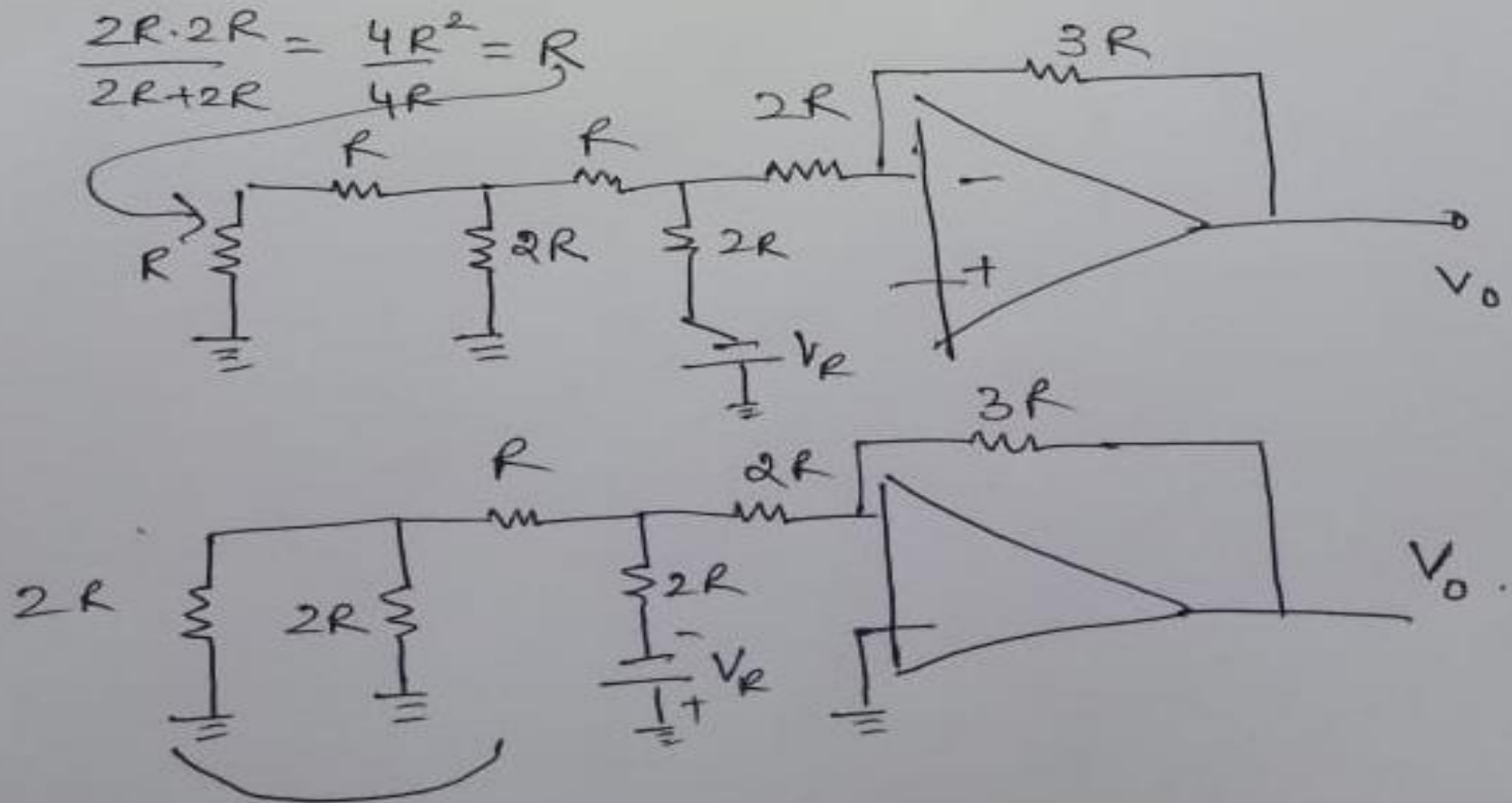

Contd..
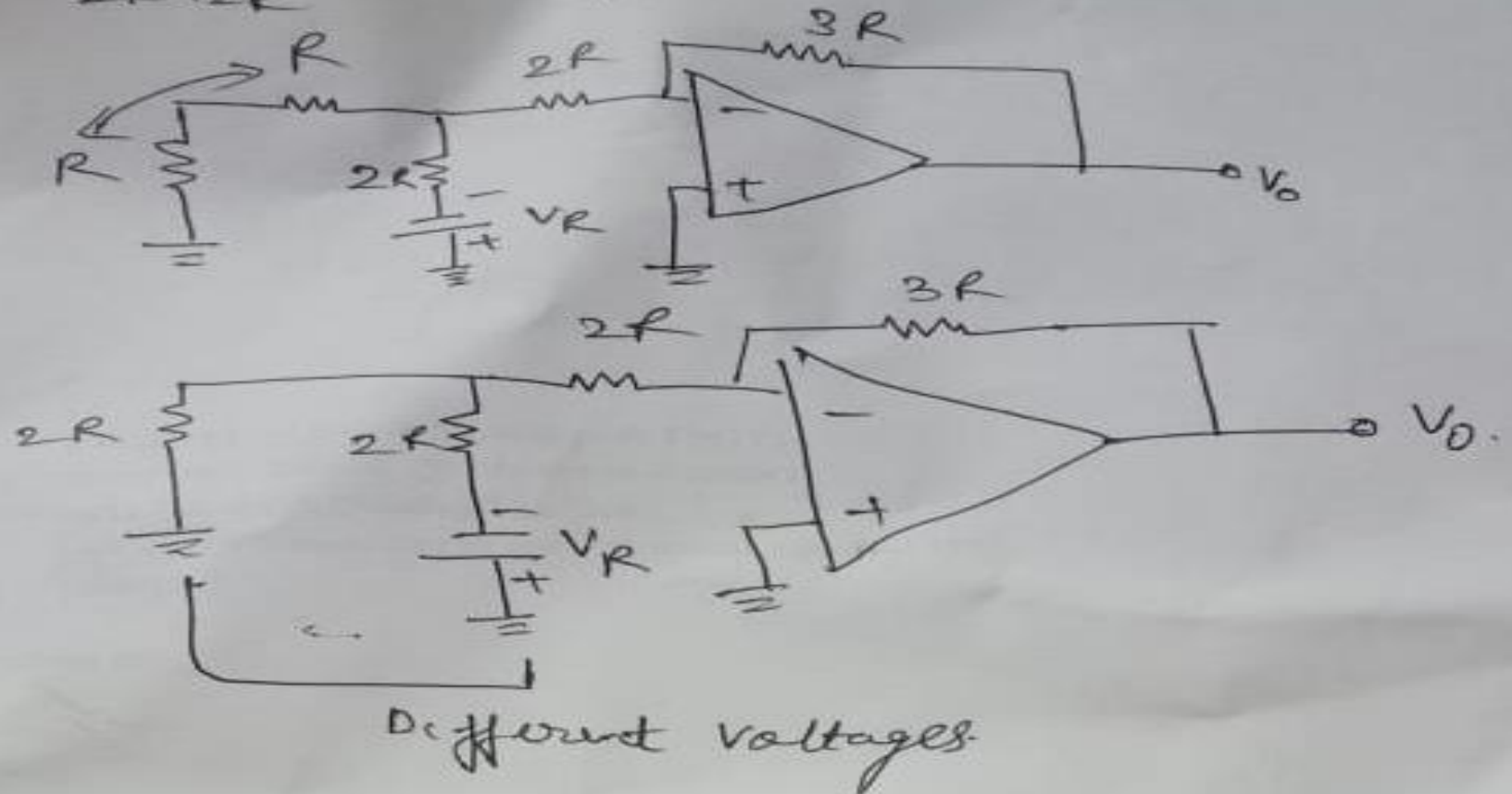
$$\frac{2R \cdot 2R}{2R + 2R} = \frac{4R^2}{4R} = R$$




Contd..


$$V_{th} = \frac{(-V_R) 2R}{2R + 2R}$$

$$V_{th} = -\frac{V_R \cdot 2R}{2R + 2R} = -\frac{V_R}{2}$$
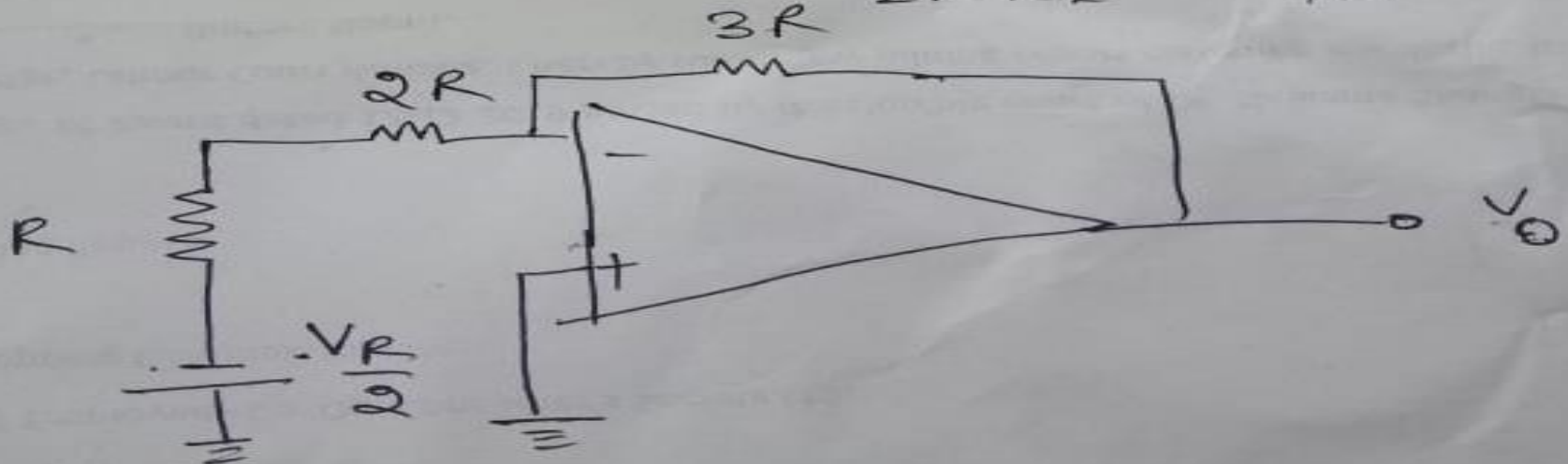
$$R_{th} = \frac{2R \cdot 2R}{2R + 2R} = \frac{4R^2}{4R} = R$$



Contd..


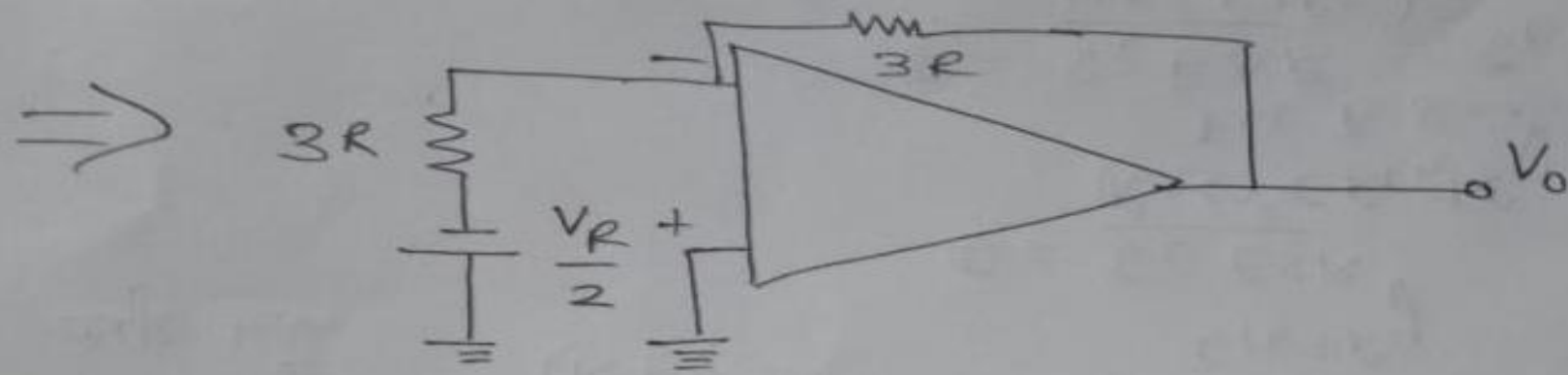


$$V_{out} = \frac{\text{feedback Resistor}}{\text{Input Resistor}} \times \text{input voltage}$$




$$= \frac{-(3R)}{3R} \left( -\frac{V_R}{2} \right) = \frac{V_R}{2}$$



# 4 Bit DAC

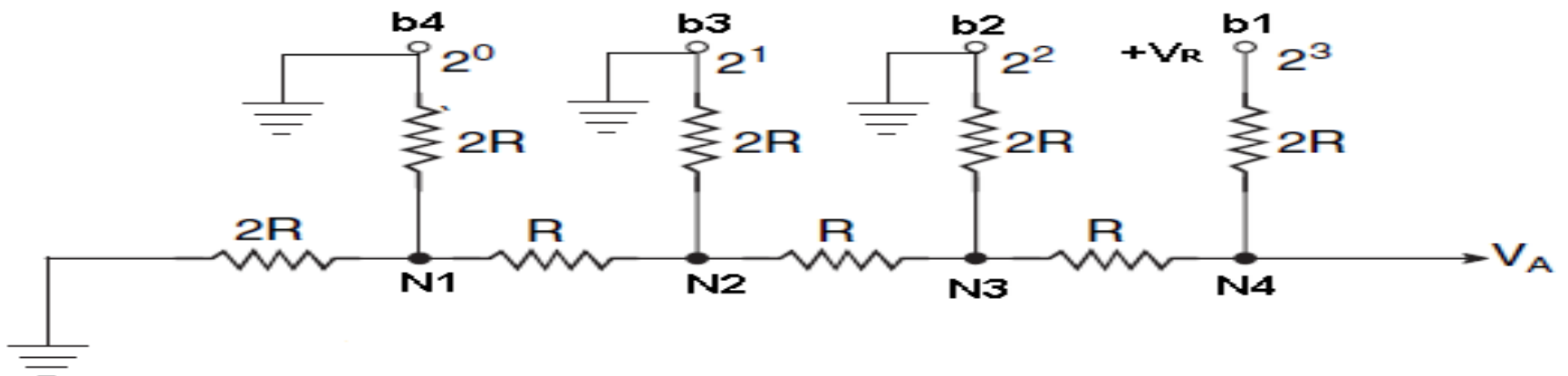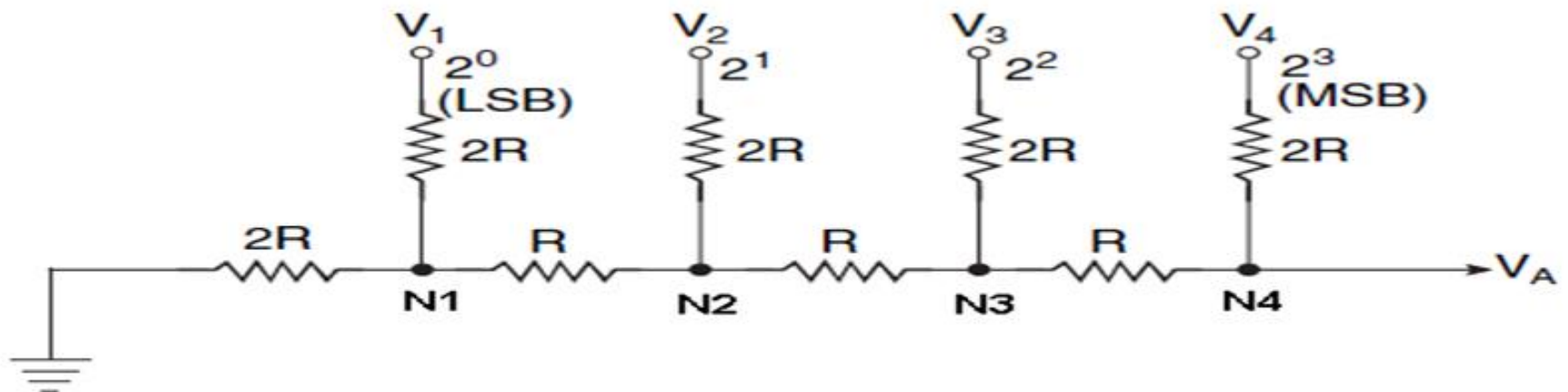

Contd..

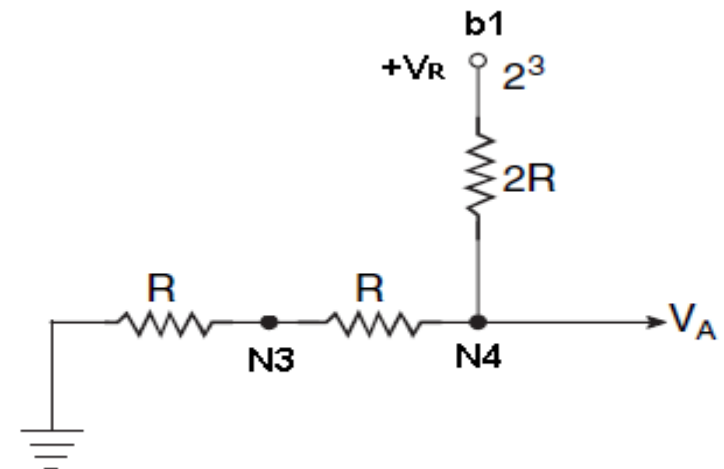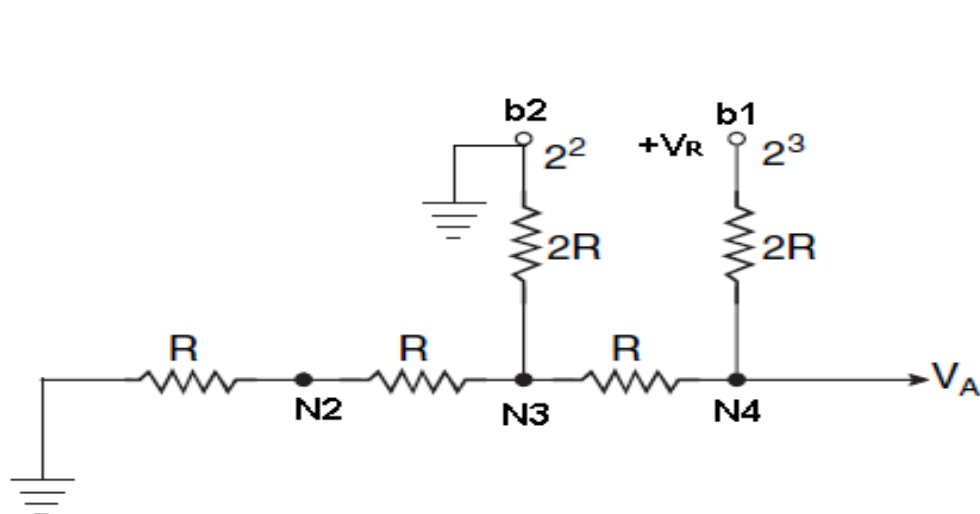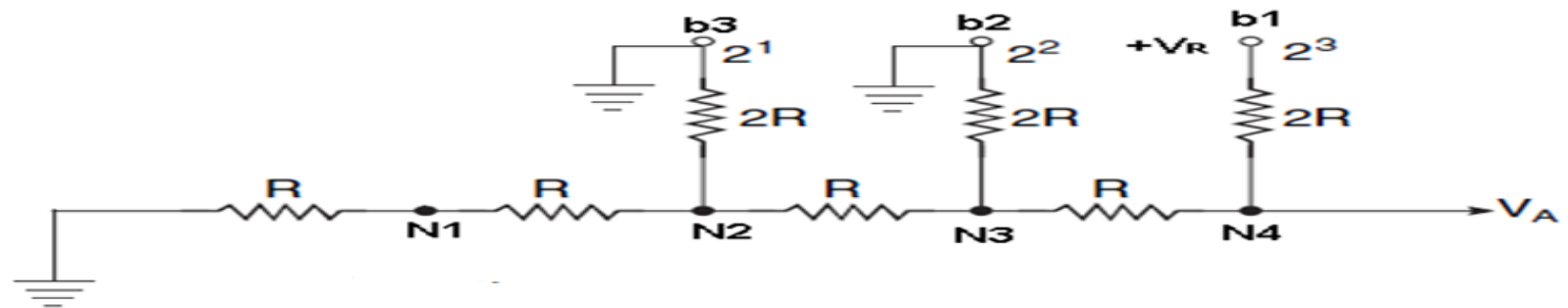

# Contd,


- ▶ Now at N4, calculate the output analog equivalent voltage i.e.
- ▶  $V_A = V_R * 2R / (R + R + 2R)$
- ▶  $= V_R / 2$
- ▶ By using superposition theorem one can find in any n-bit ladder network the output voltage will be
- ▶  $V_A = V_R / 2^1 + V_R / 2^2 + V_R / 2^3 + \dots + V_R / 2^n$

Example: An  $R$ - $2R$  ladder has a binary input of 1011. If a HIGH = +5.0 V and a LOW = 0 V, what is  $V_{out}$

Apply  $V_{out} = -\frac{V_S}{2^{n-i}}$  to all inputs that are HIGH, then sum the results.

$$V_{out}(D_0) = -\frac{5 \text{ V}}{2^{4-0}} = -0.3125 \text{ V} \quad V_{out}(D_1) = -\frac{5 \text{ V}}{2^{4-1}} = -0.625 \text{ V}$$
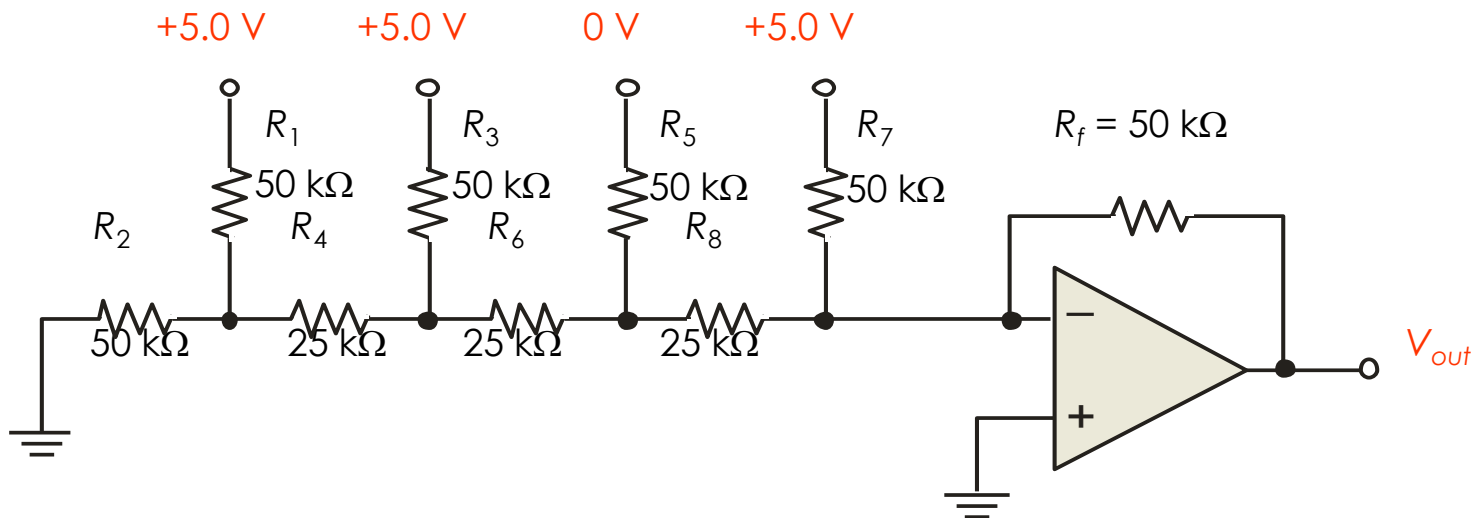
$$V_{out}(D_3) = -\frac{5 \text{ V}}{2^{4-3}} = -2.5 \text{ V} \quad \text{Applying superposition, } V_{out} = -3.43 \text{ V}$$



# Advantages and Disadvantages of R/2R ladder DACs

## Advantages

- ▶ Easier to build accurately as only two precision metal film resistors are required.
- ▶ Number of bits can be expanded by adding more sections of same **R/2R** values.
- ▶ In inverted **R/2R ladder DAC**, node voltages remain constant with changing input binary words.



## Disadvantages

- ▶ Slower conversion rate
- ▶ More confusing analysis


# Applications

## Digital to Analog Converter (DAC) and Its Applications

### Need of conversion

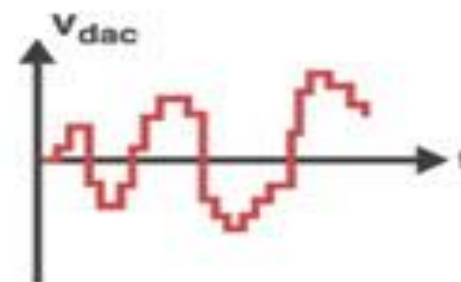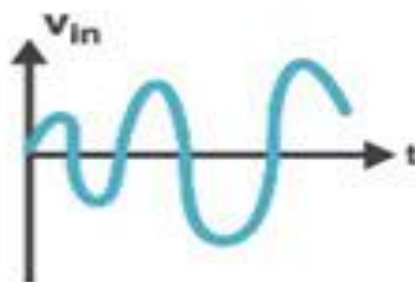

# DAC0808

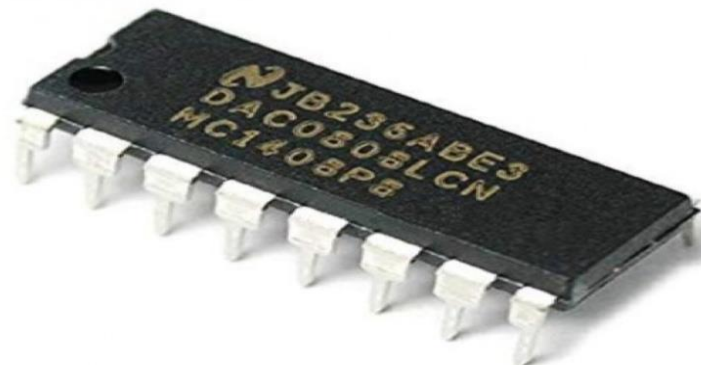

- ❖ Relative Accuracy:  $\pm 0.78\%$  error maximum
- ❖ Full Scale Error:  $\pm 1$  LSB typical
- ❖ Fast Settling Time: 150ns typical
- ❖ Noninverting Digital Inputs are TTL and CMOS Compatible
- ❖ High Speed Multiplying Input Slew Rate: 8mA/ $\mu$ s
- ❖ Power Supply Voltage Range:  $\pm 4.5$ V to  $\pm 18$ V
- ❖ Low Power Consumption: 33 mW @ $\pm 5$ V

# Thanks