

Thapar Institute of Engineering & Technology, Patiala

Department of Electronics and Communication Engineering
Course Code: UEC-301; **Course Name:** Analog Electronic Circuits
B.E. (ENC) (III-Sem),

Tutorial No.08

1	Find C_{de} , C_{je} , C_{π} , C_{μ} and f_T for a BJT operating at a dc collector current $I_C=1\text{mA}$ and CBJ reverse bias of 2 V. The device has $\tau_f=20\text{ps}$, $C_{je0}=20\text{fF}$, $C_{\mu0}=20\text{fF}$, $V_{oe}=0.9\text{V}$, $V_{oc}=0.5\text{V}$, and $m_{CBJ} = 0.33$.
2	For a BJT operated at $I_C=1\text{mA}$, determine C_{π} and f_T if $C_{\mu}=2\text{pF}$, $\beta_o=100$ and $h_{fe}=10$ at 50MHz.
3	Draw the BJT(npn) high frequency model.