

Thapar Institute of Engineering & Technology, Patiala

Department of Electronics and Communication Engineering

Course Code: UEC-301; **Course Name:** Analog Electronic Circuits

B.E. (ECE/ENC) (IV-Sem),

Tutorial Sheet No. - 4

[1] For the fixed-bias configuration of Fig. 1, determine

- a. I_{BQ} .
- b. I_{CQ} .
- c. V_{CEQ} .
- d. V_C .
- e. V_B .
- f. V_E .

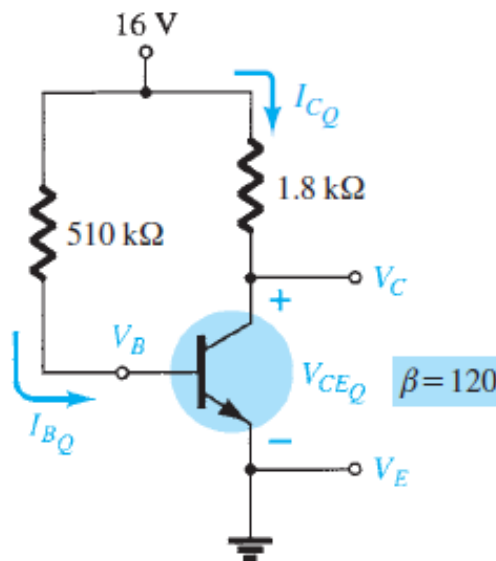


Fig. 1

[2]

Given the BJT transistor characteristics of Fig. 2:

- Draw a load line on the characteristics determined by $E = 21\text{ V}$ and $R_C = 3\text{ k}\Omega$ for a fixed-bias configuration.
- Choose an operating point midway between cutoff and saturation. Determine the value of R_B to establish the resulting operating point.
- What are the resulting values of I_{CQ} and V_{CEQ} ?
- What is the value of β at the operating point?
- What is the value of α defined by the operating point?
- What is the saturation current (I_{Csat}) for the design?
- Sketch the resulting fixed-bias configuration.
- What is the dc power dissipated by the device at the operating point?
- What is the power supplied by V_{CC} ?
- Determine the power dissipated by the resistive elements by taking the difference between the results of parts (h) and (i).

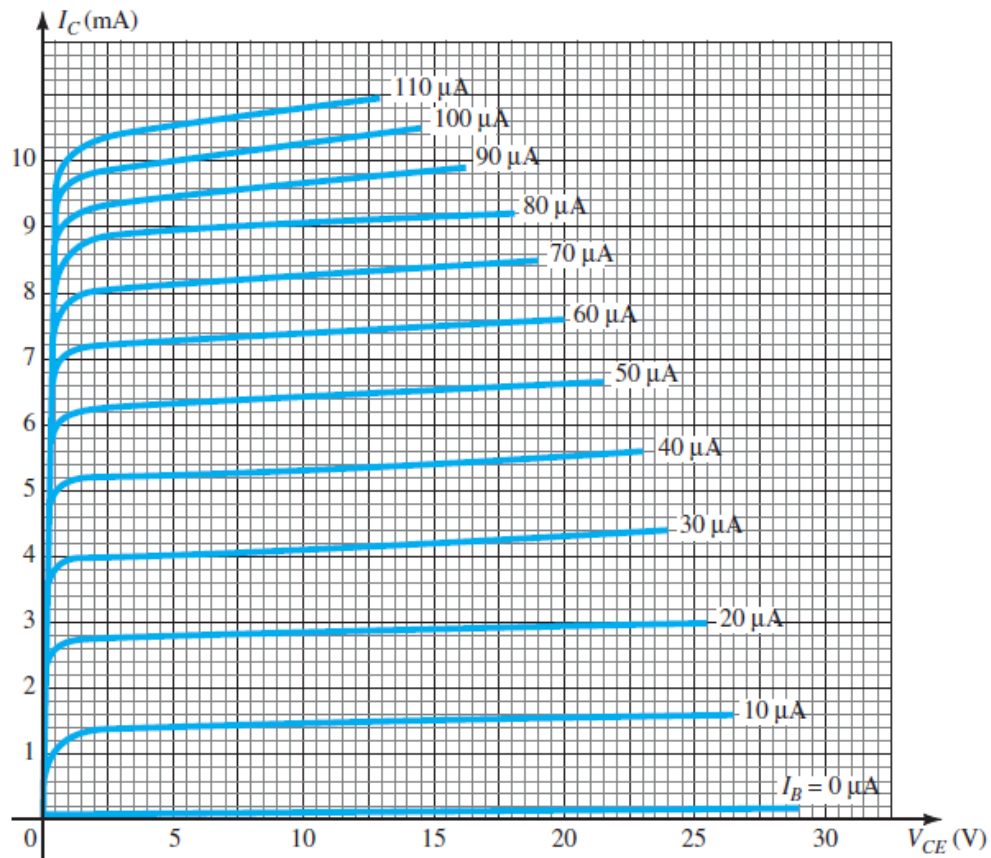


Fig. 2

[3]

If the base resistor of Fig. 1 is increased to 910 kohm, find the new Q -point and resulting values of I_{CQ} and V_{CEQ} .

[4]

Given the information provided in Fig. 3, determine:

- R_C .
- R_E .

- c. R_B .
- d. V_{CE} .
- e. V_B .

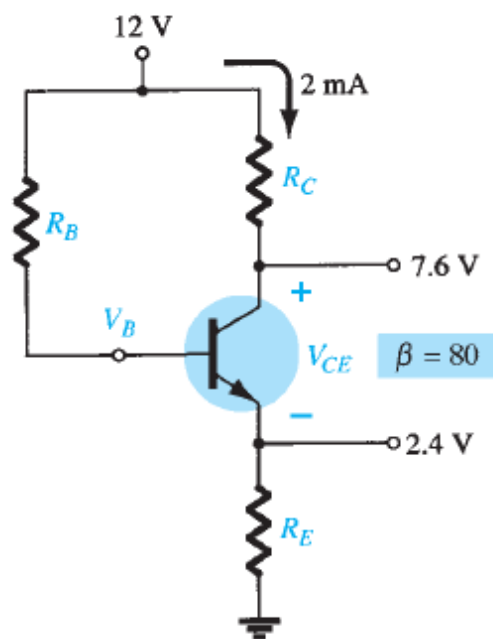


Fig. 3