

Tut Sheet -4
Solution

Ans. 1.

1. (a) $I_{B_Q} = \frac{V_{CC} - V_{BE}}{R_B} = \frac{16 \text{ V} - 0.7 \text{ V}}{470 \text{ k}\Omega} = \frac{15.3 \text{ V}}{470 \text{ k}\Omega} = \mathbf{32.55 \mu A}$
- (b) $I_{C_Q} = \beta I_{B_Q} = (90)(32.55 \mu A) = \mathbf{2.93 \text{ mA}}$
- (c) $V_{CE_Q} = V_{CC} - I_{C_Q} R_C = 16 \text{ V} - (2.93 \text{ mA})(2.7 \text{ k}\Omega) = \mathbf{8.09 \text{ V}}$
- (d) $V_C = V_{CE_Q} = \mathbf{8.09 \text{ V}}$
- (e) $V_B = V_{BE} = \mathbf{0.7 \text{ V}}$
- (f) $V_E = \mathbf{0 \text{ V}}$

Ans. 2.

- (a) Load line intersects vertical axis at $I_C = \frac{21 \text{ V}}{3 \text{ k}\Omega} = 7 \text{ mA}$
and horizontal axis at $V_{CE} = 21 \text{ V}$.
- (b) $I_B = 25 \mu A$: $R_B = \frac{V_{CC} - V_{BE}}{I_B} = \frac{21 \text{ V} - 0.7 \text{ V}}{25 \mu A} = \mathbf{812 \text{ k}\Omega}$
- (c) $I_{C_Q} \cong \mathbf{3.4 \text{ mA}}$, $V_{CE_Q} \cong \mathbf{10.75 \text{ V}}$
- (d) $\beta = \frac{I_C}{I_B} = \frac{3.4 \text{ mA}}{25 \mu A} = \mathbf{136}$
- (e) $\alpha = \frac{\beta}{\beta + 1} = \frac{136}{136 + 1} = \frac{136}{137} = \mathbf{0.992}$
- (f) $I_{C_{sat}} = \frac{V_{CC}}{R_C} = \frac{21 \text{ V}}{3 \text{ k}\Omega} = \mathbf{7 \text{ mA}}$
- (g) —
- (h) $P_D = V_{CE_Q} I_{C_Q} = (10.75 \text{ V})(3.4 \text{ mA}) = \mathbf{36.55 \text{ mW}}$
- (i) $P_s = V_{CC}(I_C + I_B) = 21 \text{ V}(3.4 \text{ mA} + 25 \mu A) = \mathbf{71.92 \text{ mW}}$
- (j) $P_R = P_s - P_D = 71.92 \text{ mW} - 36.55 \text{ mW} = \mathbf{35.37 \text{ mW}}$

Ans. 3

$$I_{B_Q} = \frac{16 \text{ V} - 0.7 \text{ V}}{910 \text{ k}\Omega} = 16.81 \mu\text{A}$$

$$I_{C_Q} = \beta I_{B_Q} = (120)(16.81 \mu\text{A}) = \mathbf{2.017 \text{ mA}}$$

$$\text{(from characteristics)} \quad V_{E_Q} = \mathbf{11.5 \text{ V}}, \quad I_{C_Q} = \mathbf{2.4 \text{ mA}}$$

Ans.4

$$\text{(a)} \quad R_C = \frac{V_{CC} - V_C}{I_C} = \frac{12 \text{ V} - 7.6 \text{ V}}{2 \text{ mA}} = \frac{4.4 \text{ V}}{2 \text{ mA}} = \mathbf{2.2 \text{ k}\Omega}$$

$$\text{(b)} \quad I_E \cong I_C: \quad R_E = \frac{V_E}{I_E} = \frac{2.4 \text{ V}}{2 \text{ mA}} = \mathbf{1.2 \text{ k}\Omega}$$

$$\text{(c)} \quad R_B = \frac{V_{R_B}}{I_B} = \frac{V_{CC} - V_{BE} - V_E}{I_B} = \frac{12 \text{ V} - 0.7 \text{ V} - 2.4 \text{ V}}{2 \text{ mA}/80} = \frac{8.9 \text{ V}}{25 \mu\text{A}} = \mathbf{356 \text{ k}\Omega}$$

$$\text{(d)} \quad V_{CE} = V_C - V_E = 7.6 \text{ V} - 2.4 \text{ V} = \mathbf{5.2 \text{ V}}$$

$$\text{(e)} \quad V_B = V_{BE} + V_E = 0.7 \text{ V} + 2.4 \text{ V} = \mathbf{3.1 \text{ V}}$$