

# Analog Electronic Circuits (UEC301)

By



**Dr. Mayank Kumar Rai**  
**Associate Professor,**  
**ECED, TIET, Patiala**

Thapar Institute of Engineering & Technology  
(Deemed to be University)  
Bhadson Road, Patiala, Punjab, Pin-147004  
Contact No. : +91-175-2393201  
Email : [info@thapar.edu](mailto:info@thapar.edu)

**ti**  
**THAPAR INSTITUTE**  
OF ENGINEERING & TECHNOLOGY  
(Deemed to be University)



# Subject: Analog Electronic Circuits (UEC301)

Faculty names: Dr. Mayank Kumar Rai ( Associate Professor & Course Coordinator)

Topic of today's Lecture : Small Signal Models and Operation of Enhancement Mode NMOS

## Key points

Contents of this lecture are based on the following books:


- **Second Order Effects**
- **Small Signal Low Frequency Models of Enhancement Mode NMOS**
- **Small Signal high frequency model of Enhancement Mode NMOS**
- **Small Signal Parameters**
- **Types of Single Stage Amplifier**
- **Low Frequency Small Signal operation of Single Stage Common Source Amplifier**

- *Jacob Milman & C.C.Halkias, “Integrated Electronics Analog and Digital Circuit and Systems” Second Edition.*
- *Adel S. Sedra & K. C. Smith, “MicroElectronic Circuits Theory and Application” Fifth Edition.*
- *Robert L. Boylestad & L. Nashelsky, “Electronic Devices and Circuit Theory” Eleventh Edition.*




# Second Order Effects


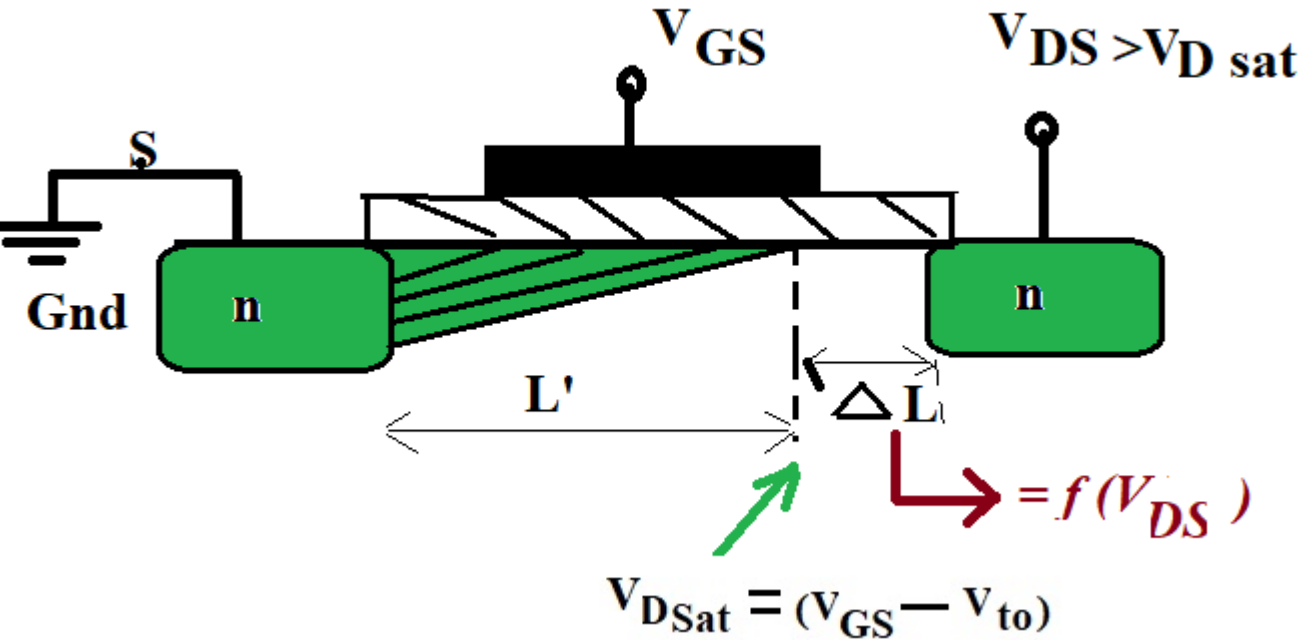
## (i) Channel length Modulation(Lambda effect )



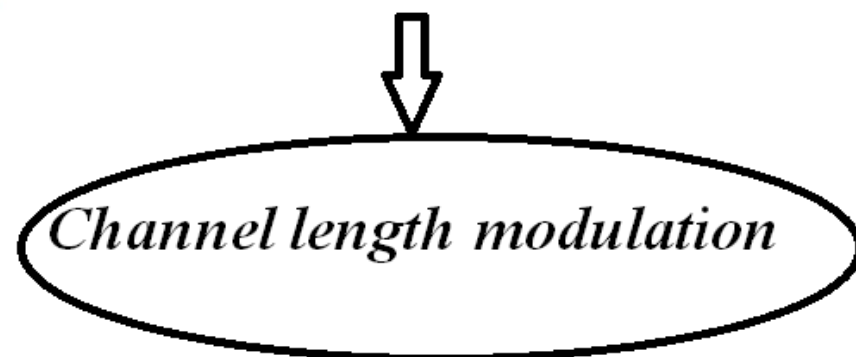As  $V_{DS}$  increases ( $V_{DS} > V_{DS,sat}$ ), the channel gradually moves toward the source end i.e. The channel length decreases ( $L$ ) with increase in  $V_{DS}$



## (ii) Body Effect( $\gamma$ effect)

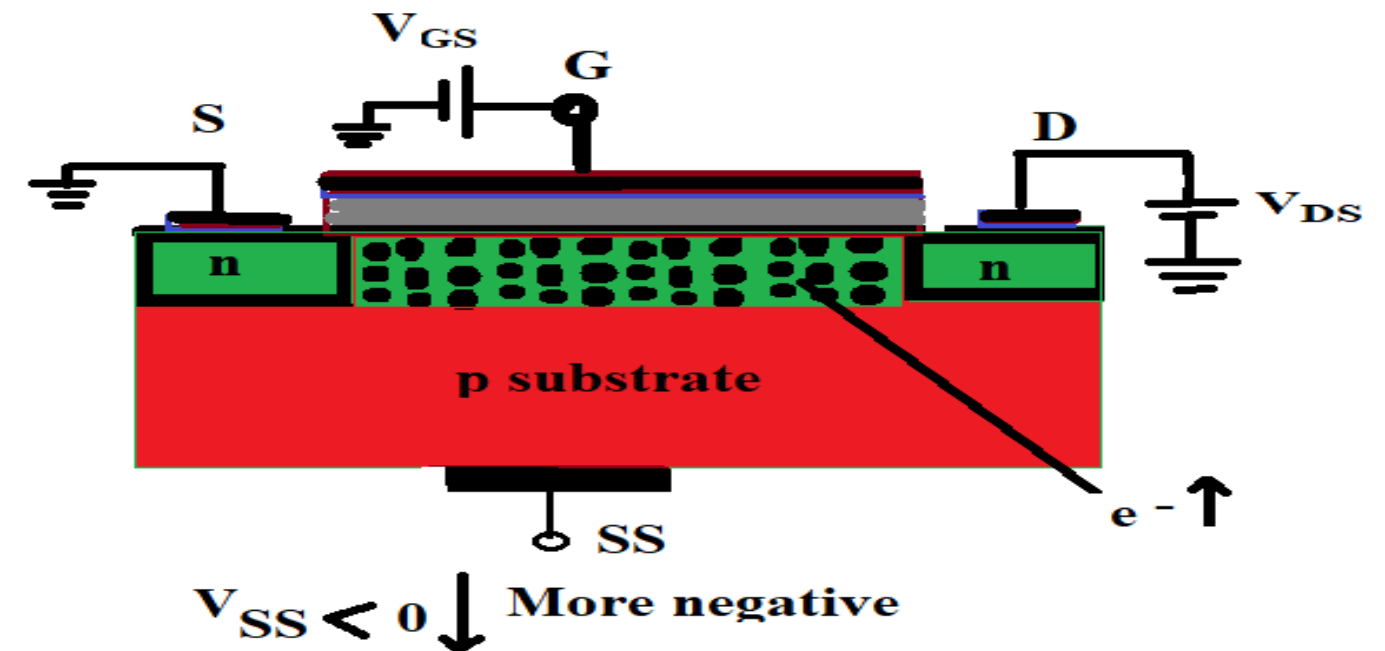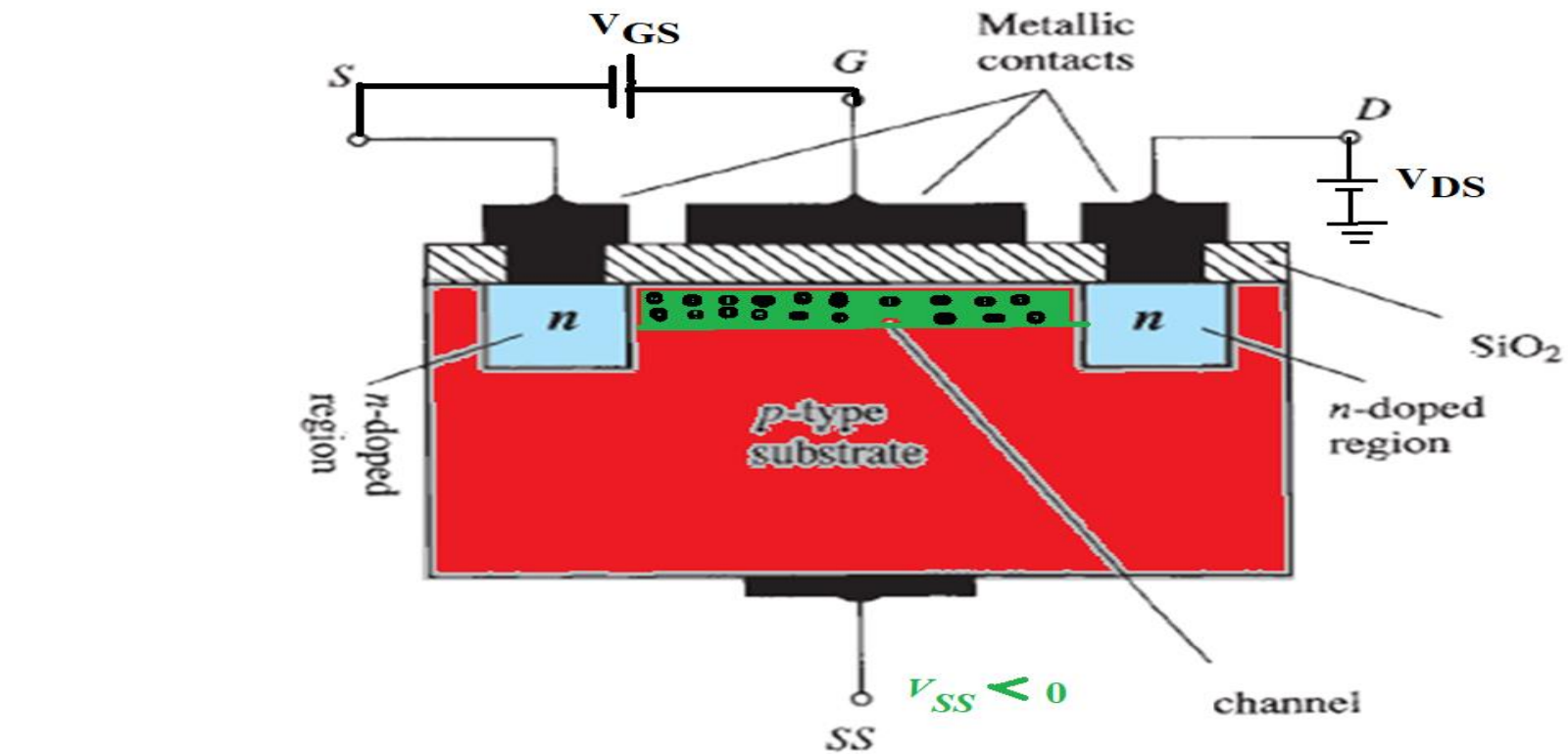

# Small Signal Low Frequency Models of Enhancement Mode NMOS

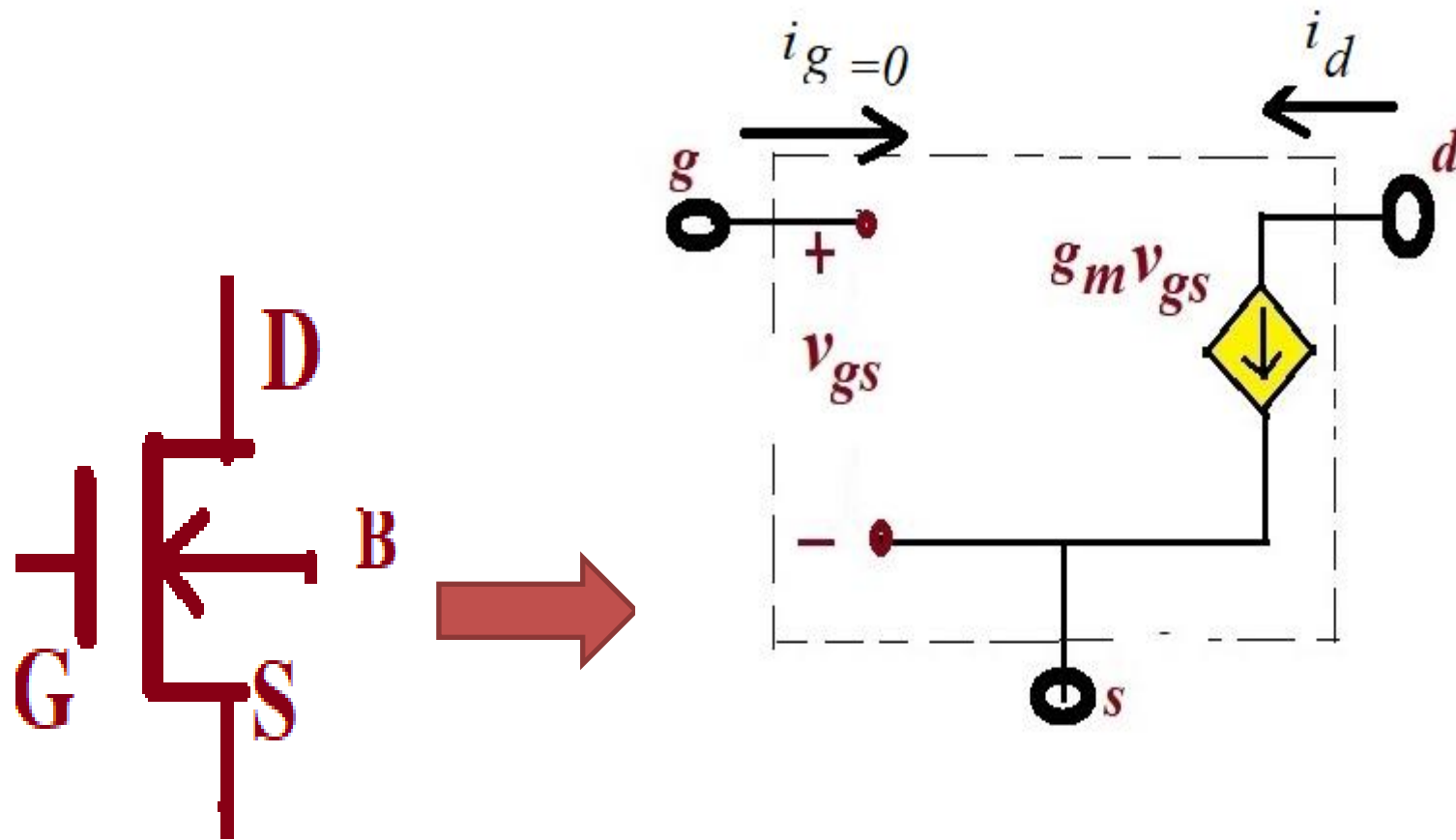


Figure 1 : The small signal  $\pi$  model without channel length and body effect.

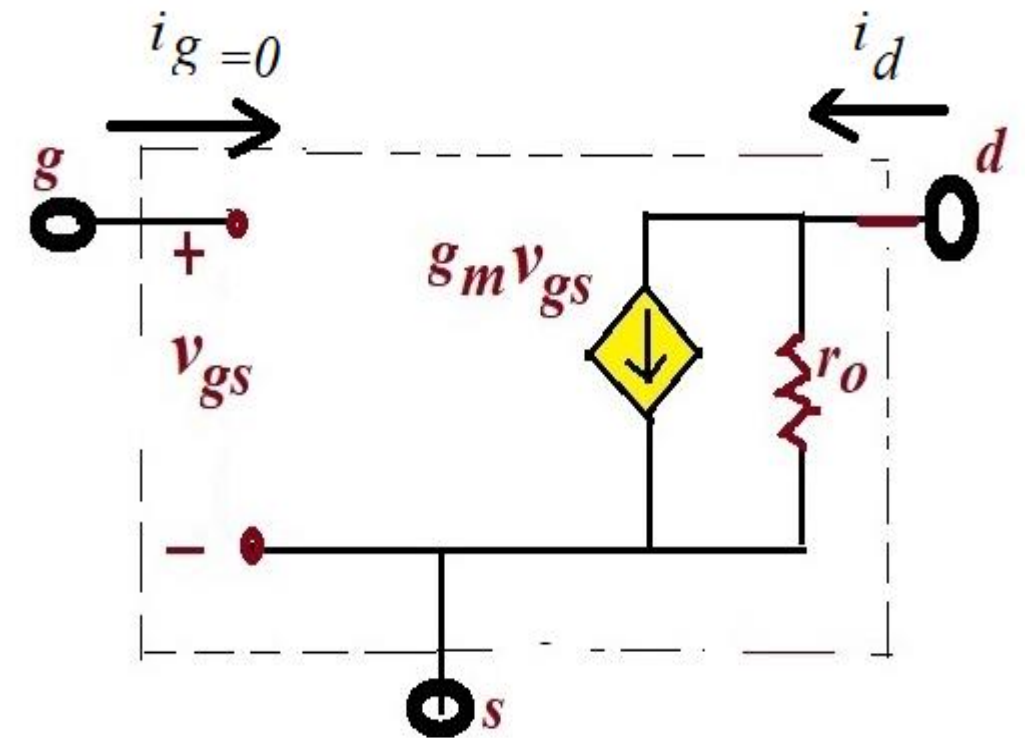


Figure 2 : The small signal  $\pi$  model with channel length modulation and without body effect ( $\gamma = 0$ ).

# Small Signal High Frequency Model of Enhancement Mode NMOS

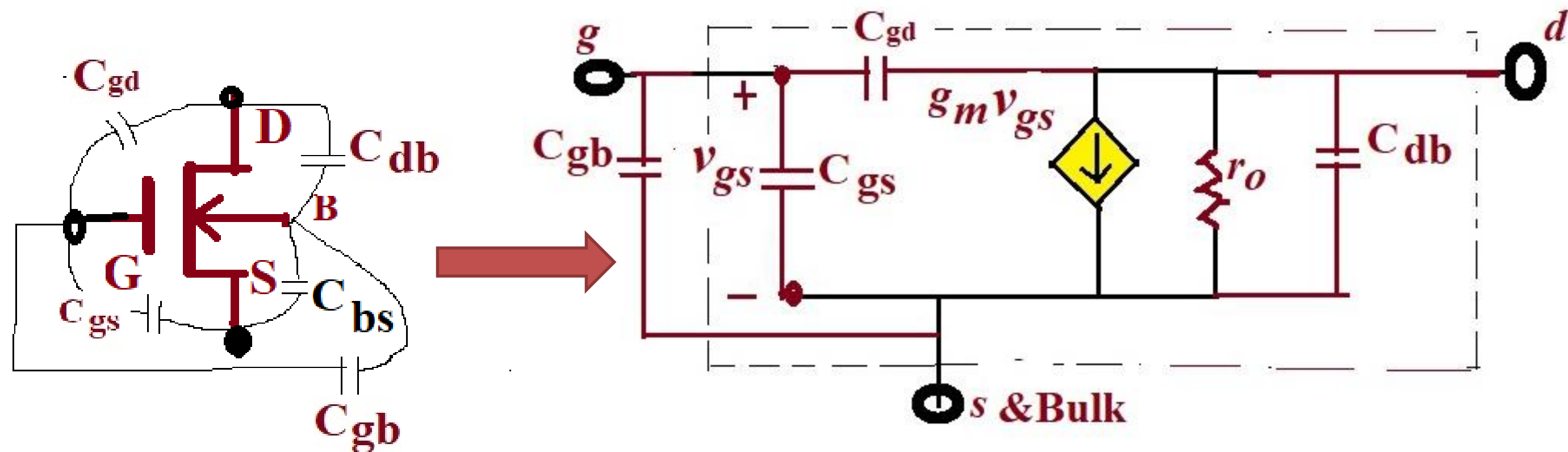


Figure 3: High frequency  $\pi$  model of enhancement mode NMOS with no body effect.

## Small signal parameters

$$i_D = \frac{1}{2} \mu_n C_{OX} \frac{W}{L} (v_{GS} - V_{to})^2 \dots\dots\dots(1),$$

$$i_D = \frac{1}{2} \mu_n C_{OX} \frac{W}{L} (V_{GS} + v_{gs} - V_{to})^2 \dots\dots\dots(2),$$

$$i_D = \frac{1}{2} \mu_n C_{OX} \frac{W}{L} (V_{GS} - V_{to})^2 + \mu_n C_{OX} \frac{W}{L} (V_{GS} - V_{to}) v_{gs} + \frac{1}{2} \mu_n C_{OX} \frac{W}{L} v_{gs}^2 \dots\dots\dots(3),$$

$$\frac{1}{2} \mu_n C_{OX} \frac{W}{L} v_{gs}^2 \ll \mu_n C_{OX} \frac{W}{L} (V_{GS} - V_{to}) v_{gs} \dots\dots\dots(4),$$

resulting in

$$v_{gs} \ll 2(V_{GS} - V_{to}) \dots\dots\dots(5),$$

$$V_{OV} = (V_{GS} - V_{to}) \dots\dots\dots(6),$$

$$i_D = I_D + i_d \dots\dots\dots(7),$$

$$i_d = \mu_n C_{OX} \frac{W}{L} (V_{GS} - V_{to}) v_{gs} \dots\dots(8),$$

$$g_m = \frac{i_d}{v_{gs}} = \mu_n C_{OX} \frac{W}{L} (V_{GS} - V_{to}) \dots \dots (9),$$

from graphical interpretation

$$g_m = \frac{\partial i_D}{\partial v_{GS}} \text{ at const } V_{DS} \dots \dots \dots (10),$$

$$r_o = \frac{\partial V_{DS}}{\partial I_D} \dots \dots \dots (11),$$

$$I_D \approx \frac{1}{2} \mu_n C_{OX} \frac{W}{L} (V_{GS} - V_{to})^2 (1 + \lambda V_{DS}) \dots \dots \dots (12),$$

$$r_o = \frac{1}{\frac{\partial I_D}{\partial V_{DS}}} = \frac{1}{\frac{1}{2} \mu_n C_{OX} \frac{W}{L} (V_{GS} - V_{to})^2 \cdot \lambda} \dots \dots \dots (13),$$

$$r_o = \frac{1}{I_D \cdot \lambda} \dots \dots \dots (14),$$

where  $\lambda = \frac{1}{V_A}$

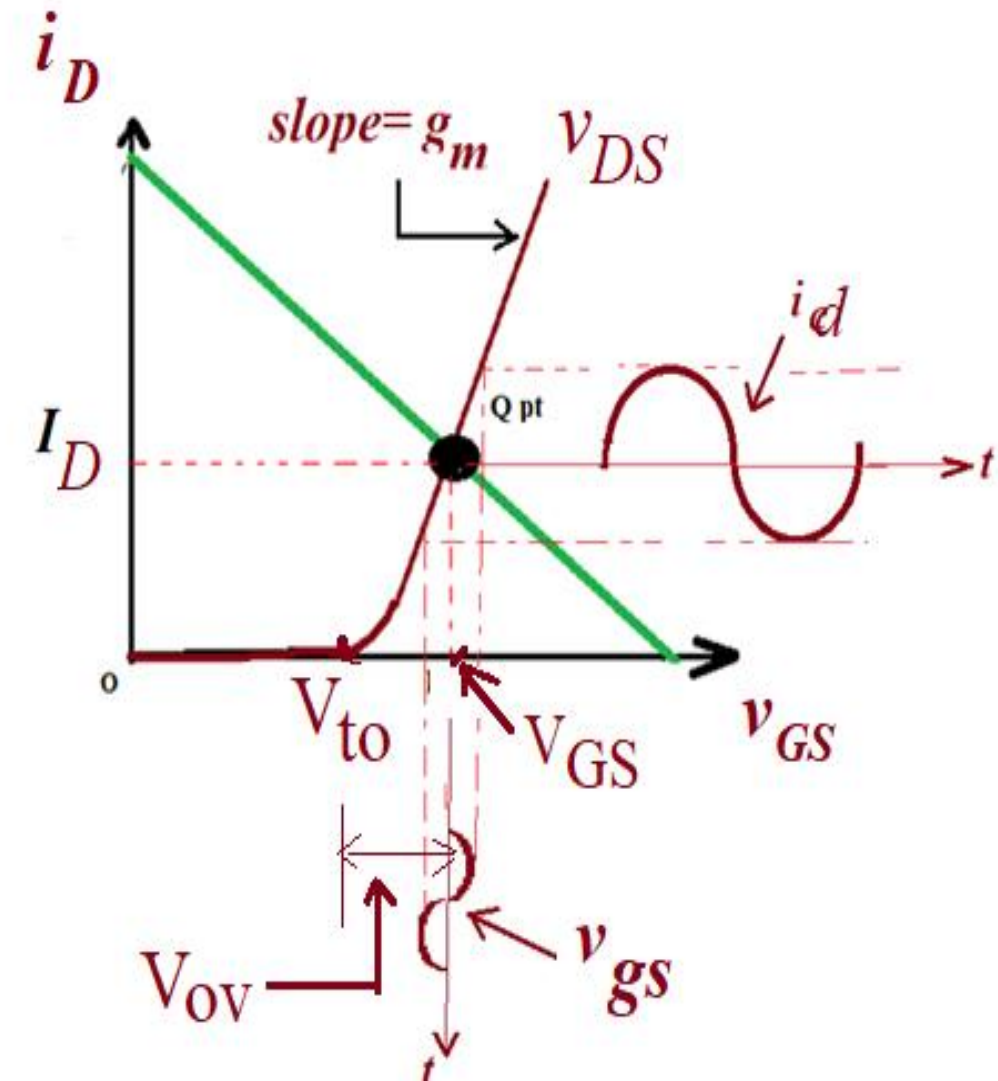


Figure 4 :  $i_D$ -  $v_{GS}$  characteristic at the bias point.

# Types of Single Stage Amplifier

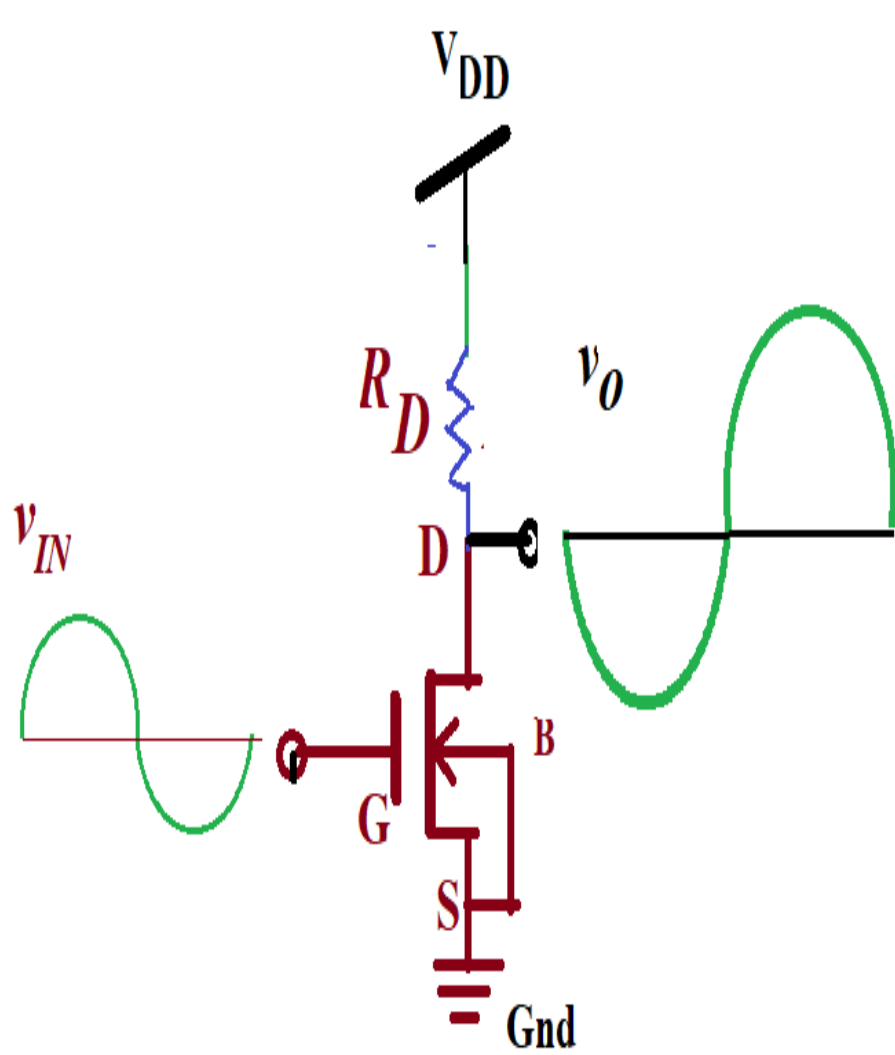


Figure 5: The Common source stage.

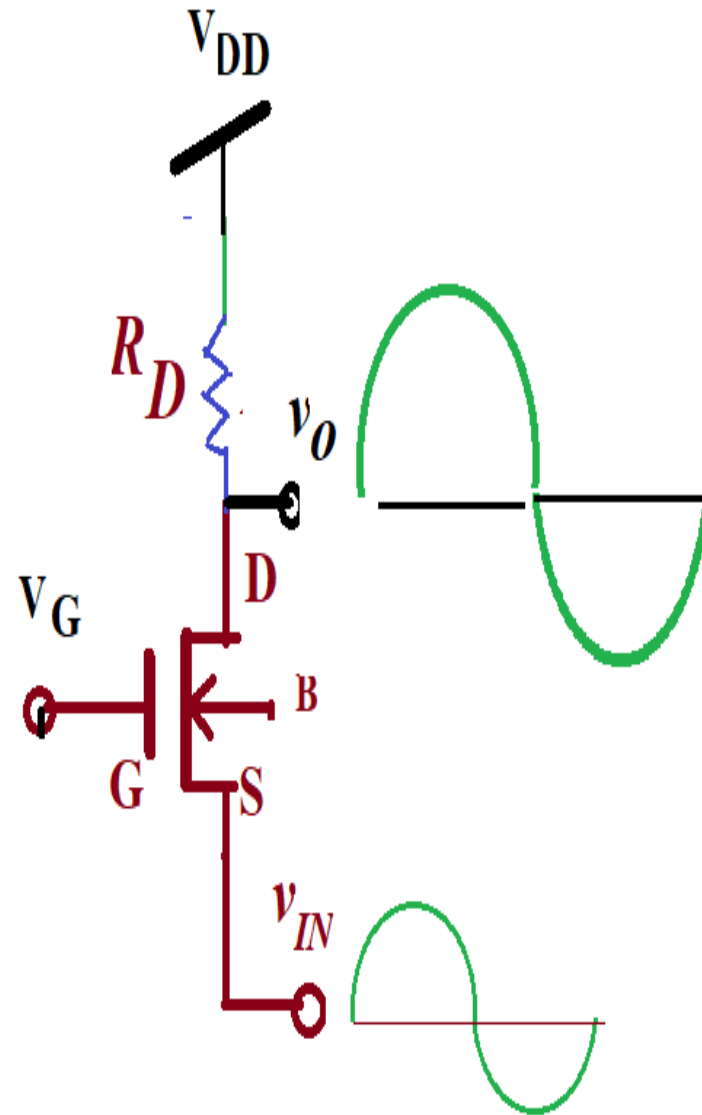


Figure 6: The Common gate stage.

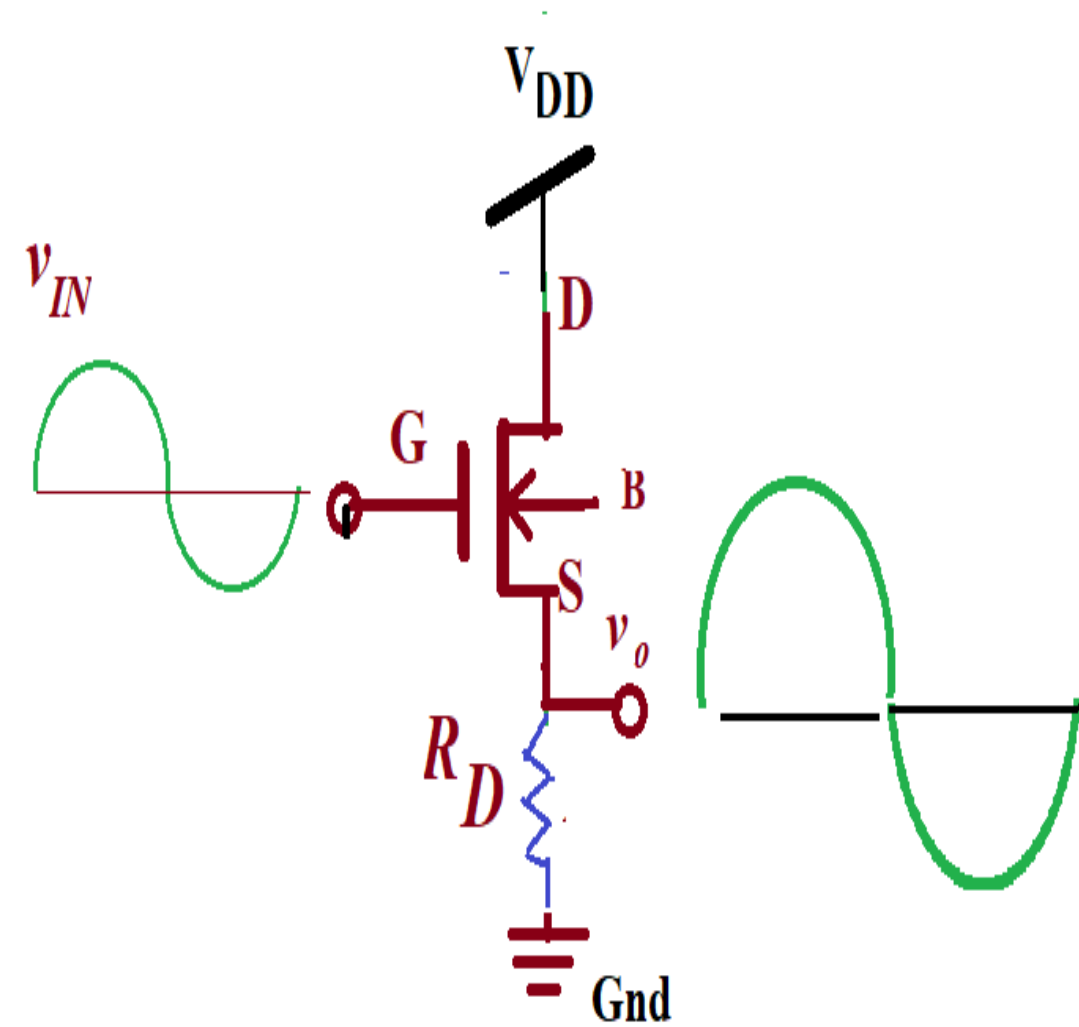


Figure 7: The Common drain stage.



# Low Frequency Small Signal operation of Single Stage Common Source Amplifier

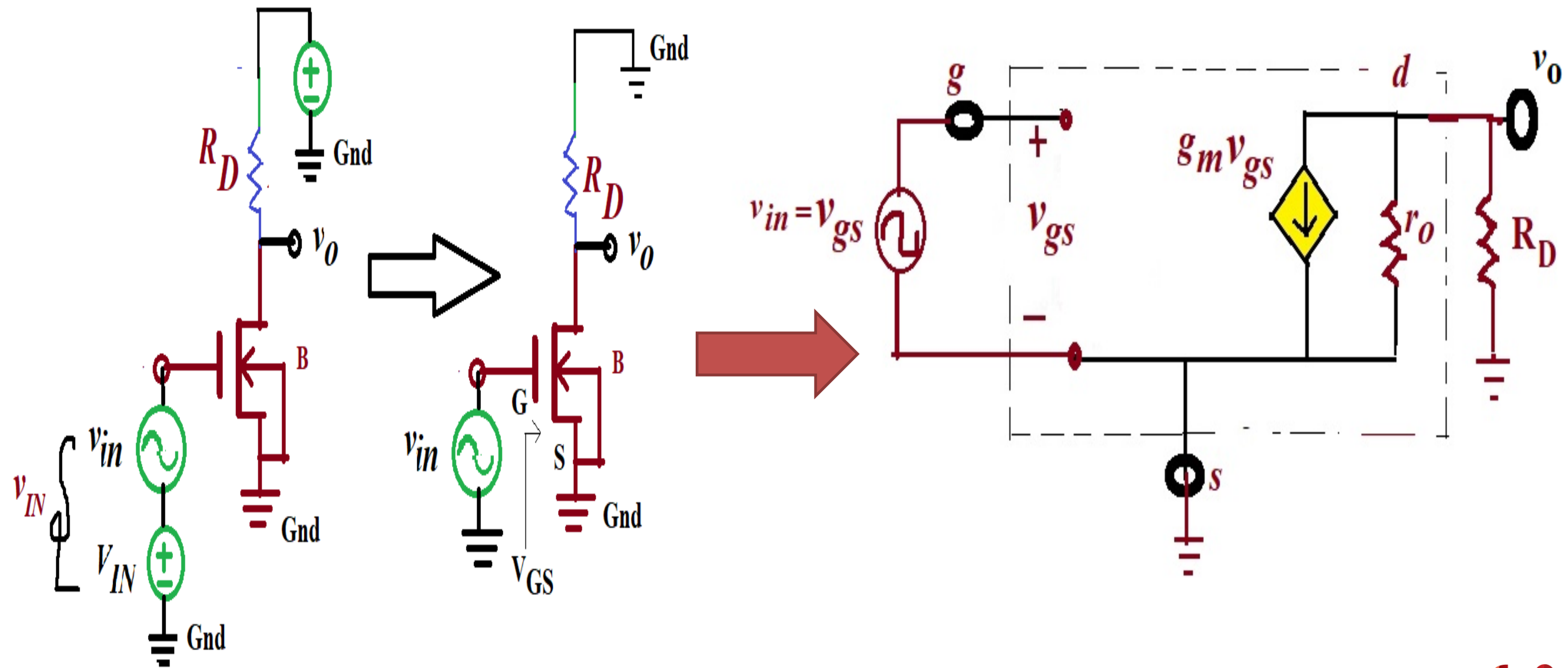


Figure 8: Small signal equivalent  $\pi$  model based single stage common source amplifier circuit with no body effect.

## Small Signal operation.....

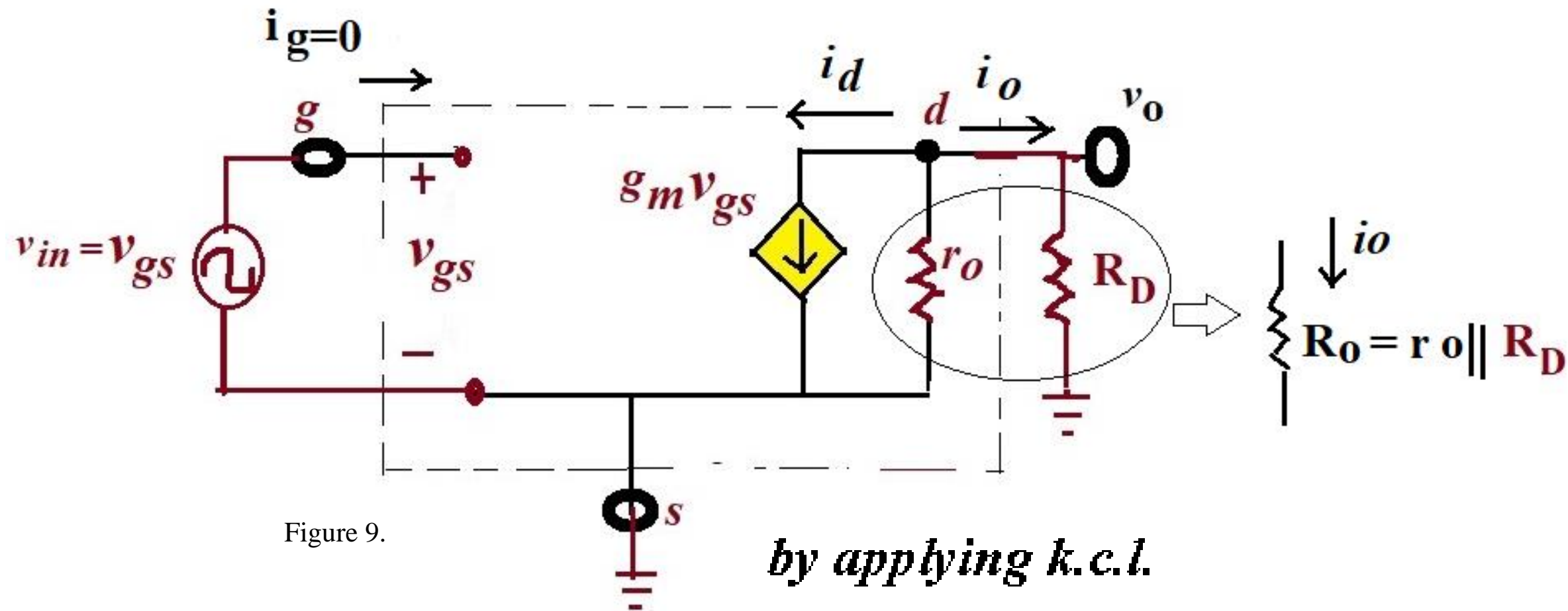


Figure 9.

*by applying k.c.l.*

$$i_o + i_d = 0 \dots\dots\dots(15)$$

$$v_o = i_o R_o = -i_d R_o = -g_m v_{GS} R_o \dots\dots(16)$$

$$A_v = \frac{v_o}{v_{in} = v_{GS}} = -g_m R_o \dots\dots(17)$$

$$R_o = r_o || R_D \dots\dots(18)$$

***Thank You***

