

Thapar Institute of Engineering & Technology, Patiala
Department of Electronics and Communication Engineering
Course Code: UEC-301; **Course Name:** Analog Electronic Circuits
B.E. (ENC) (III-Sem),
"Tutorial Sheet No. - 10"

Q1.

- (A) Calculate the input and output power for the circuit of Fig. 1. The input signal results in a base current of 5 mA rms.
- (B) Calculate the input power dissipated by the circuit of Fig. 1 if R_B is changed to 1.5 k ohm.
- (C) What maximum output power can be delivered by the circuit of Fig. 1 if R_B is changed to 1.5 k ohm?
- (D) If the circuit of Fig. 1 is biased at its center voltage and center collector operating point, what is the input power for a maximum output power of 1.5 W?

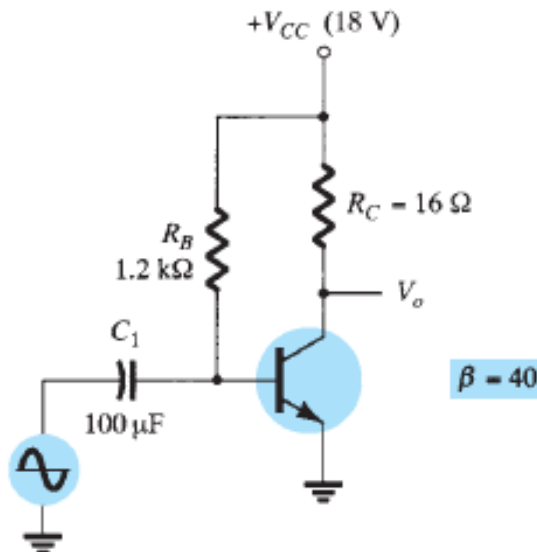


Fig. 1

- Q2.** Calculate the input power, output power, and efficiency of the amplifier circuit in Fig. 2 for an input voltage that results in a base current of 10 mA peak.

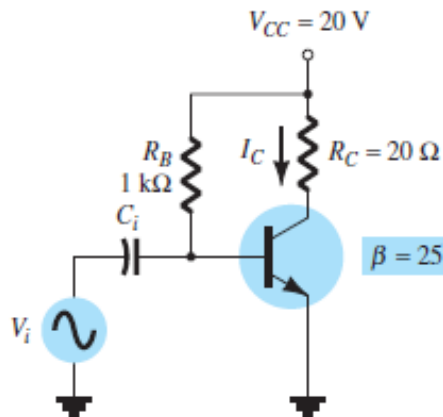


Fig. 2