

Analog Electronic Circuits (UEC301)

By



Dr. Mayank Kumar Rai
Associate Professor,
ECED, TIET, Patiala

Thapar Institute of Engineering & Technology
(Deemed to be University)
Bhadson Road, Patiala, Punjab, Pin-147004
Contact No. : +91-175-2393201
Email : info@thapar.edu

ti
THAPAR INSTITUTE
OF ENGINEERING & TECHNOLOGY
(Deemed to be University)

Subject: Analog Electronic Circuits (UEC301)

Faculty name: Dr. Mayank Kumar Rai (Associate Professor & Course Coordinator)

Topic of today's Lecture : Oscillator

Key points

- ✓ Oscillator
- ✓ Types of Oscillator
- ✓ RC Phase shift Oscillator
- ✓ Hartley and Colpitts Oscillators


Contents of this lecture are based on the following books:

- *Jacob Milman & and C.C.Halkias, “Integrated Electronics Analog and Digital Circuit and Systems”Second Edition.*
- *Adel S. Sedra & K. C. Smith, “MicroElectronic Circuits Theory and Application” Fifth Edition.*
- *Robert L. Boylestad & L. Nashelsky, “Electronic Devices and Circuit Theory” Eleventh Edition.*




Oscillator

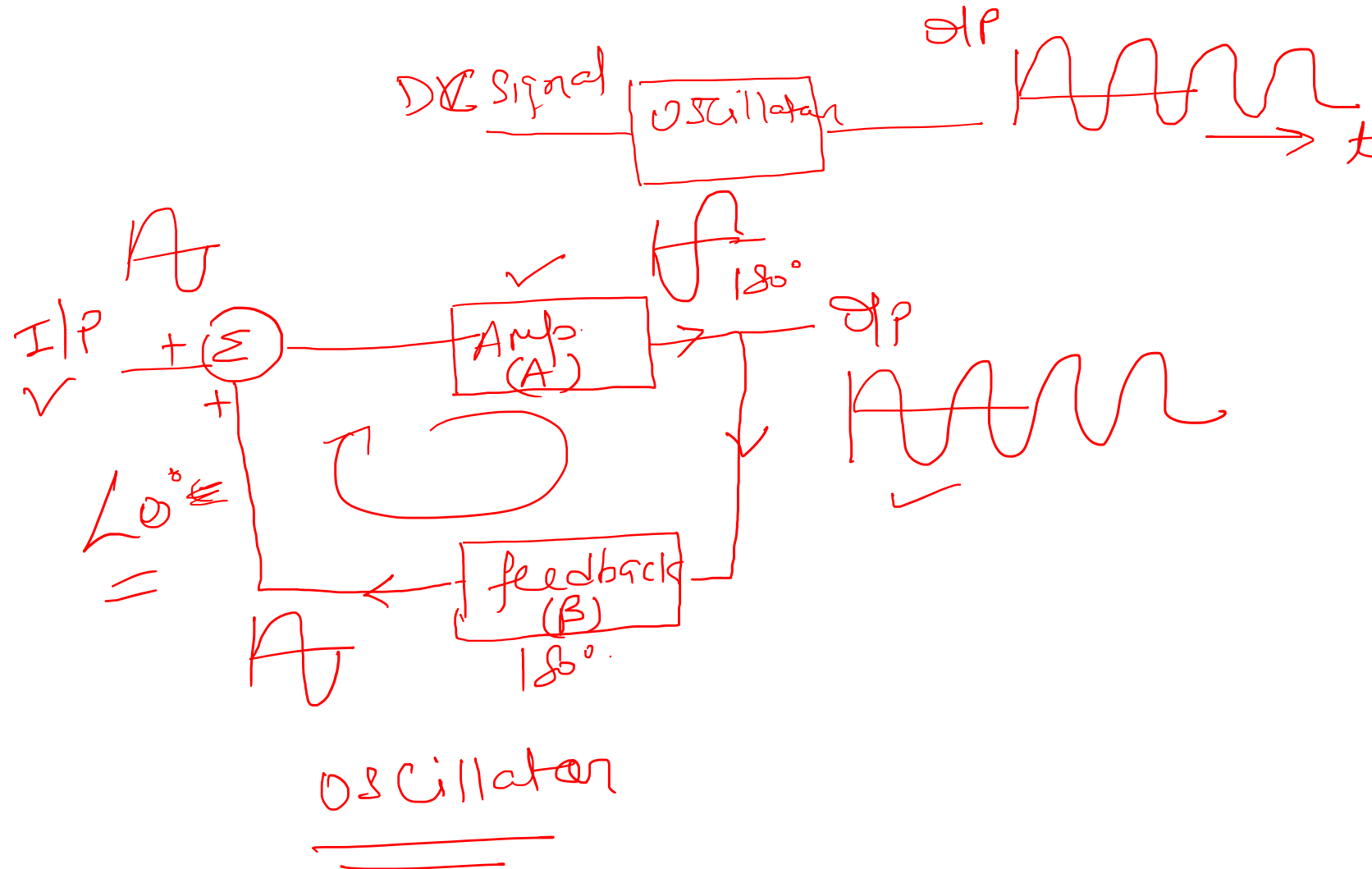The Oscillator is an amplifier with positive feedback, which accepts the DC voltage and generates the periodic time varying waveform of desired frequency.



Mathematical Analysis


β = feedback fraction

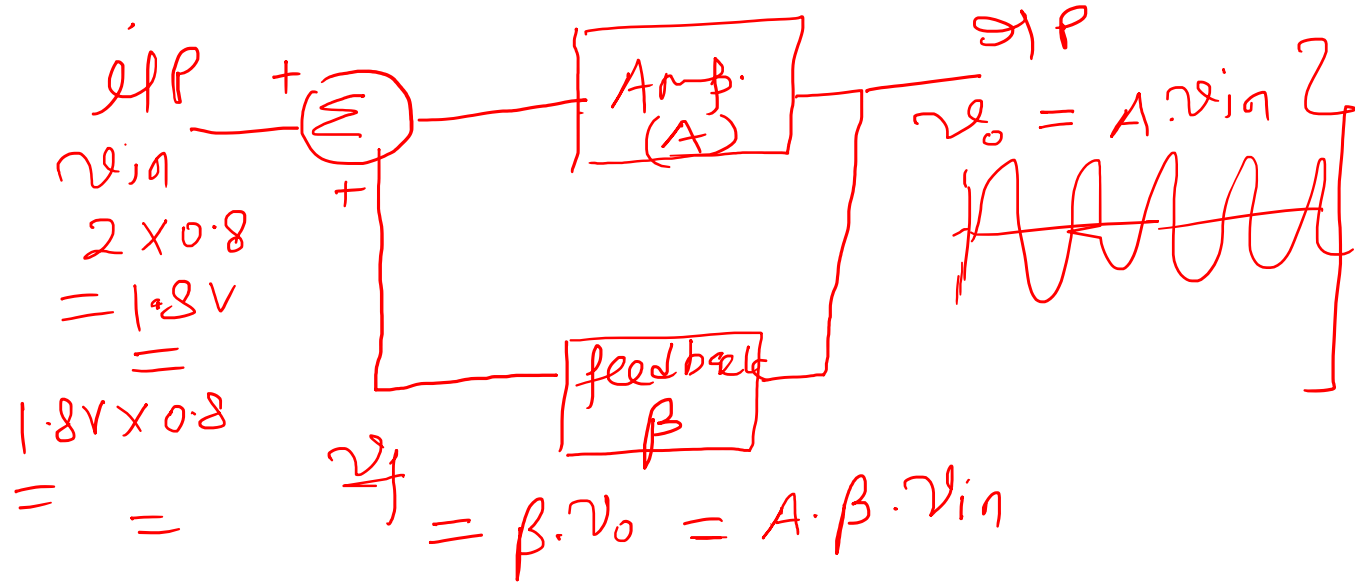


$$v_f = A \cdot \beta \cdot v_{in} \rightarrow \textcircled{1} \quad \left. \begin{array}{l} v_f = v_{in} \\ A \cdot \beta = \text{loop gain} \end{array} \right\} \boxed{A \beta = 1}$$


Barkhausen Criteria:
 $A \cdot \beta = 1$

Case 1: $A \cdot \beta < 1 \Rightarrow \beta < 1$
 $\beta = 0.8$
 $v_{in} = 2$

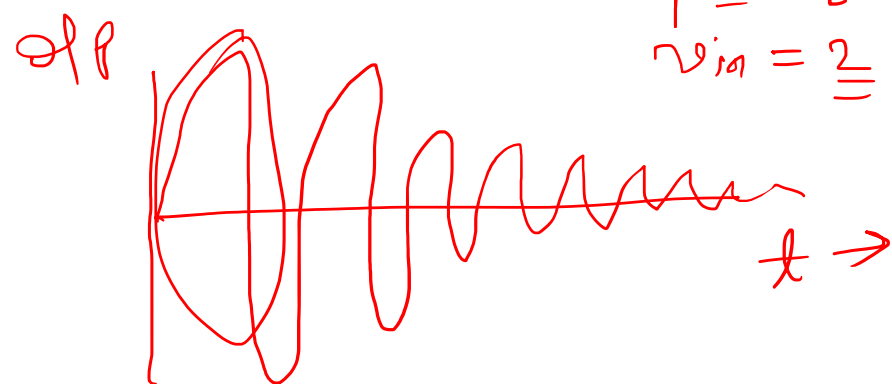

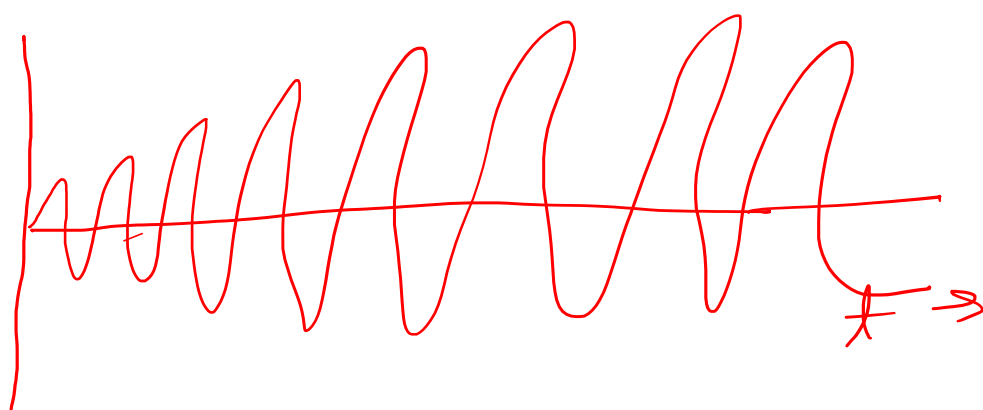Case 2: $A \cdot \beta > 1 \Rightarrow \beta > 1$ = 1.2




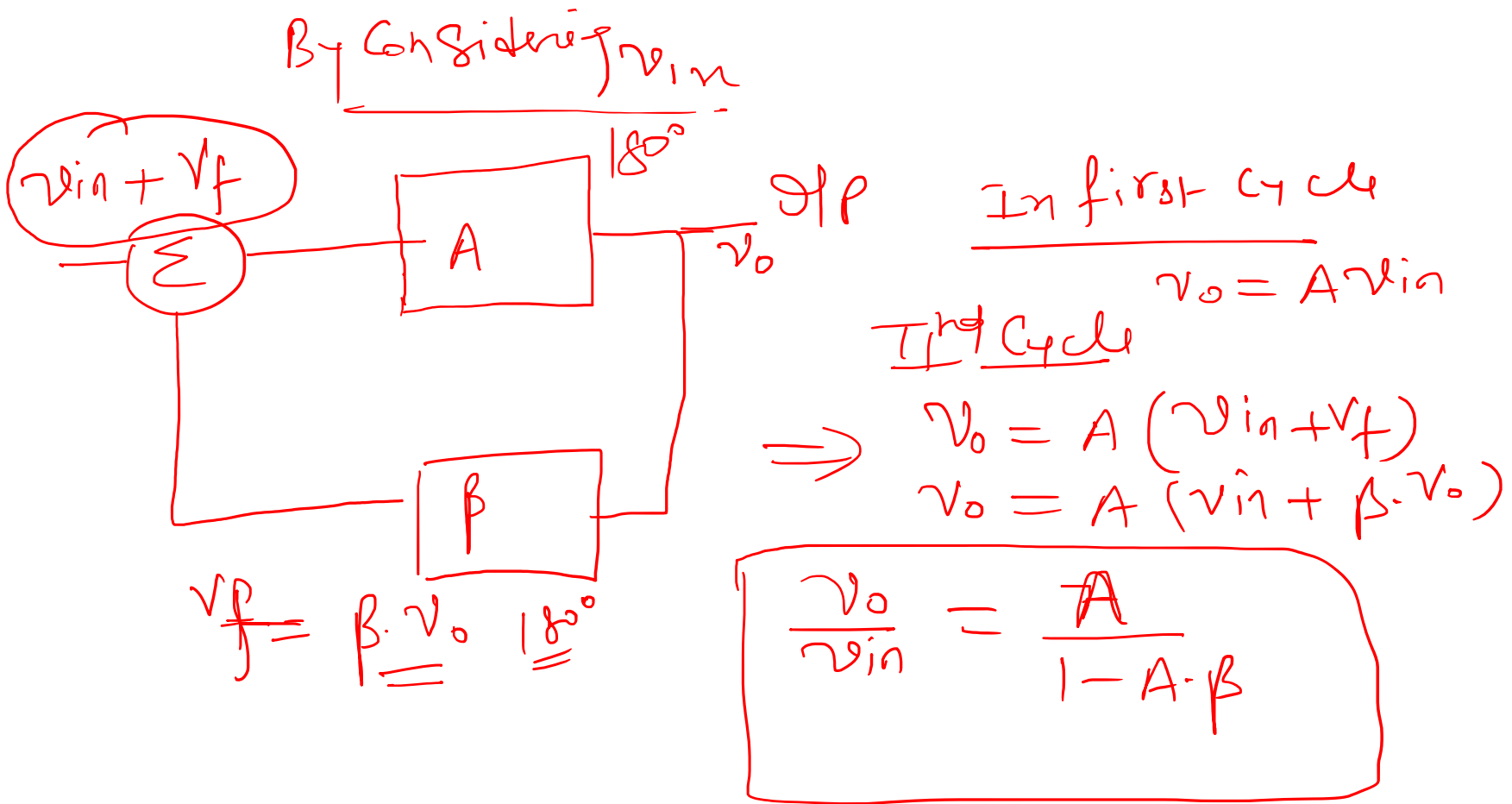

2 $(v_{in} = 0)$

$A \beta = 1$

$\angle \phi = 0^\circ$

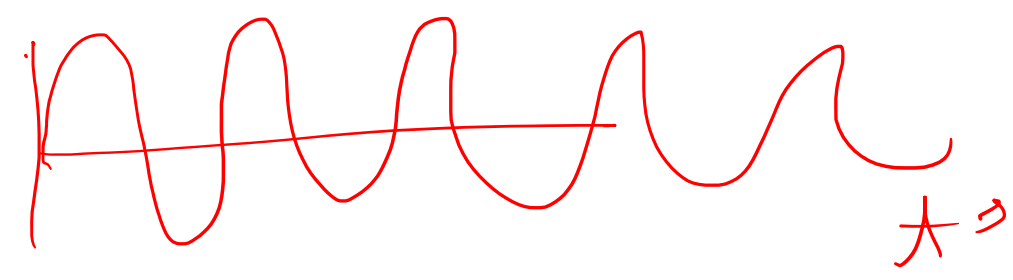

Types of Oscillator

Depending on the type of feedback


- ① ✓ RC Oscillator ✓
- ①① ✓ LC Oscillator ✓
- ①①① ✓ Crystal Oscillator ✓

Depending on the arrangement of R, L and C components:



- RC Phase shift Oscillator ✓
- Colpitts Oscillator ✓
- Hartley Oscillator ✓

Depending on the output of Oscillator

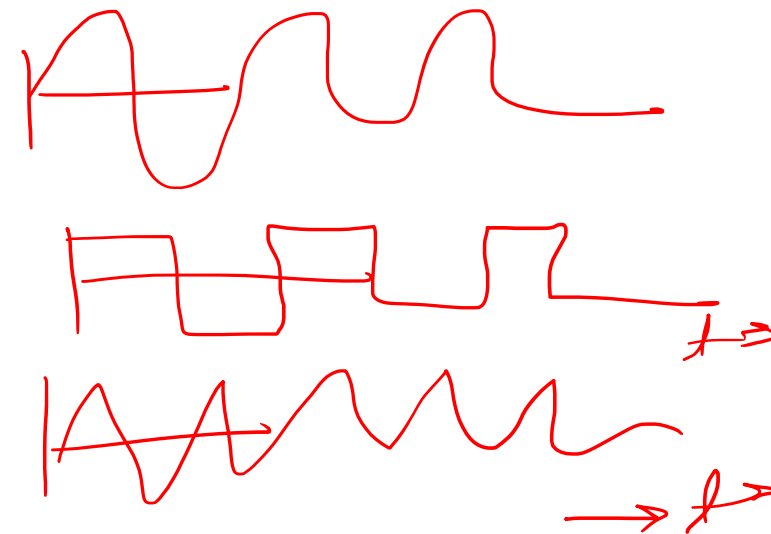
- Harmonic Oscillator ✓ (Sinusoidal)
- Relaxation Oscillator ✓ (Non Sinusoidal)



RC Phase shift Oscillator

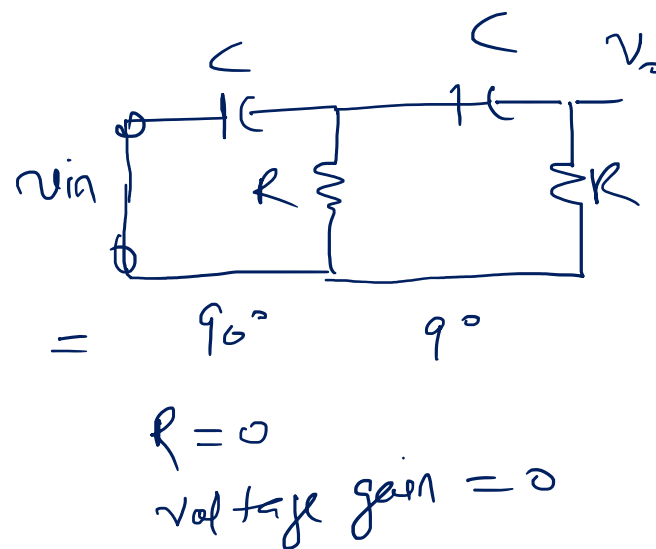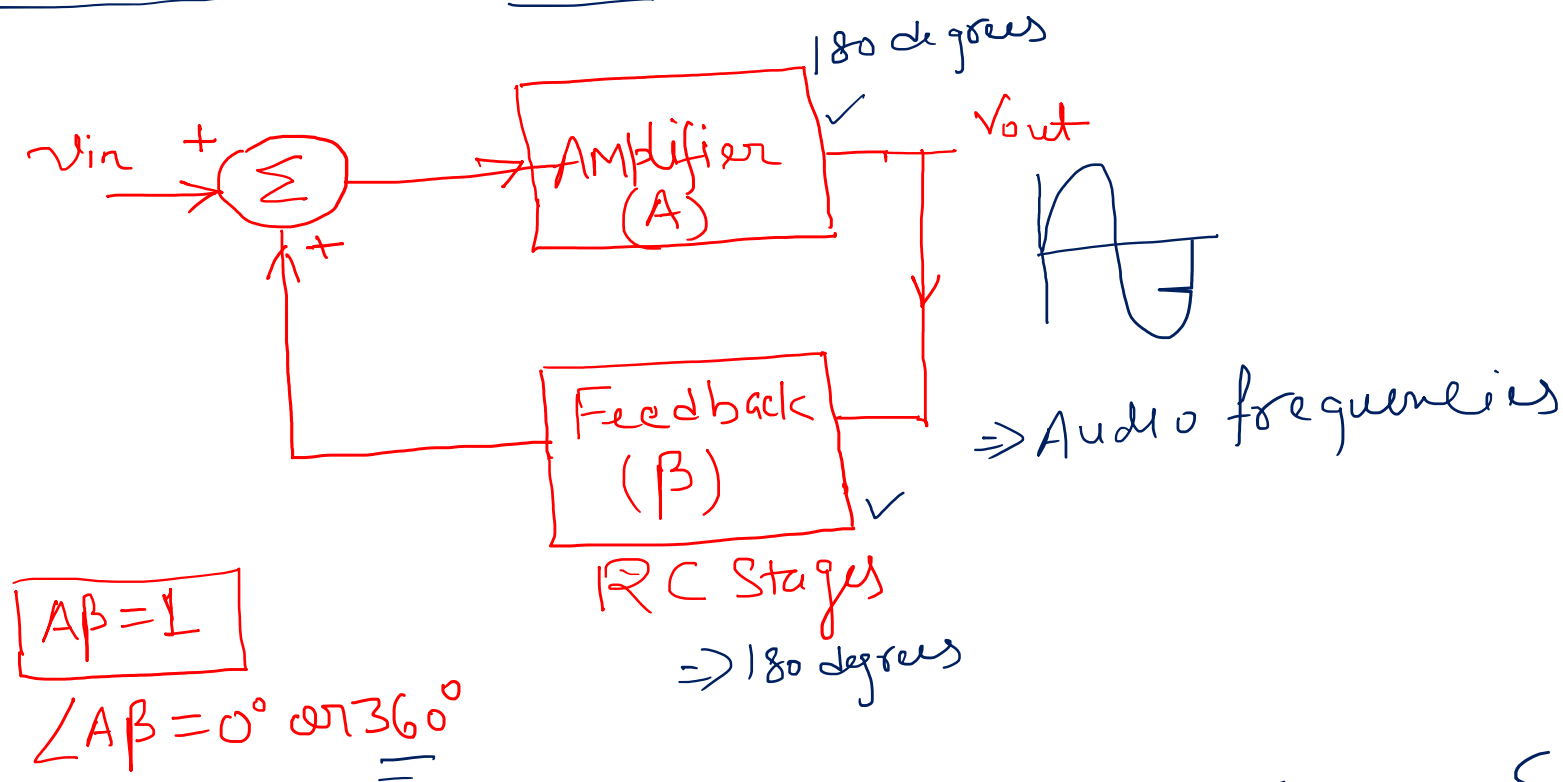

RC Stage

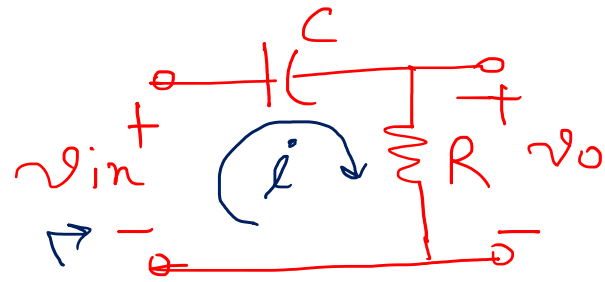

Transfer function ($\frac{v_o}{v_{in}}$)

$$i = \frac{v_{in}}{\frac{1}{j\omega C} + R}$$

$$v_o = i \cdot R = \frac{v_{in}}{R + \frac{1}{j\omega C}} \cdot R \Rightarrow \boxed{\frac{v_o}{v_{in}} = \frac{R}{R + \frac{1}{j\omega C}}}$$


$$\boxed{\frac{v_o}{v_{in}} = \frac{1}{1 + 1/j\omega CR}} \rightarrow \textcircled{1}, \text{ phase shift } \angle A \cdot \beta \text{ or } \angle \phi$$

$$\boxed{\angle \phi = 0 - \tan^{-1}\left(-\frac{1}{\omega CR}\right) = \tan^{-1}\left(\frac{1}{\omega CR}\right)}$$


$$\angle \phi = \tan^{-1}\left(\frac{x_C}{R}\right) \rightarrow \textcircled{2}$$

$$\left. \begin{array}{l} \text{if } x_C \Rightarrow 0, \angle \phi \cong 0 \\ R \Rightarrow 0, \angle \phi \cong 90^\circ \end{array} \right\}$$

CasCade Stages \rightarrow RC network

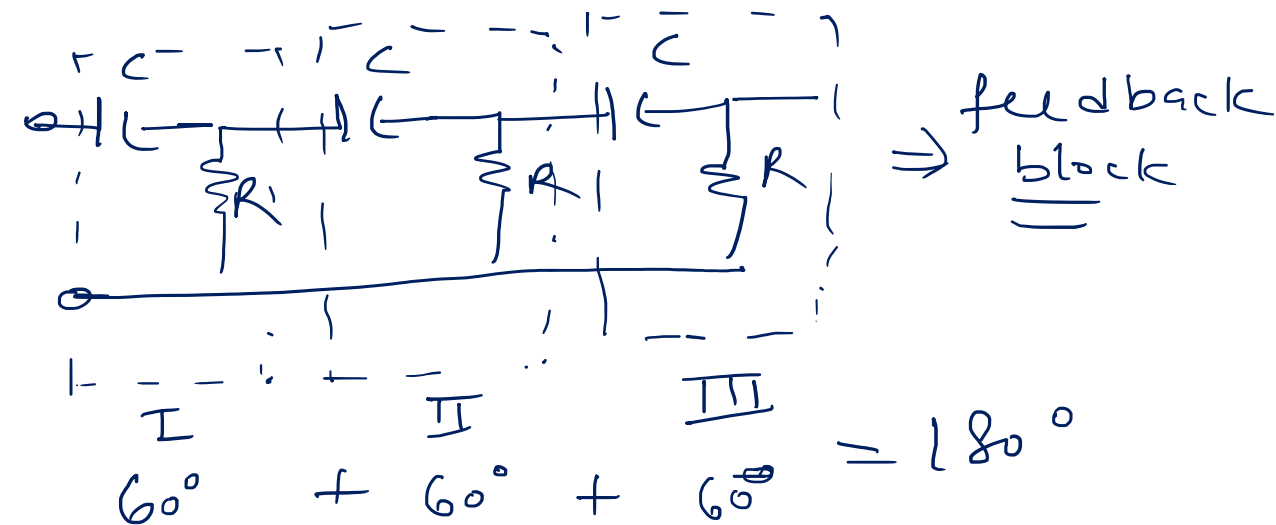

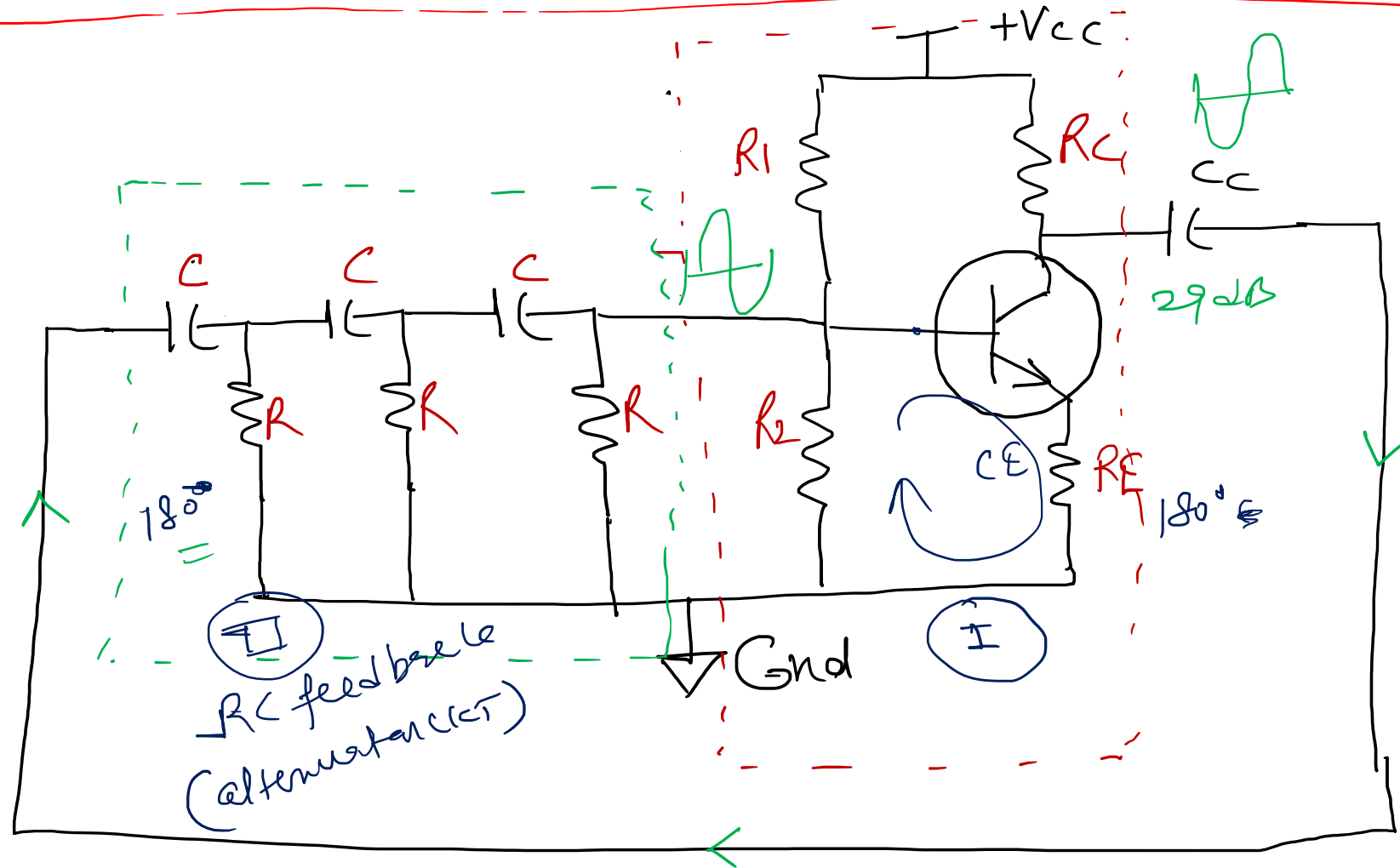Circuit level implementation of RC phase shift oscillator




$$A \cdot \beta = 1$$

$$\left\{ \begin{array}{l} \beta = -\frac{1}{29} \text{ dB} \\ A = 29 \text{ dB} \end{array} \right\} \Rightarrow A \cdot \beta = 1$$

$$f = \frac{1}{2\pi RC \sqrt{2} \cdot N}$$

$N = \text{No. of stages \& RC network}$

Mathematical Analysis

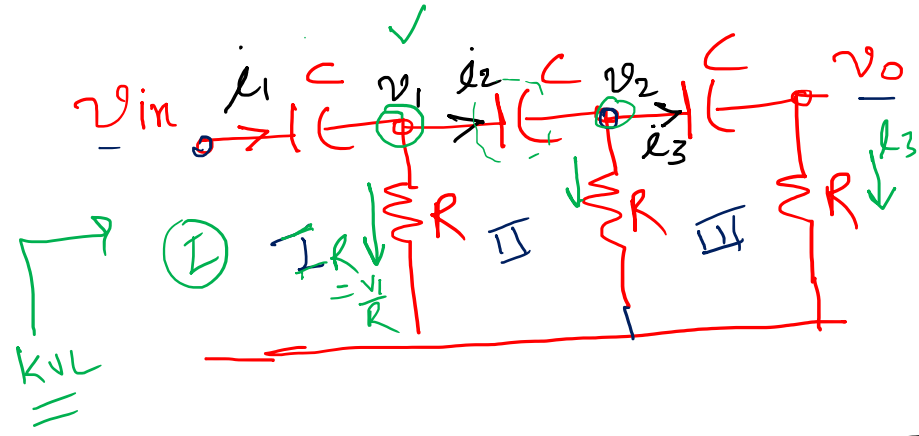

feedback ckt

At node v_2

$$v_2 = \frac{i_3}{j\omega C} + v_o \rightarrow (1), i_3 = \frac{v_o}{R}$$

$$v_2 = \frac{v_o}{j\omega RC} + v_o$$

$$v_2 = v_o \left[1 + \frac{1}{j\omega RC} \right] \rightarrow (2)$$

By applying KCL at node v_2

$$i_2 = i_3 + \frac{v_2}{R} \rightarrow (3)$$

from eqn (2)

$$i_2 = \frac{v_o}{R} + \frac{v_o}{R} \left[1 + \frac{1}{j\omega RC} \right]$$

$$i_2 = \frac{v_o}{R} \left[2 + \frac{1}{j\omega RC} \right] \rightarrow (4)$$

at node v_1

$$v_1 = v_2 + \frac{i_2}{j\omega C} \rightarrow (5)$$

from eqn (2) & (4)

$$v_1 = v_o \left[1 + \frac{1}{j\omega RC} \right] + \frac{v_o}{j\omega RC} \left[2 + \frac{1}{j\omega RC} \right] \rightarrow (6)$$

$$v_1 = v_o \left[1 + \frac{3}{j\omega RC} - \frac{1}{\omega^2 R^2 C^2} \right] \rightarrow (7)$$

Applying KCL at v_1

$$i_1 = i_2 + \frac{v_1}{R} \rightarrow (8)$$

from eqn (4) & (7)

$$i_1 = \frac{v_o}{R} \left[2 + \frac{1}{j\omega RC} \right] + \frac{v_o}{R} \left[1 + \frac{3}{j\omega RC} - \frac{1}{\omega^2 R^2 C^2} \right] \rightarrow (9)$$

Finally

$$v_{in} = v_1 + \frac{i_1}{j\omega C}$$

from eqn (7) & (9)

$$v_{in} = v_o \left[\underbrace{1 - \frac{5}{\omega^2 R^2 C^2}}_{\text{Real}} + \underbrace{\frac{6}{j\omega RC} - \frac{1}{j\omega^3 R^3 C^3}}_{\text{Imag.}} \right] \rightarrow (10)$$

Imag.

$$\frac{6}{j\omega RC} - \frac{1}{j\omega^3 R^3 C^3} = 0$$

$$\omega^2 R^2 C^2 = \frac{1}{6}$$

$$\omega = \frac{1}{\sqrt{6} RC}$$

$$\omega = 2\pi f$$

$$f = \frac{1}{2\pi RC\sqrt{6}} \rightarrow (10)$$

for N RC stages

$$f_N = \frac{1}{2\pi RC\sqrt{2 \cdot N}} \rightarrow (11)$$

$N = \text{No. of RC stages}$



Gain of the feedback ckt

Real term from Eqn (11)

$$V_{in} = V_o \left\{ 1 - \frac{5}{\omega^2 R^2 C^2} \right\} \rightarrow (12)$$

$$\Rightarrow V_{in} = V_o \left\{ 1 - \frac{5}{\frac{1}{6R^2C^2} \times R^2C^2} \right\}, \quad \omega = \frac{1}{RC\sqrt{6}}$$

for three stages of RC network

$$V_{in} = V_o \{1 - 30\}$$

$$\boxed{\frac{V_o}{V_{in}} = -\frac{1}{29}} \rightarrow (13)$$


"-ve" Sign $\Rightarrow 180^\circ$ phase shift

\Rightarrow Attenuator ckt = feedback RC ckt

Close loop gain (A.f) = 1



Colpitt's Oscillator


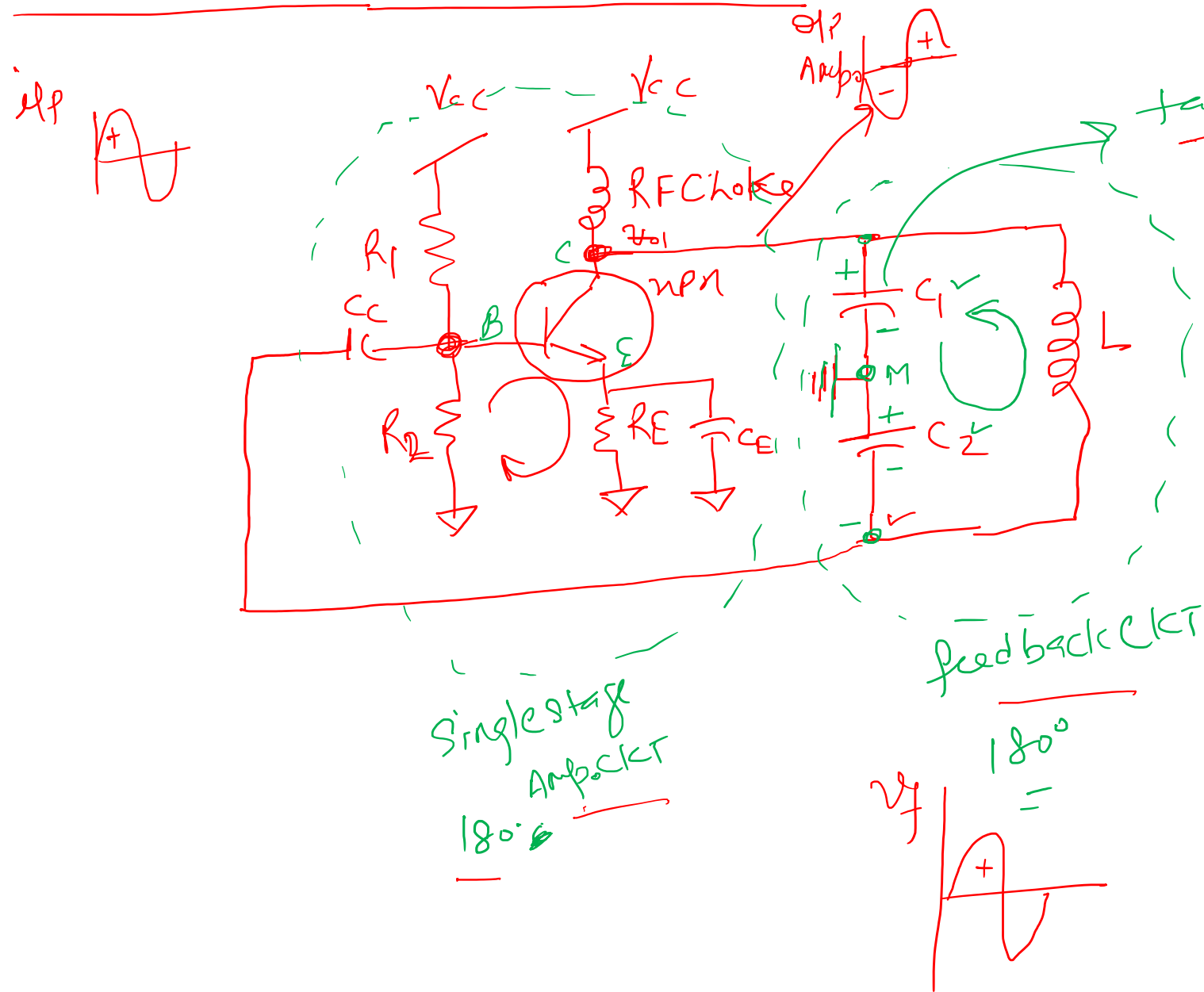


tapped Cap. Coupl.


$$f = \frac{1}{2\pi\sqrt{L \cdot C_T}}$$

$$\Rightarrow C_T = \frac{C_1 \cdot C_2}{C_1 + C_2}$$

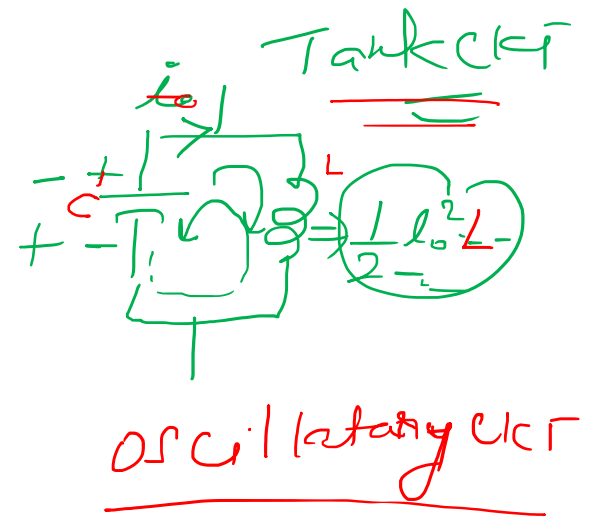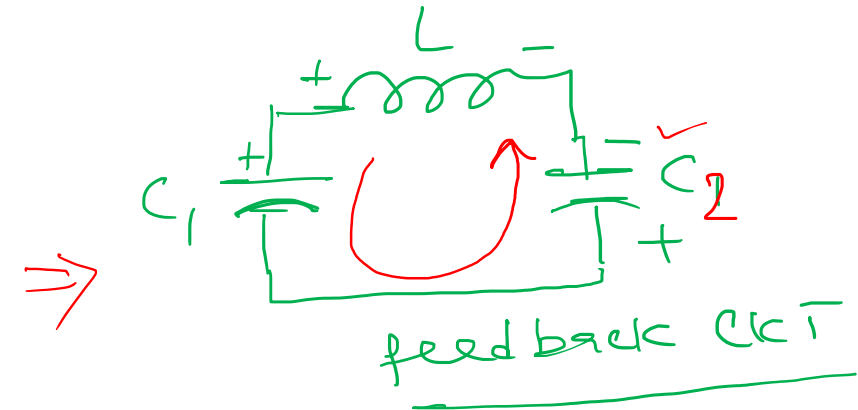feedback $C_1 \rightarrow C_2 \rightarrow L$



⇒ Hartley Oscillator

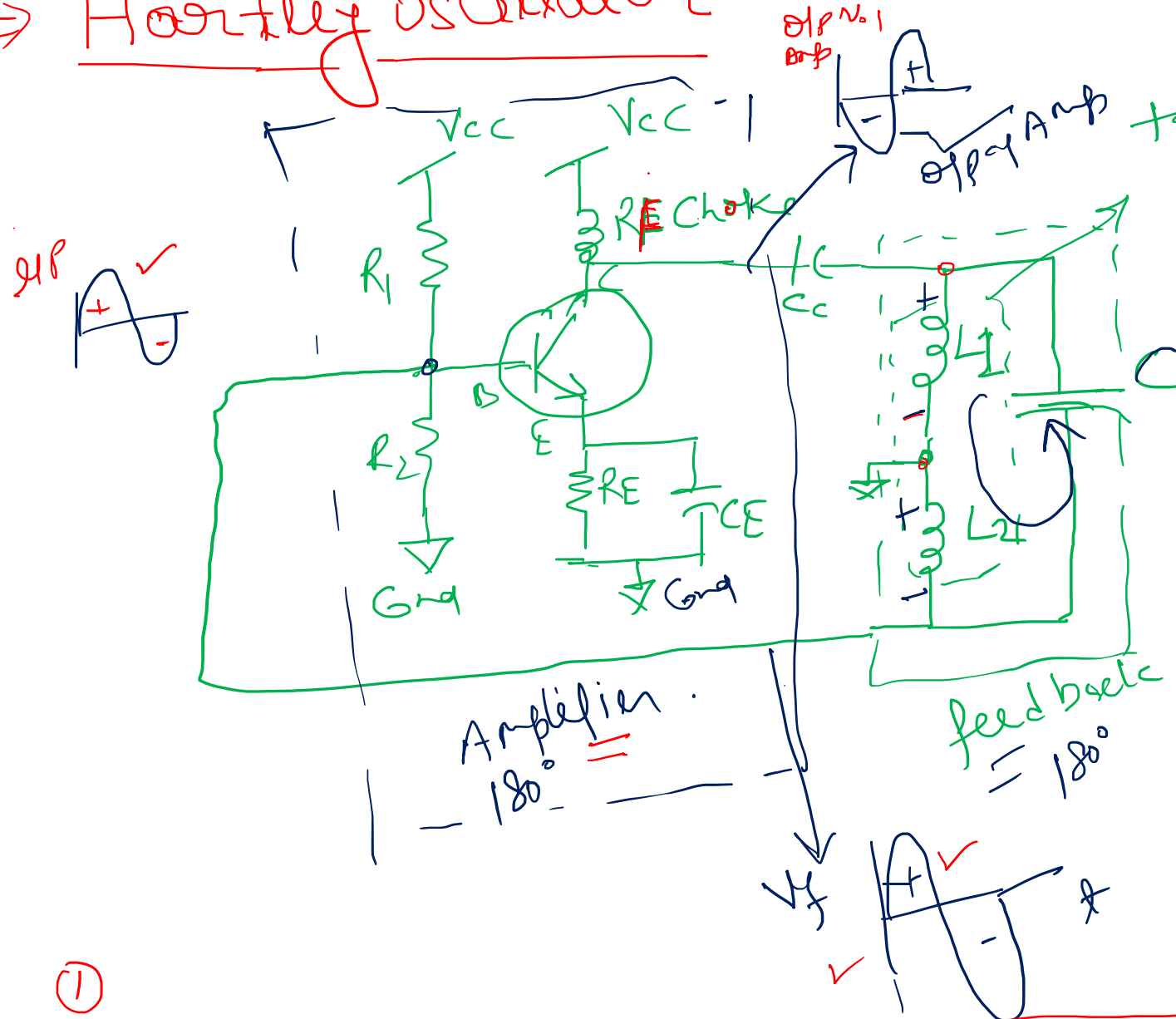

$$A \cdot \beta = 1$$

→ feedback fraction
→ open loop gain

$$f = \frac{1}{2\pi C \sqrt{L_T}}$$


$$L_T = L_1 + L_2 + 2M$$

M = mutual inductance b/w L1 & L2

$$L_1 \rightarrow L_2 \rightarrow C$$

direction of feedback path.

CLK op h

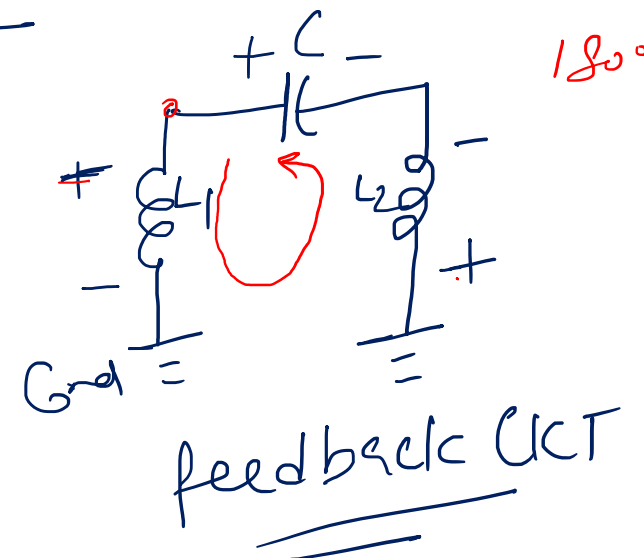

feedback Ckt

$$A \cdot \beta = 1 \Rightarrow \text{Barkhausen criterion}$$

$$f = \frac{1}{2\pi \sqrt{C \cdot L_T}}$$



Thank You

