

Analog and Digital Systems (UEE505)

Lecture # 14 Multivibrators




THAPAR INSTITUTE
OF ENGINEERING & TECHNOLOGY
(Deemed to be University)

Deptt. Of Electrical & Instrumentation Engineering
Thapar Institute of Engineering & Technology Patiala, India

Multivibrators

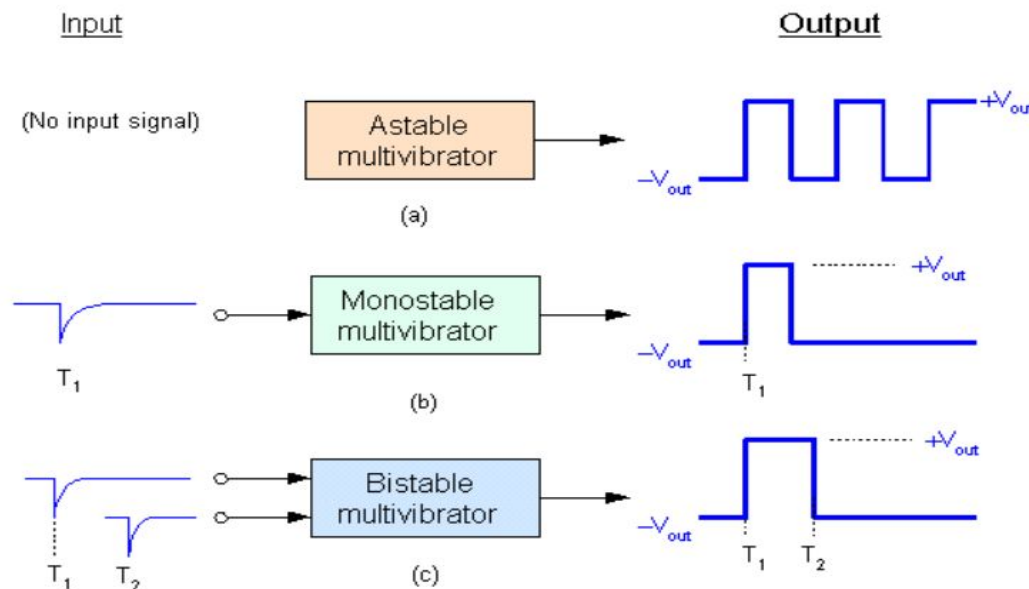
- Non sinusoidal signal generators.
- Clock pulses are generally continuous square or rectangular shaped waveform that is produced by a single pulse generator circuit such as a **Multivibrator**.
- A *Multivibrator* circuit oscillates between a “HIGH” state and a “LOW” state producing a continuous output.
- **Types:**



Multivibrators

- In the **Multivibrator** circuits, the op-amp works as an analogue **comparator**.
- An op-amp comparator compares the voltages on its two inputs and gives a positive or negative output depending on whether the input is greater or less than **some reference value, V_{REF}** .

Bistable Multivibrator

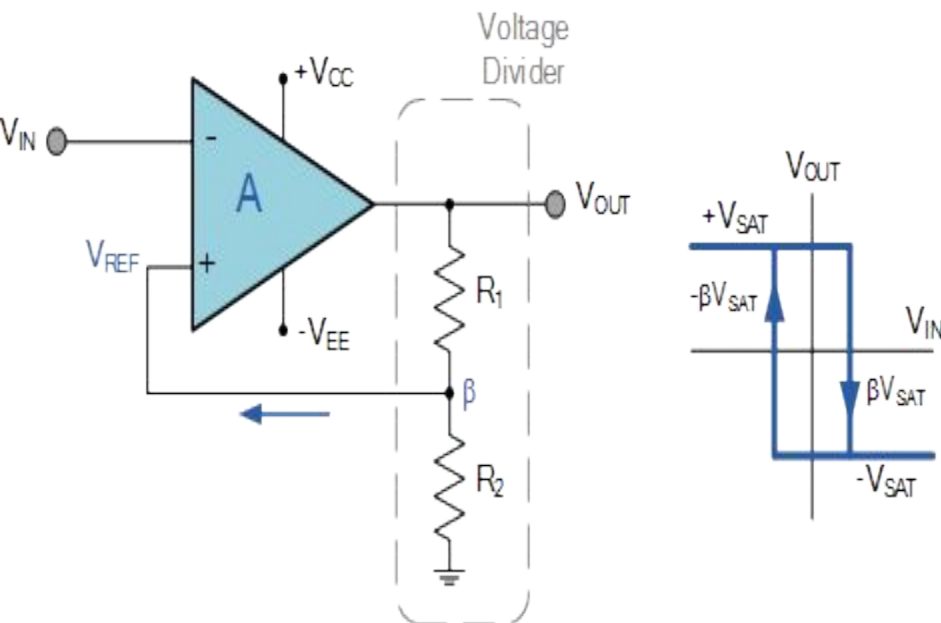

$$V_{REF} = V_{OUT} \frac{R_2}{R_1 + R_2} = \beta V_{SAT}$$

$$\beta = \frac{R_2}{R_1 + R_2}$$



β is called as feedback fraction.

Therefore, $+V_{REF} = +\beta V_{SAT}$

$$-V_{REF} = -\beta V_{SAT}$$

Where $+V_{SAT}$ is the positive op-amp DC saturation voltage and $-V_{SAT}$ is the negative op-amp DC saturation voltage

Astable Multivibrator

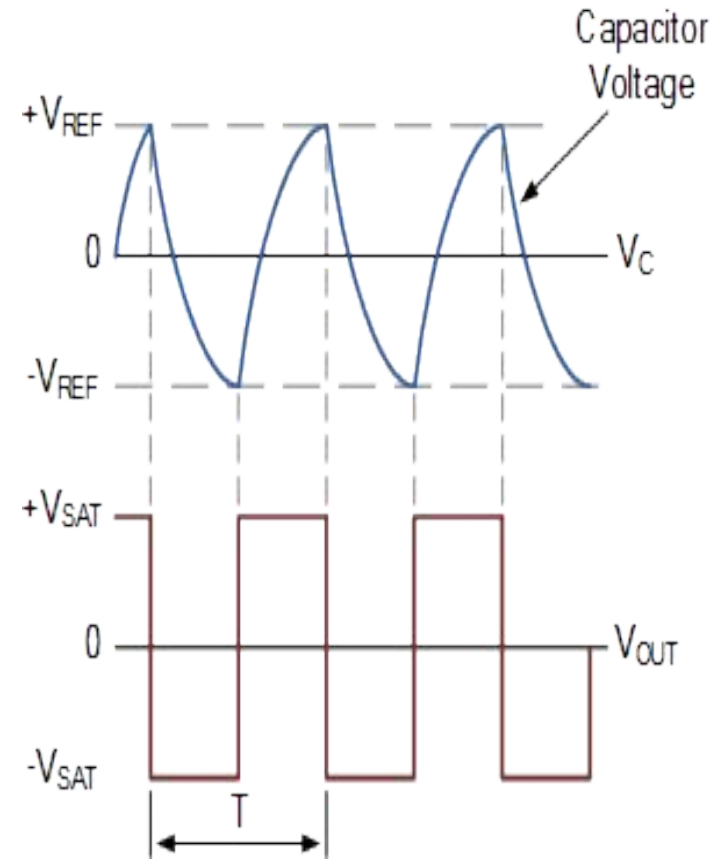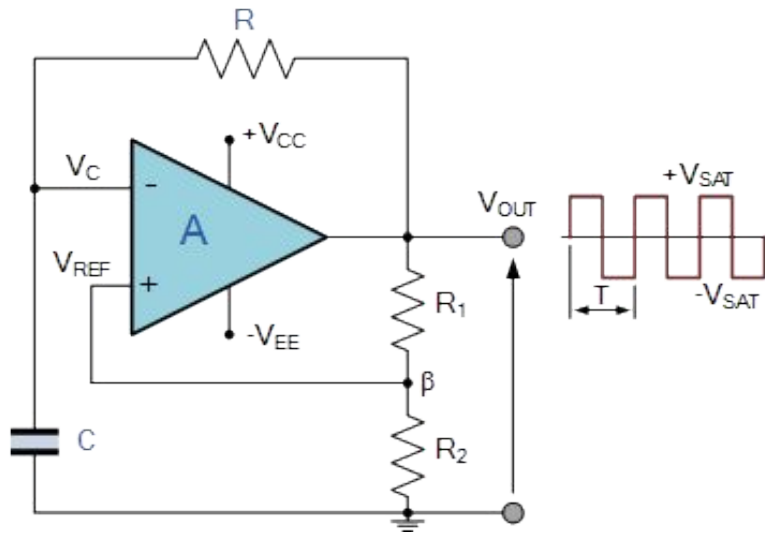

If the positive and negative values of the amplifiers saturation voltage have the same magnitude, then $t_1 = t_2$ and the expression to give the period of oscillation becomes:


$$\beta = \frac{R_2}{R_1 + R_2}$$

$$T = 2RC \times \ln \left(\frac{1 + \beta}{1 - \beta} \right) \quad \therefore f = \frac{1}{T}$$

Derivation for Frequency of Oscillations

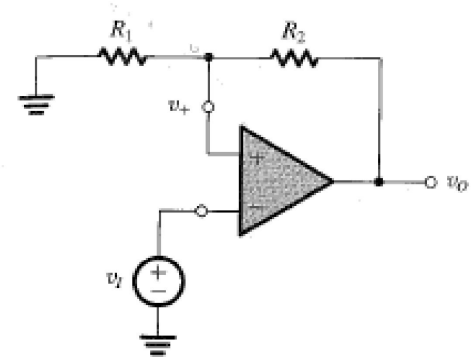Example

The op amp in the bistable circuit shown has output saturation voltages of $\pm 13 \text{ V}$. Design the circuit to obtain threshold voltages of $\pm 5 \text{ V}$.
For $R_1 = 10 \text{ k}\Omega$ find the values of R_2 .



References

❖ For more details, refer to:

- *Boylestad R. L., Electronic Devices and Circuit Theory, Pearson Education*
- *Neamen, Donald A., Electronic Circuit Analysis and Design, McGraw Hill*
- *Sedra A. S. and Smith K. C., Microelectronic Circuits, Oxford University Press*