

Analog and Digital Systems (UEE505)

Lecture # 9

Butterworth filters using op amp -I



THAPAR INSTITUTE
OF ENGINEERING & TECHNOLOGY
(Deemed to be University)

Deptt. Of Electrical & Instrumentation Engineering
Thapar Institute of Engineering & Technology Patiala, India

Filter Introduction

- A filter is a circuit that passes some frequency signals without any attenuation (Reduction in amplitude) or with some amplification and attenuate other frequency depending on the types of the filter.
- Filters can be used to attenuate unwanted signals such as interference or noise or to isolate desired signals from unwanted.
- A common instrumentation filter application is the attenuation of high frequencies to avoid frequency aliasing in the sampled data.

Classification of Filters

- ❖ Classification of filters based on their frequency response and construction:
 - **Analog and Digital Filter** (depending on type of techniques used in the process of analog signals)
 - **Passive and Active filters** (depending on type of elements used in their construction)
 - (According to operating frequency range) **Audio or Radio Frequency Filters**

Filter Classification according to Frequency Response

- i) Low Pass Filter ii) High Pass Filter
- iii) Bandpass Filter iv) Band Stop Filter


- Butterworth, Chebyshev, and Elliptical Filters are some of most widely used practical filters for approximating the ideal response.

□ Key Characteristics:


- Butterworth : Flat passband as well as flat stop band (flat flat filter).
- Chebyshev : Ripple passband and flat stop band.
- Elliptical : Ripple passband as well as Ripple stop band (Provide best stopband response)

Low Pass Filter

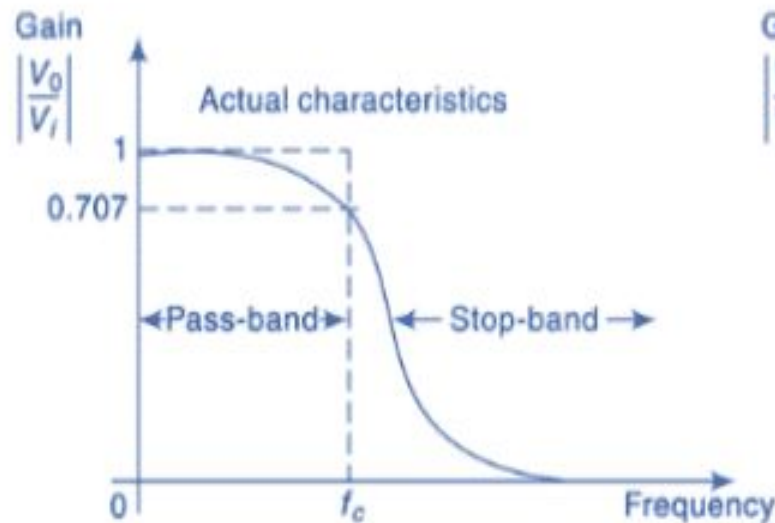- It is a type of Filter which attenuates all the frequencies above the cut-off frequencies.
- It provides a constant output (gain) from zero to cut-off frequency.




(a)

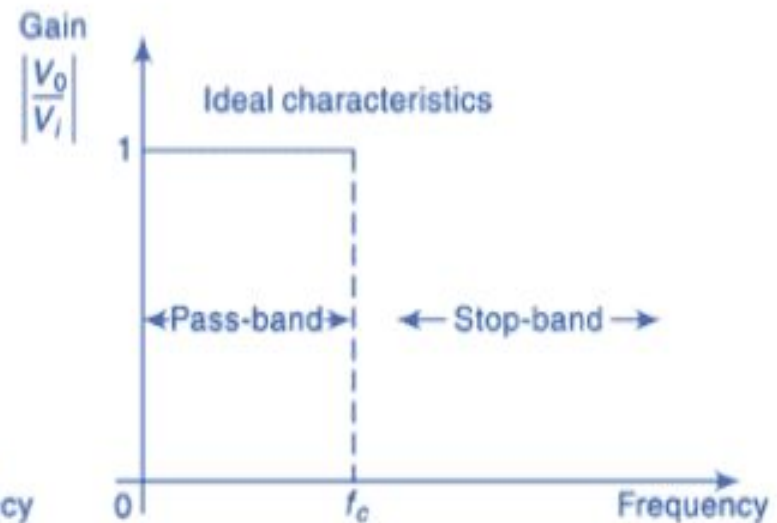


(b)

High Pass Filter

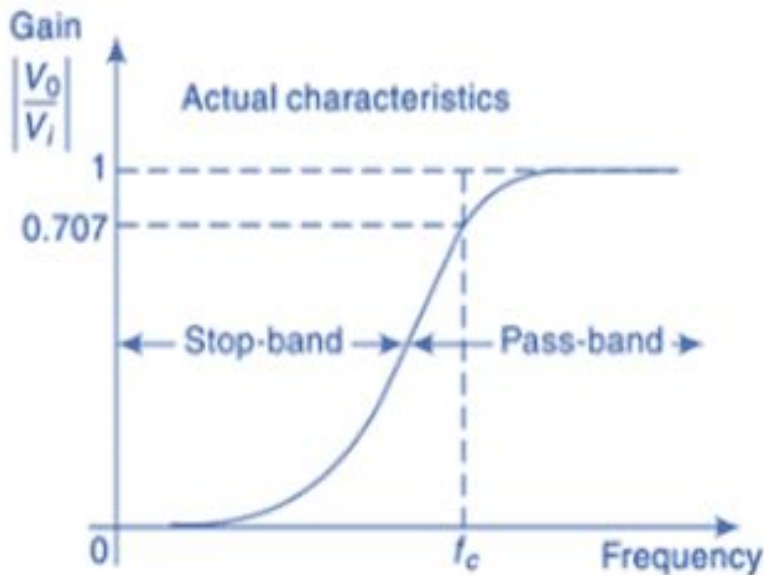- It is a type of Filter which attenuates all the frequencies below the cut-off frequencies.
- It provides a constant output (gain) above the cut-off frequency.




(a)

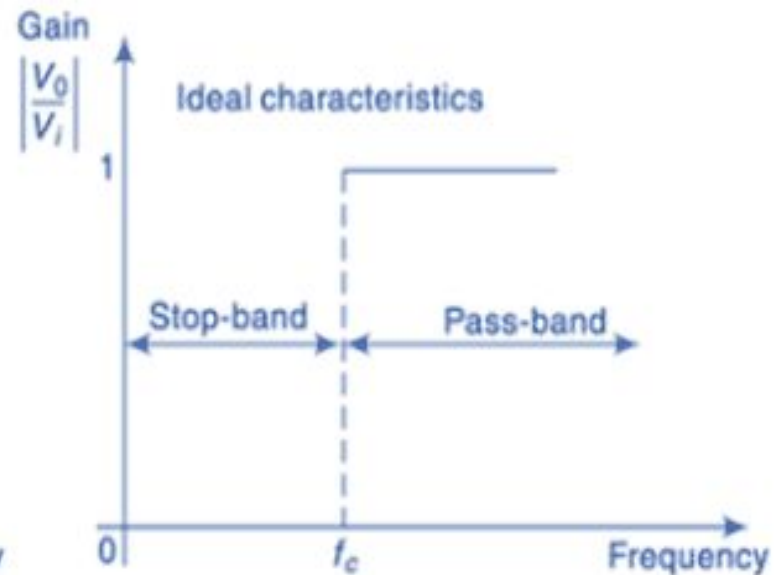

(b)


Bandpass Filter

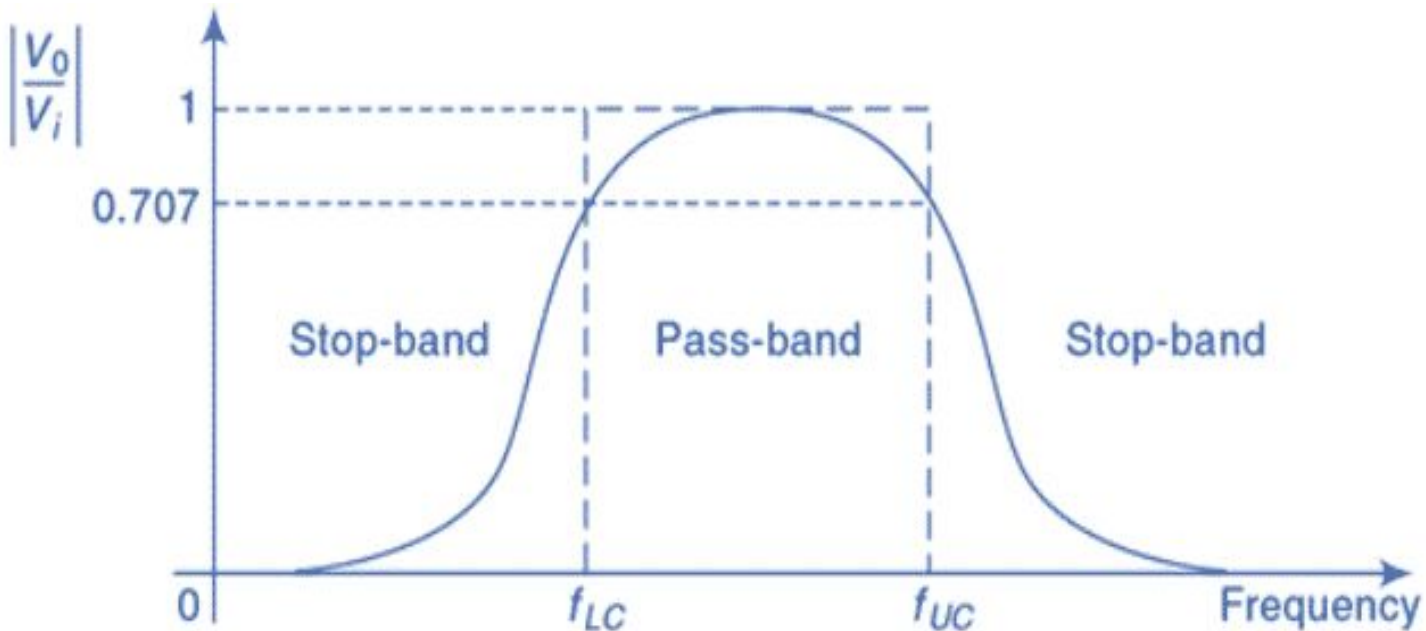- It is a type of filter which allows specific band of frequencies to pass through and all other frequencies outside the band are attenuated.



Band Stop Filters

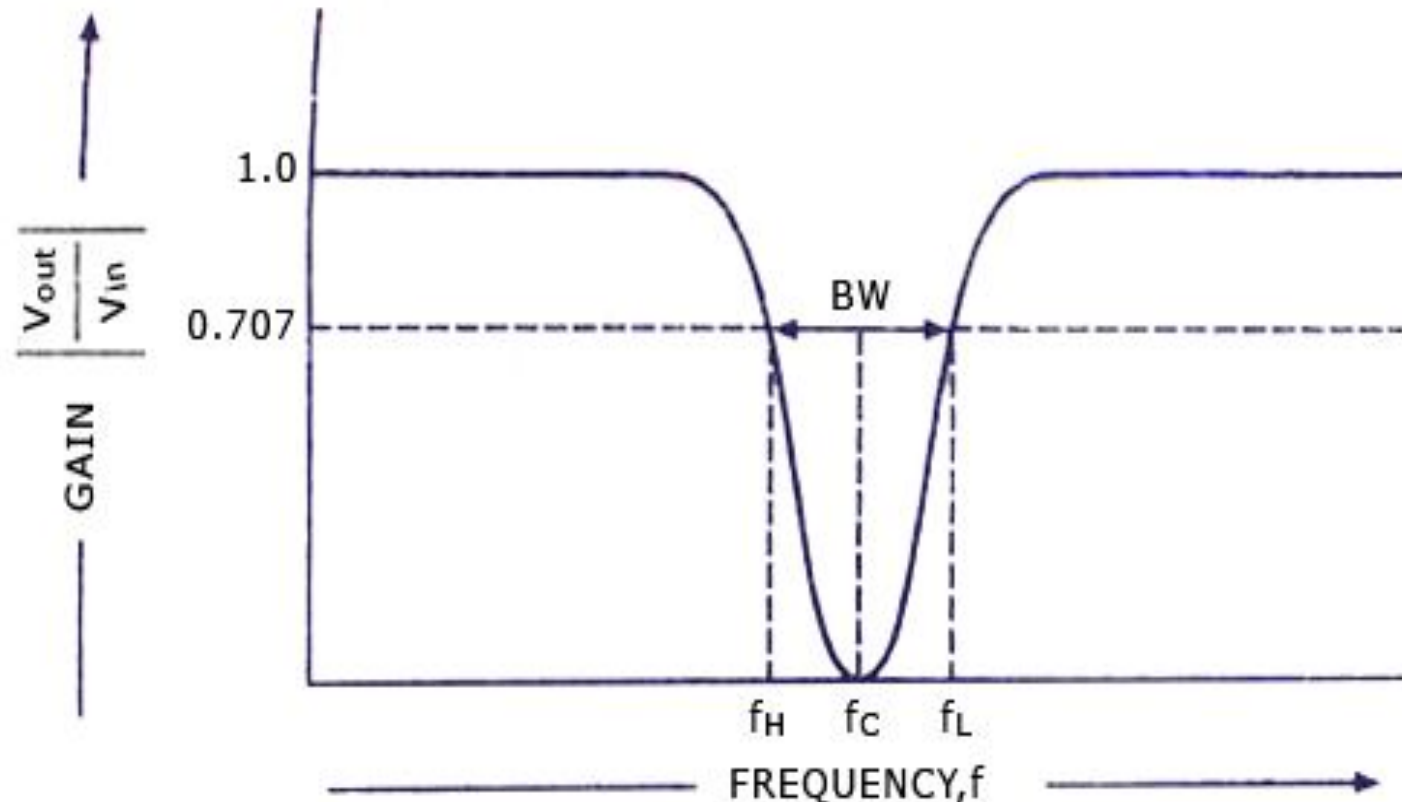- Specific Band of frequencies gets rejected and allows passing of frequencies outside the Band.



Applications of Filters

- Filter Circuits are used to eliminate background Noise
- They are used in Radio tuning to a specific frequency and in signal processing circuits
- Filter Circuits are extensively used in Medical Electronic Systems

Designing of Low Pass Filter

Voltage at non inverting input terminal(voltage across the capacitor) is :

$$V_1 = [-j X_c / (R - j X_c)] V_{in}$$

$$\text{Here, } -j X_c = 1/2\pi f c$$

$$V_1 = V_{in} / (1 + j2\pi f RC)$$

Now the op-amp here used in non inverting configuration, thus

$$V_o = (1 + R_2 / R_1) V_1.$$

$$V_o = (1 + R_F / R_1) [V_{in} / (1 + j2\pi f RC)]$$

$$V_o / V_{in} = A_F / (1 + j (f / f_L))$$

Here,


V_{out} / V_{in} : gain of the filter as a function of frequency

$AF = (1 + R_F / R_1)$: passband gain of the filter

f : frequency of the input signal

$f_L = 1 / 2\pi RC$: cutoff frequency of the filter.

1st order Butterworth LPF

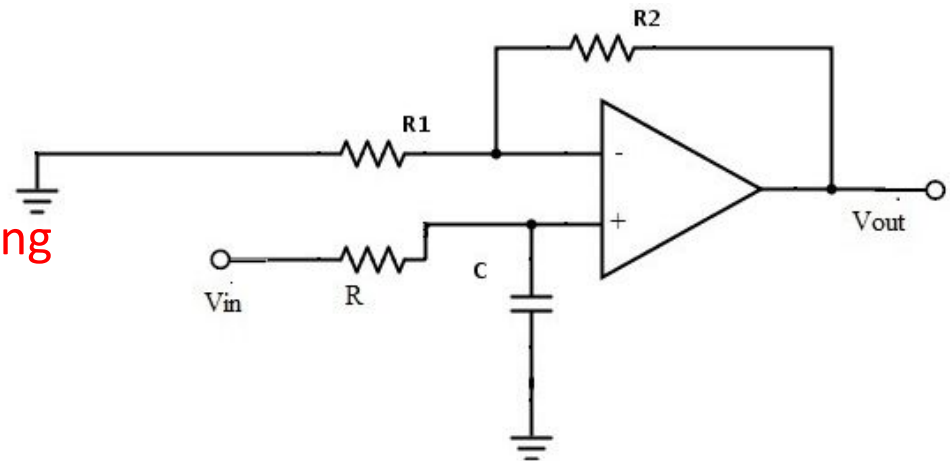

Frequency Response of Low Pass Filter


$$V_o / V_{in} = A_F / (1 + j(f/f_L)) \quad \left| \frac{V_o}{V_{in}} \right| = \frac{A_F}{\sqrt{1 + \left(\frac{f}{f_L}\right)^2}} \text{ and } \theta = -\tan^{-1}\left(\frac{f}{f_L}\right)$$

Now to observe the change in gain magnitude with the change in the frequency of the input signal, consider three cases:

Case1: $f \ll f_L$, $\left| \frac{V_o}{V_{in}} \right| = \frac{A_F}{\sqrt{1 + (0)^2}} = A_F$

Case2: $f = f_L$, $\left| \frac{V_o}{V_{in}} \right| = \frac{A_F}{\sqrt{1 + (1)^2}} = \frac{A_F}{\sqrt{2}} = 0.707 A_F$

Case3: $f > f_L$, $\left| \frac{V_o}{V_{in}} \right| < A_F$

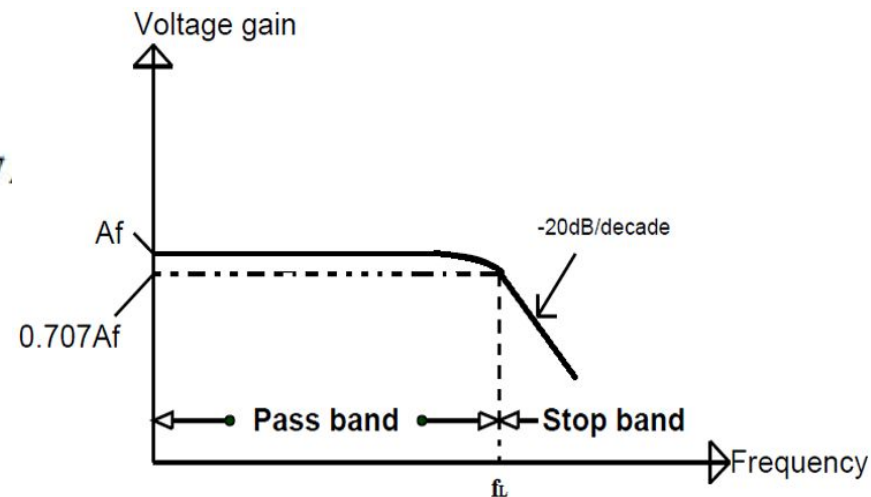

References

- ❖ For more details, refer to:
 - *Boylestad R. L., Electronic Devices and Circuit Theory, Pearson Education*
 - *Op-Amps and Linear Intergrated Circuits , Ramakant A. Gayakwad*
 - *Neamen, Donald A., Electronic Circuit Analysis and Design, McGraw Hill*