
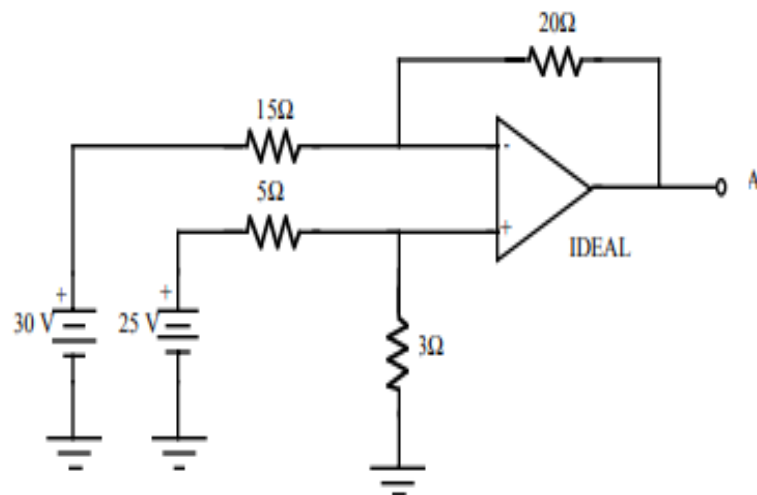


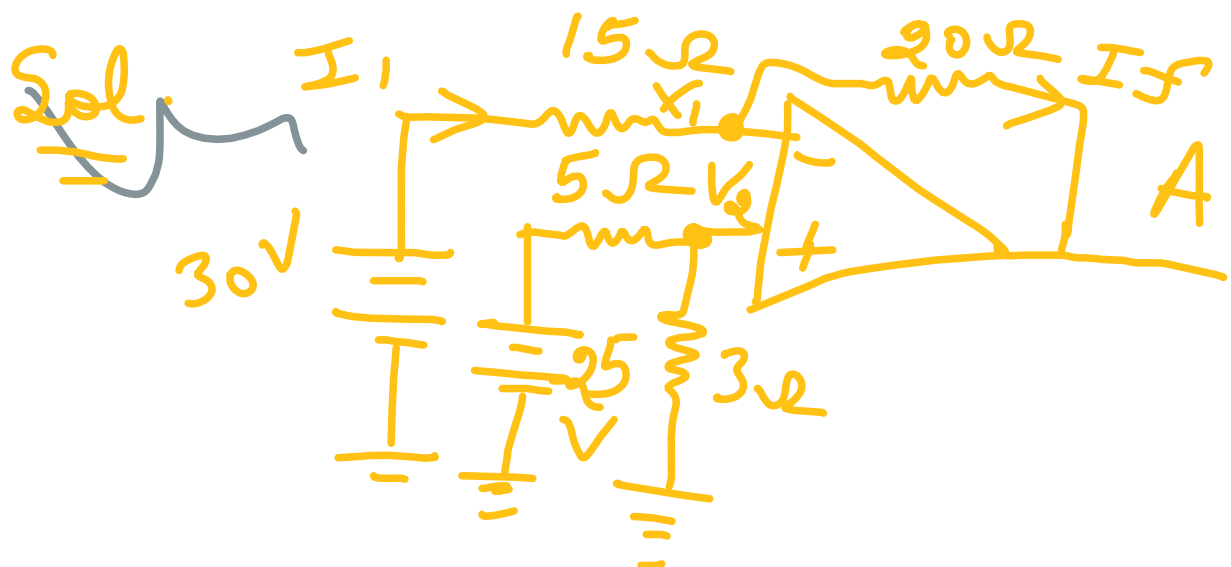Q1. Find the voltage at terminal A in given figure:



Answer : -18.13V



$$V_2 = \frac{25 \times 3}{3+5} = \frac{75}{8} \\ = 9.375V$$

Due to Concept of Virtual ground

$$V_1 = V_2 = 9.375V$$

Now

$$I_1 = I_f \rightarrow \text{feedback Current}$$

$$\therefore \frac{30 - V_1}{3.15} = \frac{V_1 - V_A}{204}$$

$$120 - 4V_1 = 3V_1 - 3V_A$$


$$3V_A = 3V_1 + 4V_1 - 120$$

$$V_A = \frac{7V_1 - 120}{3}$$

$$\therefore V_A = \frac{7 \times 9.375 - 120}{3}$$

$$= -18.125 \text{ Volts}$$

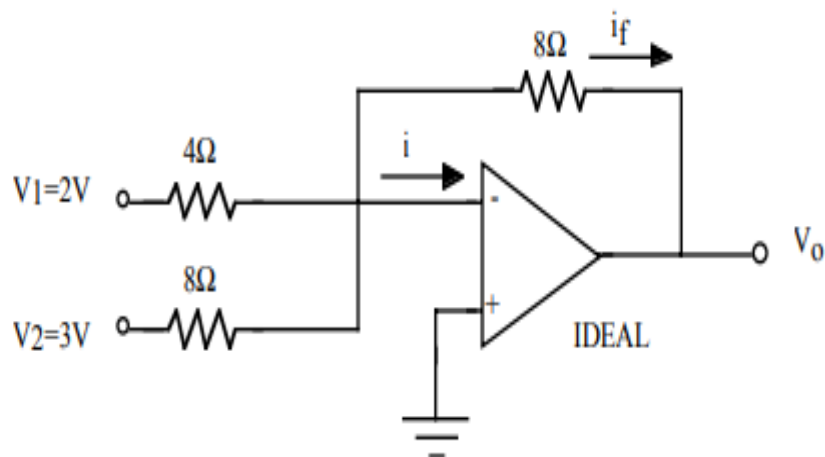
Q2. Find the current i and output voltage in given figure.



$$i_f \text{ } 8\Omega$$

Answer : $i = 0A$, $V_o = -7V$

Sol

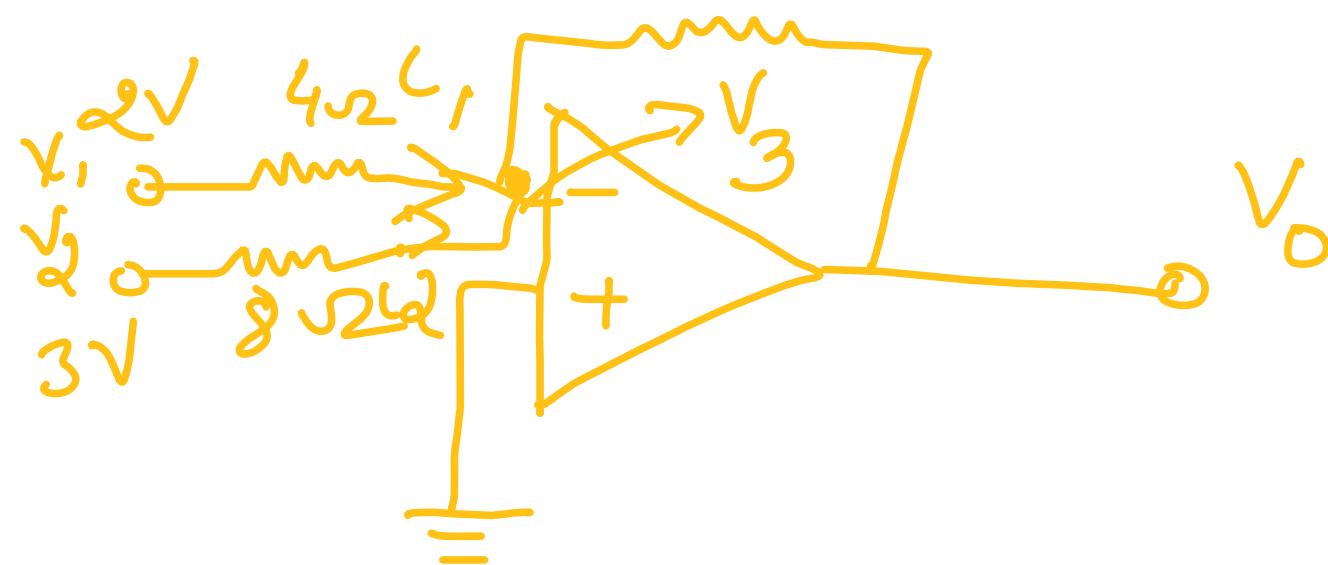

input current is very small $i \approx 0A$

$V_3 = 0$ due to virtual ground

$$i_1 + i_2 = i_f$$


$$\frac{V_1 - V_3}{4} + \frac{V_2 - V_3}{8} = \frac{V_3 - V_0}{8}$$

$$2 - 0 + 3$$

$$\frac{\quad}{4} \quad \frac{-0}{8} = \frac{0 - V_o}{8}$$


Solving the above equation
 $V_o = -7V$

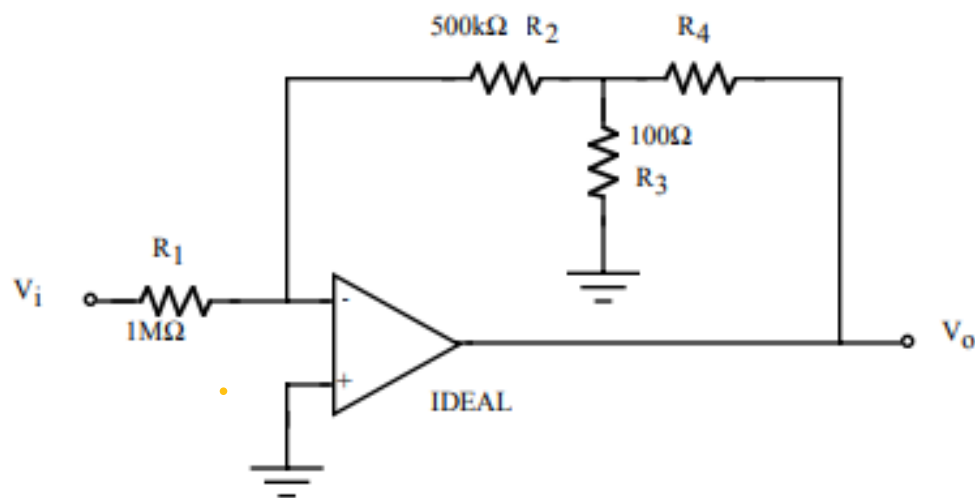Q3. Evaluate the following amplifier circuit to determine the value of resistor R_4 in order to obtain a voltage gain (v_o/v_i) of -120.



Answer : $R_4 = 24 \text{ kohm}$

Sol.

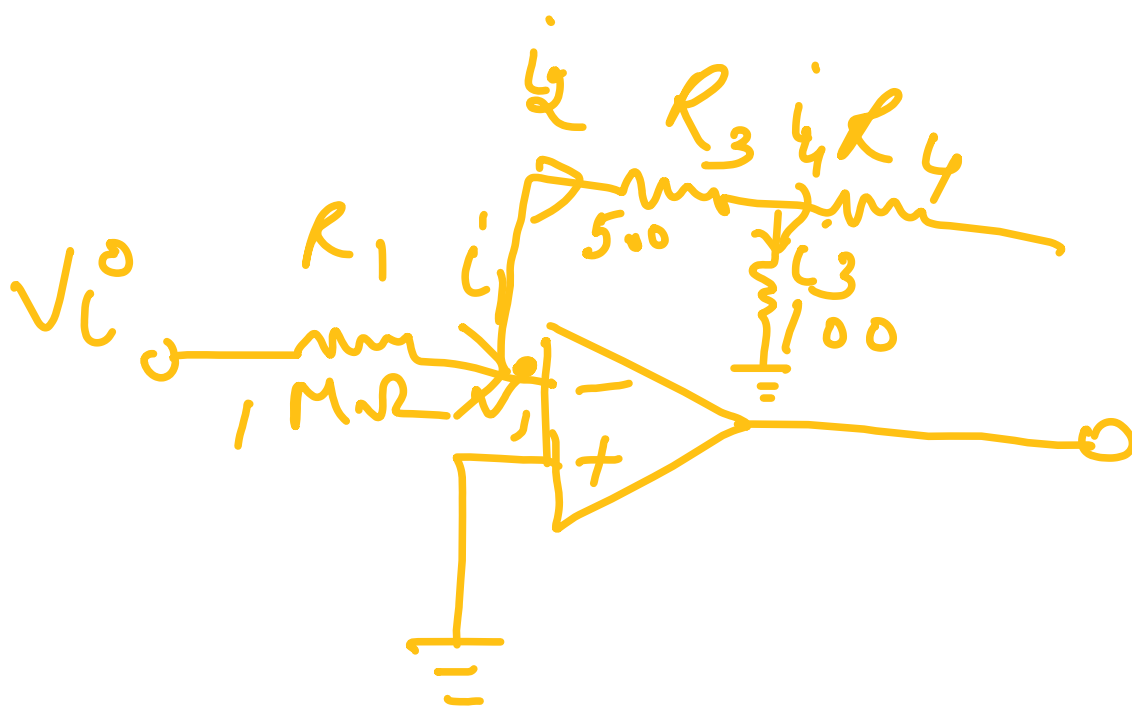

$$i_2 = i_3 + i_4$$

$$i_1 = i_2$$

and $V_1 = 0$ due to virtual ground.

$$\frac{V_i - V_1}{1 \times 10^6} = \frac{V_1 - V_x}{500 \times 10^3} \quad \text{--- (1)}$$

$$i_2 = i_3 + i_4$$

using


$$\frac{V_1 - V_{oc}}{500 \times 10^3} = \frac{V_2 - 0}{1100} + \frac{V_2 - V_o}{R_4} \quad (2)$$

$$\underline{V_o} = -120$$

V_o^c
solve eq (1) + (2)


$$R_4 = 23.9 \text{ k}\Omega$$

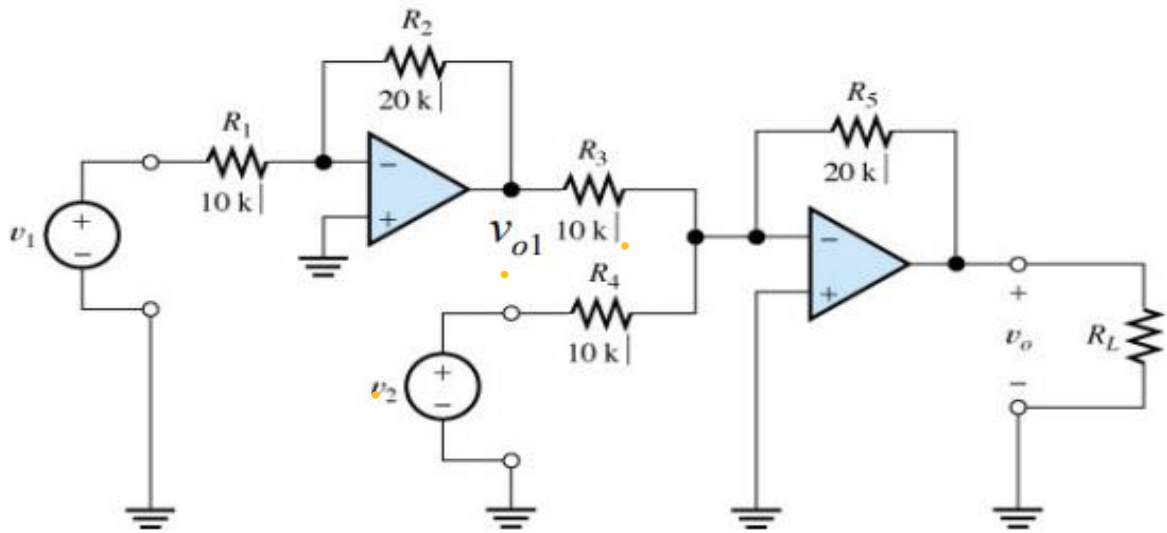- Q4. Find an expression for the output voltage of given circuit.



Answer : $V_o = 4v_1 - 2v_2$

Solution

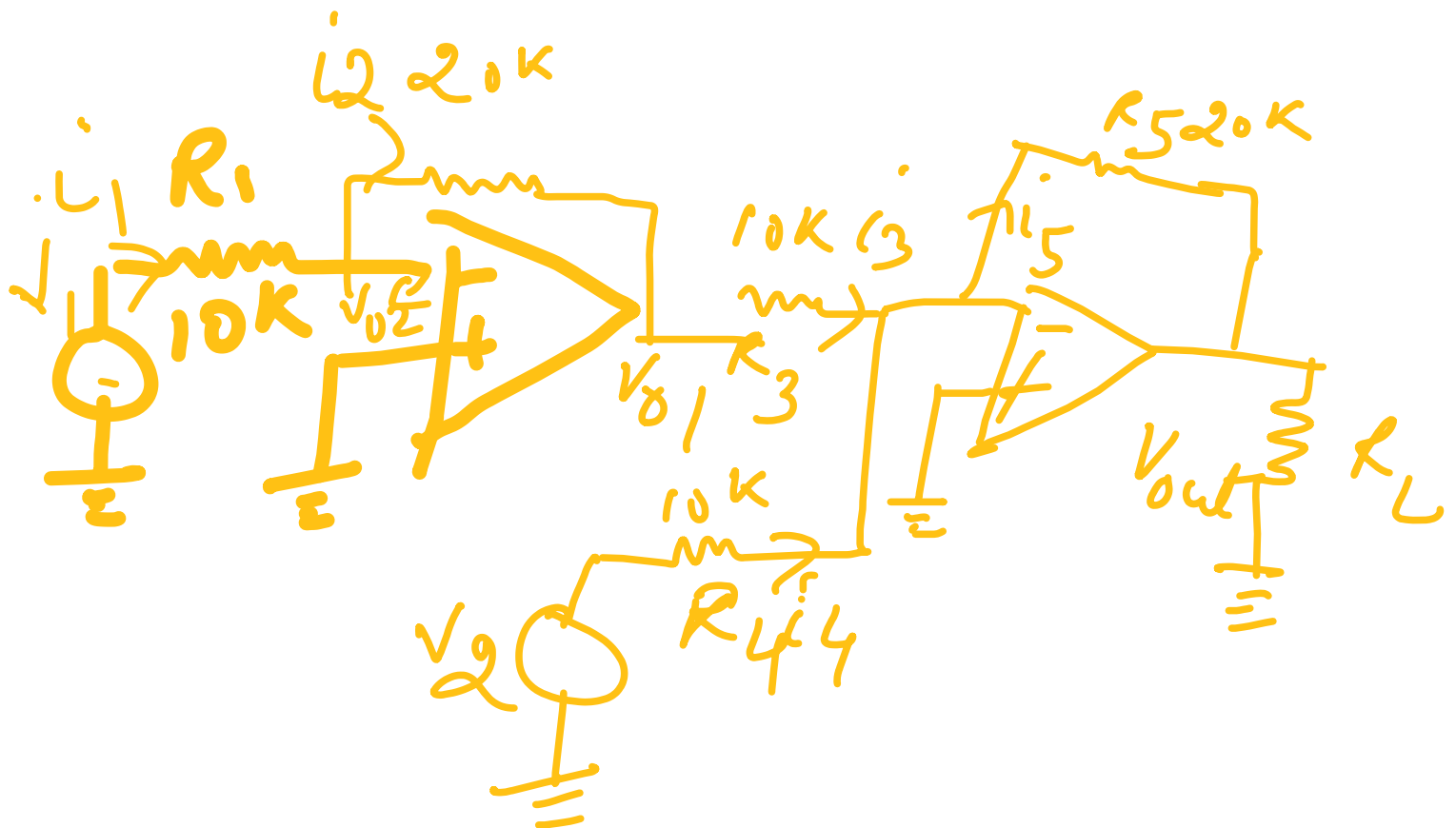

$$i_1 = i_2$$

$$\frac{V_1 - V_{02}}{10} = \frac{V_{02} - V_{01}}{20}$$

$V_{02} = 0$ due to virtual ground

$$\frac{V_1}{10} = -\frac{V_{01}}{20} \quad \text{Also } i_3 + i_4 = 5$$

$$V_0 = 4V_1 - 2V_2$$