


## TUTE 7

### Network, Analysis, and Synthesis

Q.1. Find the hybrid parameter of the following circuit shown in figure 1.

**Ans.**


$$\begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} = \begin{bmatrix} \frac{R_A(R_B + R_C) + (1 - \alpha)R_B R_C}{R_B + R_C} & \frac{R_B}{R_B + R_C} \\ \frac{(\alpha R_C + R_B)}{(R_B + R_C)} & \frac{1}{(R_B + R_C)} \end{bmatrix}$$

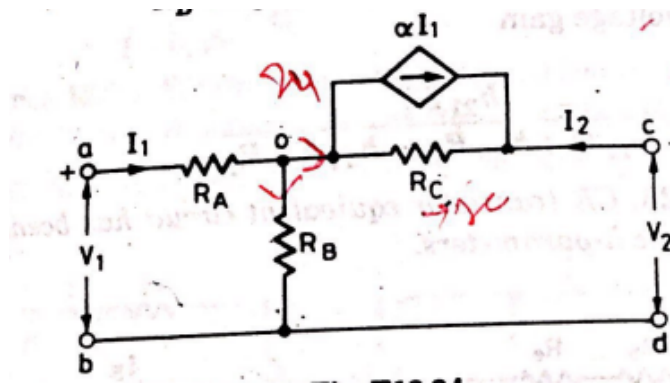

**Figure.1.**

Q2. Obtain transmission parameters of the network shown in figure 2

$$\text{Ans. } \begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 4 & \frac{5}{2} \\ 2 & \frac{3}{2} \end{bmatrix}$$

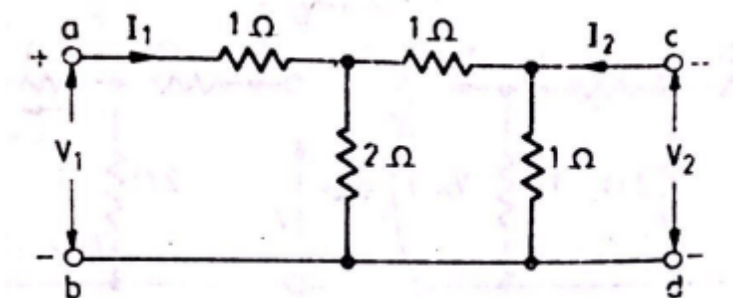

**Figure 2**

Q3. Find ABCD parameters of the following network shown in figure 3.

Ans.  $\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 3 & 8 \\ 1 & 3 \end{bmatrix}$

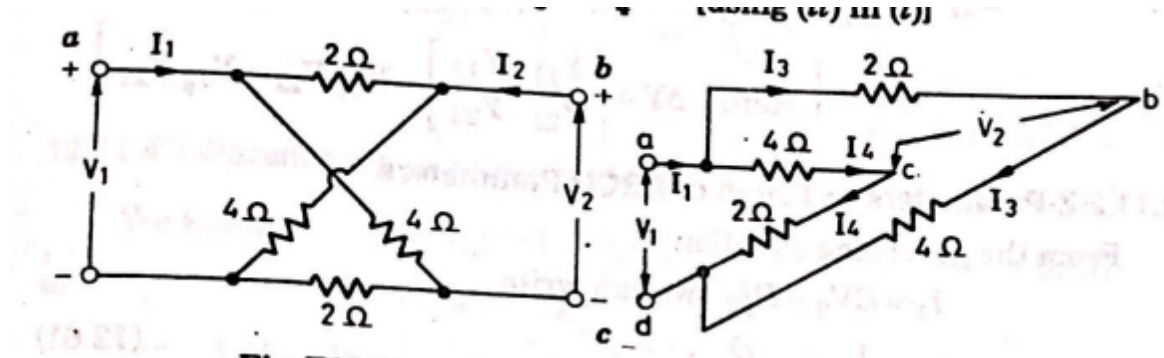


Figure 3

Q4. In the circuit shown in figure 4  $r_1 = 10 \text{ k}\Omega$ ,  $r_2 = 40 \text{ k}\Omega$ ,  $\alpha = 25$ ,  $\beta = 3 \times 10^{-4}$ , and  $R_L = 50 \text{ k}\Omega$ . Find out (1). h parameters (2). Voltage gain

Ans.  $\begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} = \begin{bmatrix} 10 & 3 \times 10^{-4} \\ 25 & 25 \times 10^{-6} \end{bmatrix}$  and  $(V_2/V_1 = -56.5)$

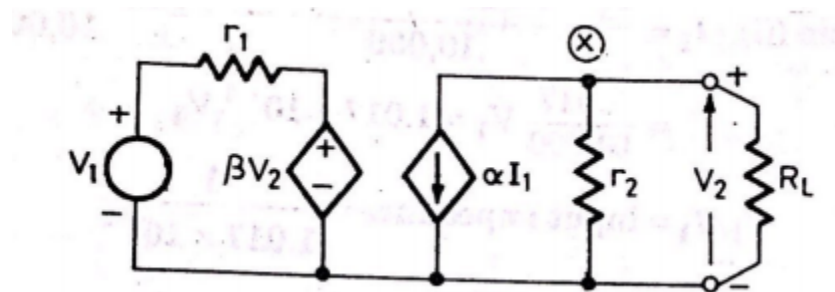


Figure 4