
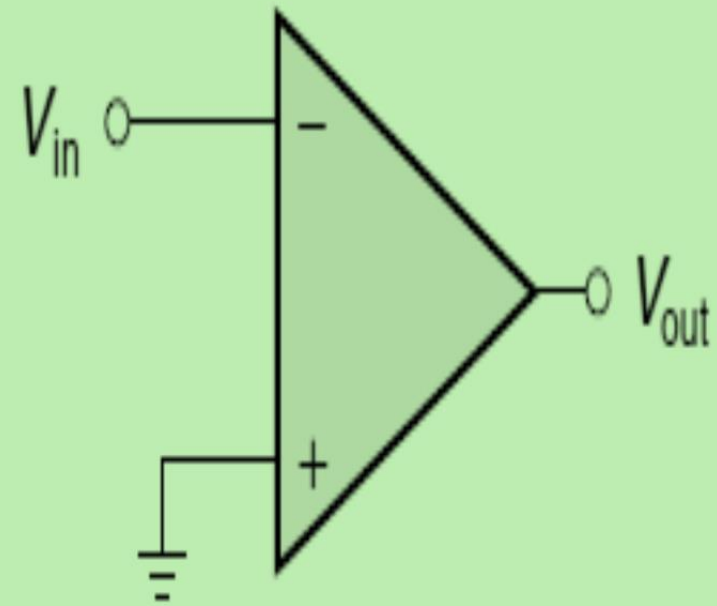


. OP-AMP BASED SIGNAL CONDITIONING CIRCUITS



Lecture -1 (B)

OP AMP CKTS

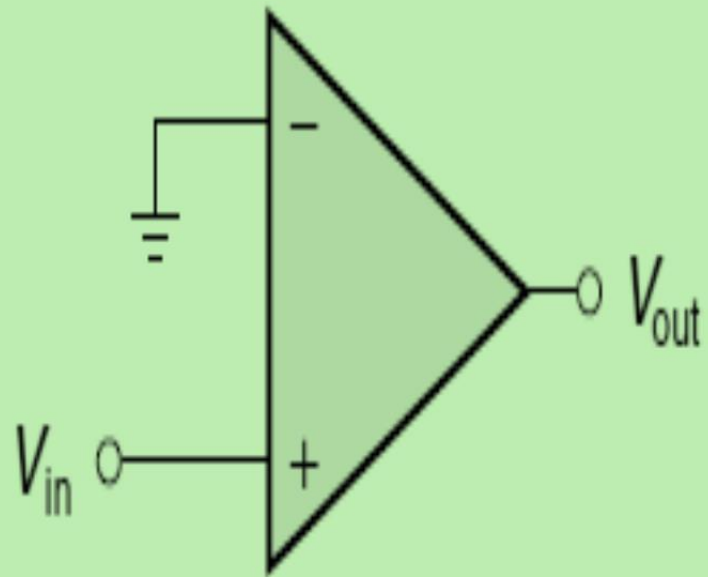


Voltage follower (Isolation Amplifier, Buffer Amplifier, and Unity-Gain Amplifier)

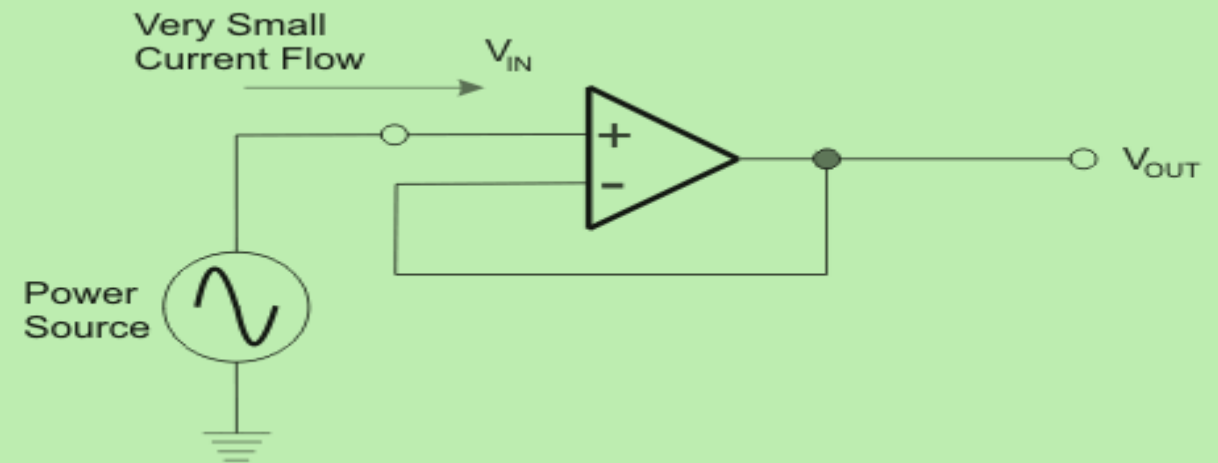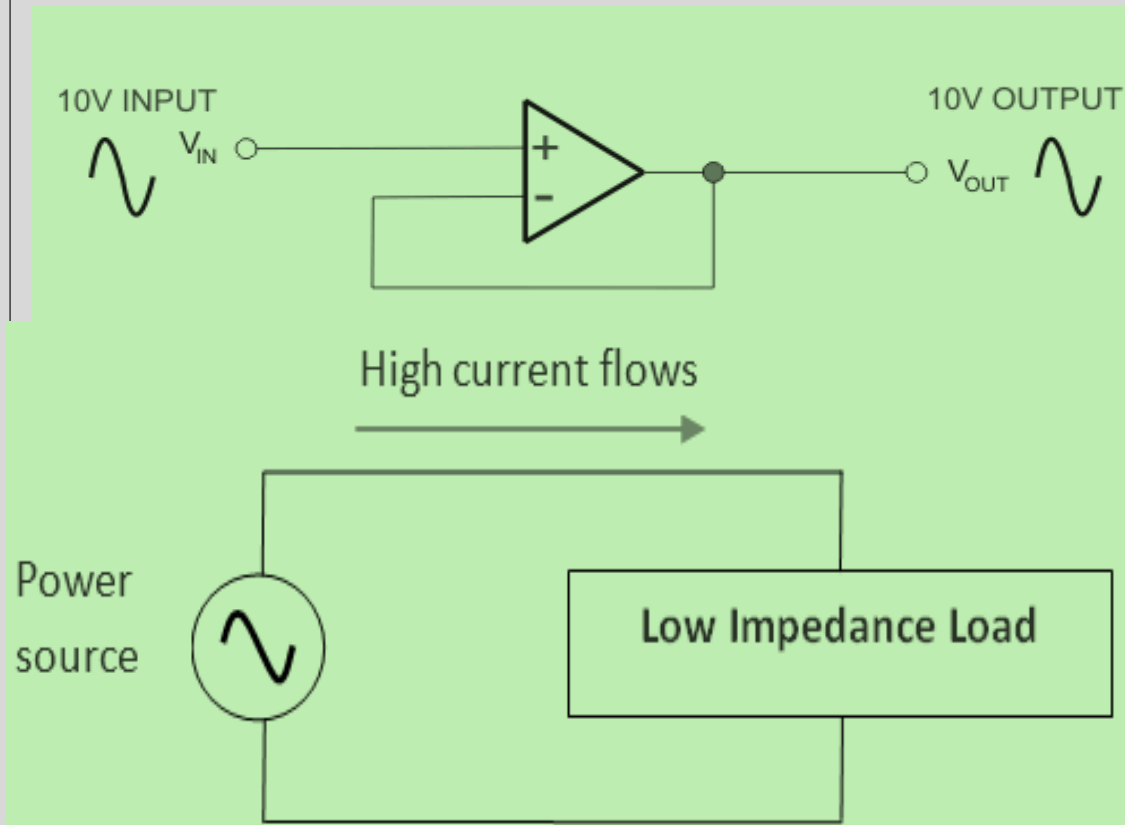- when resistance increases, the current drawn from the power source decreases.
- When Op-amp is connected, the major part of voltage will drop across it due to high impedance.
- So, if we use voltage follower in voltage divider circuits, it will let adequate voltage to be supplied across the load.



Voltage Follower (Unity Gain Buffer)


- When the circuit will have a fixed gain of "1" and would be classed as a **Voltage Follower**.
- As the input signal is connected directly to the noninverting input of the amplifier the output signal is not inverted resulting in the output voltage being equal to the input voltage, $V_{out} = V_{in}$.
- This then makes the Voltage Follower circuit ideal as a *Unity Gain Buffer* circuit because of its isolation properties as impedance or circuit isolation is more important than amplification.

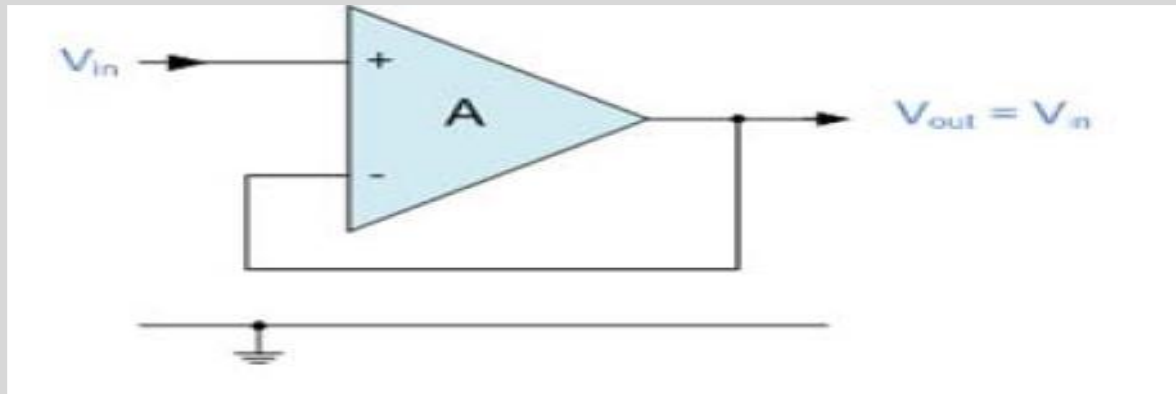

Contd..


- As the input voltage V_{in} is applied to the non-inverting input the gain of the amplifier is given as:

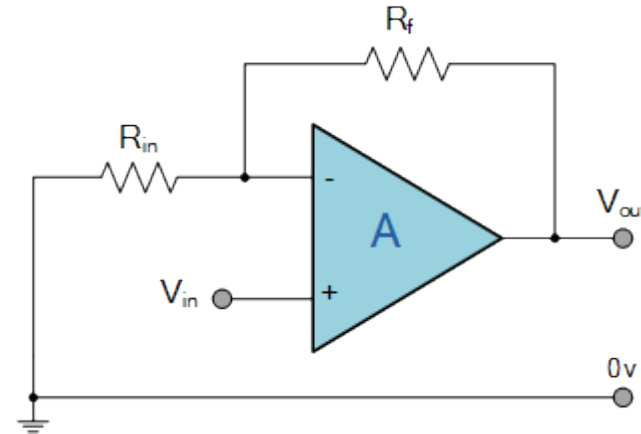- $A_{CL} = 1 + (R_{in} / R_f)$
- So $V_{out} = A_{CL} * V_{in}$
- $V_{out} = V_{in}$



- The voltage follower or unity gain buffer is a special and very useful type of **Noninverting amplifier** circuit that is commonly used in electronics to isolate circuits from each other especially in High-order state variable.

Contd...

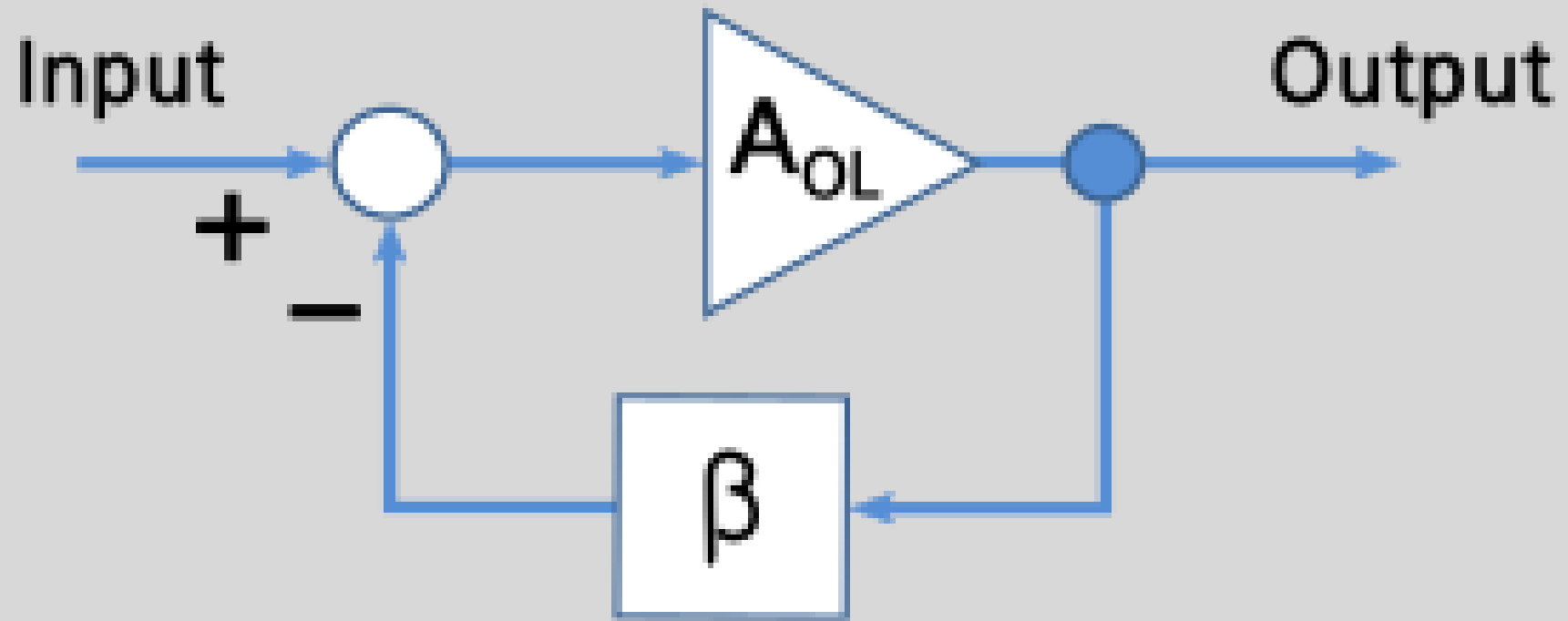


Advantages of Voltage Follower


- The Op-amp takes zero current from the input.
- Loading effects can be avoided.
- Provides power gain and current gain.
- Low output impedance to the circuit which uses the output of the voltage follower.

Summing Amplifier

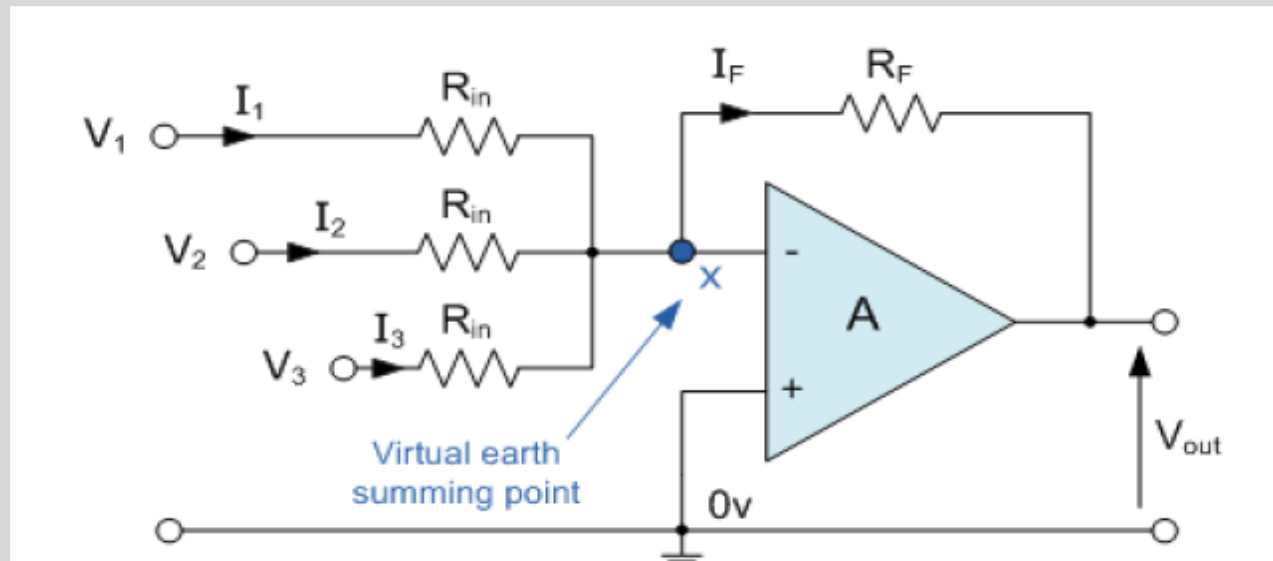- The **Summing Amplifier** is a very flexible circuit based upon the standard *Inverting Operational Amplifier* configuration.
- If add another input resistor equal in value equal to the original input resistor, a new configuration of another operational amplifier circuit called a **Summing Amplifier**, "Summing Inverter" or "Voltage Adder" circuit.



Contd..

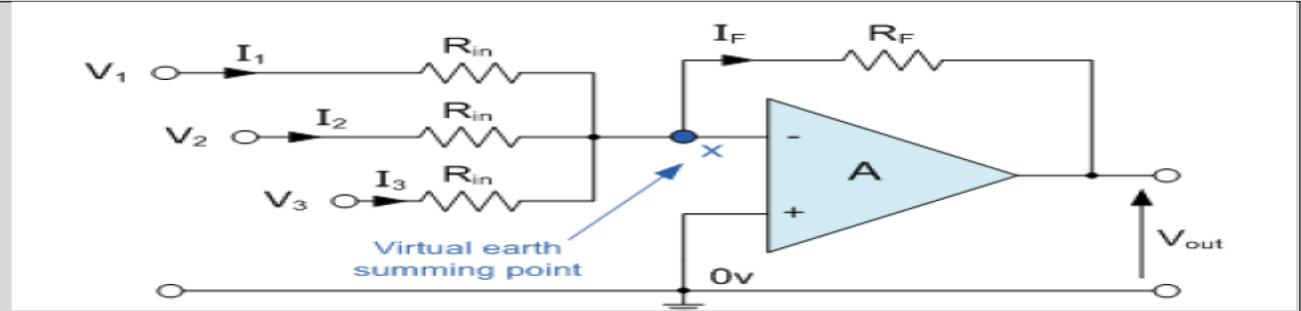


- The output voltage, (V_{out}) now becomes proportional to the sum of the input voltages, V_1 , V_2 , V_3 etc.
- Then modify the original equation for the inverting amplifier

$$I_F = I_1 + I_2 + I_3 = -\left[\frac{V_1}{R_{in}} + \frac{V_2}{R_{in}} + \frac{V_3}{R_{in}}\right]$$

$$V_{out} = -\frac{R_F}{R_{in}}(V_1 + V_2 + V_3)$$

- The **Summing Amplifier** is a very flexible circuit indeed, enabling us to effectively "Add" or "Sum" together several individual input signals.
- If the input resistors are all equal a unity gain inverting adder can be made.
- However, if the input resistors are of different values a scaling summing amplifier is produced which gives a weighted sum of the input signals.


Practical Adder circuit

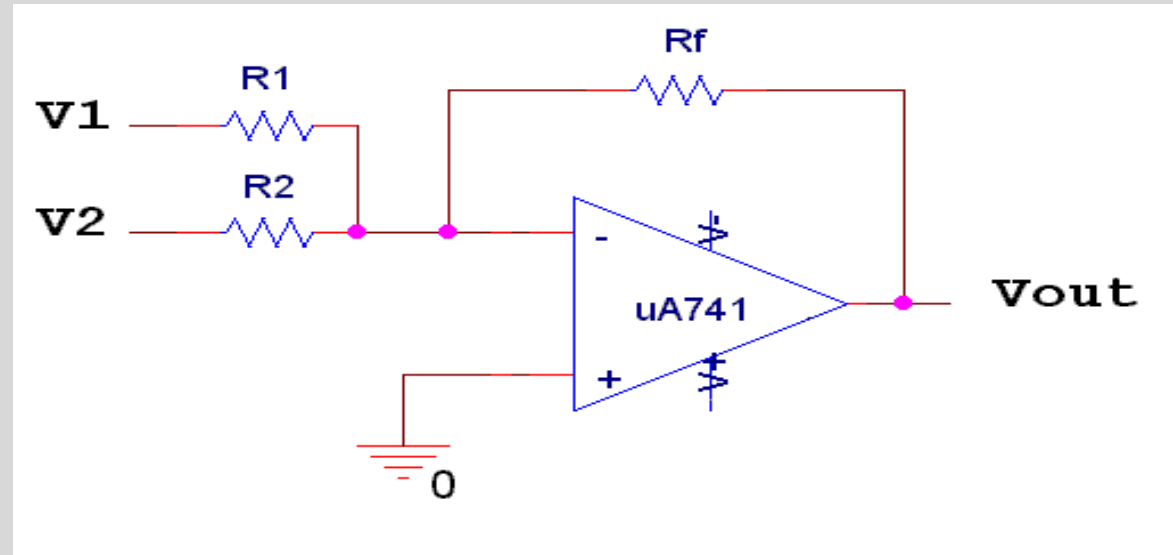

$$V_{out} = -R_f \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} \right)$$

if $R_1 = R_2$ then $\frac{V_{out}}{V_1 + V_2} = -\frac{R_f}{R_1}$

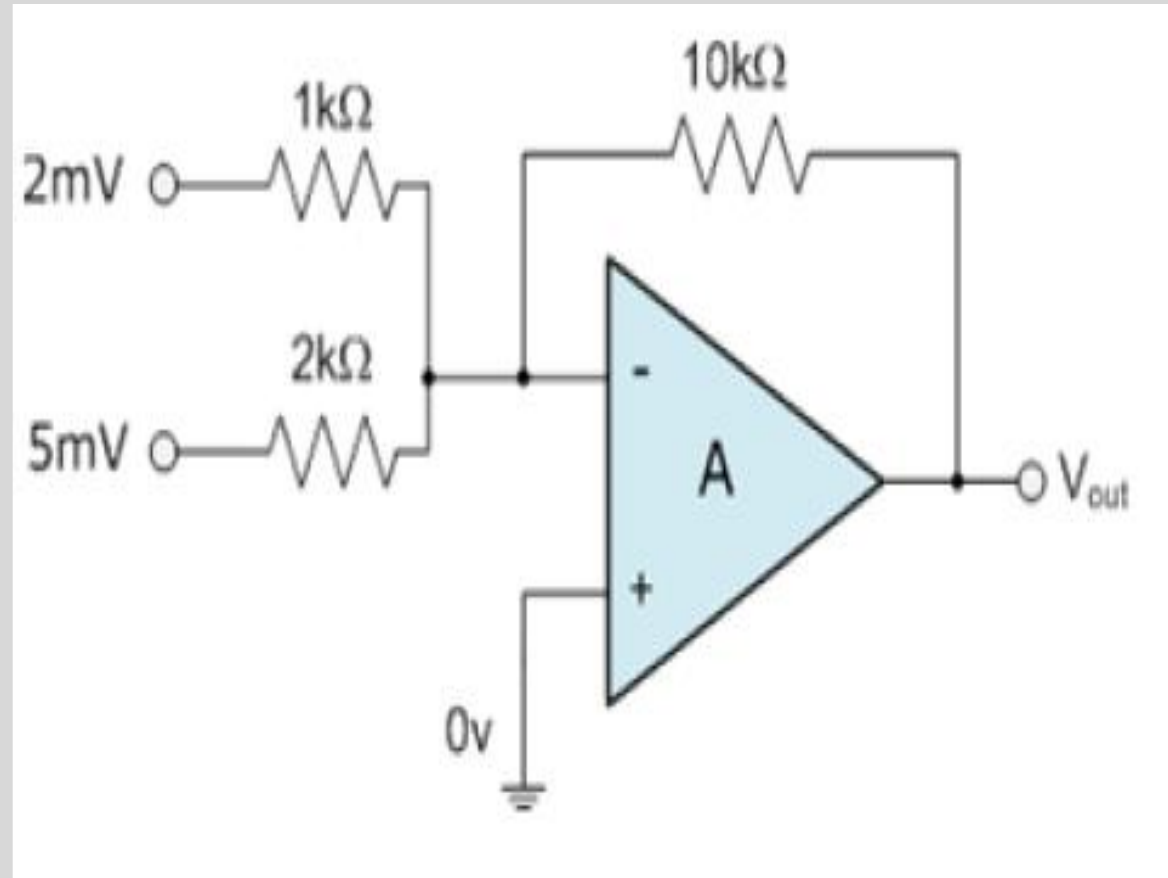Find the output voltage of the following
Summing Amplifier circuit




Solution

$$\text{Gain} = \frac{V_o}{V_{in}} = -\frac{R_f}{R_{in}}$$


$$A_1 = \frac{10k\Omega}{1k\Omega} = -10, \quad A_2 = \frac{10k\Omega}{2k\Omega} = -5$$
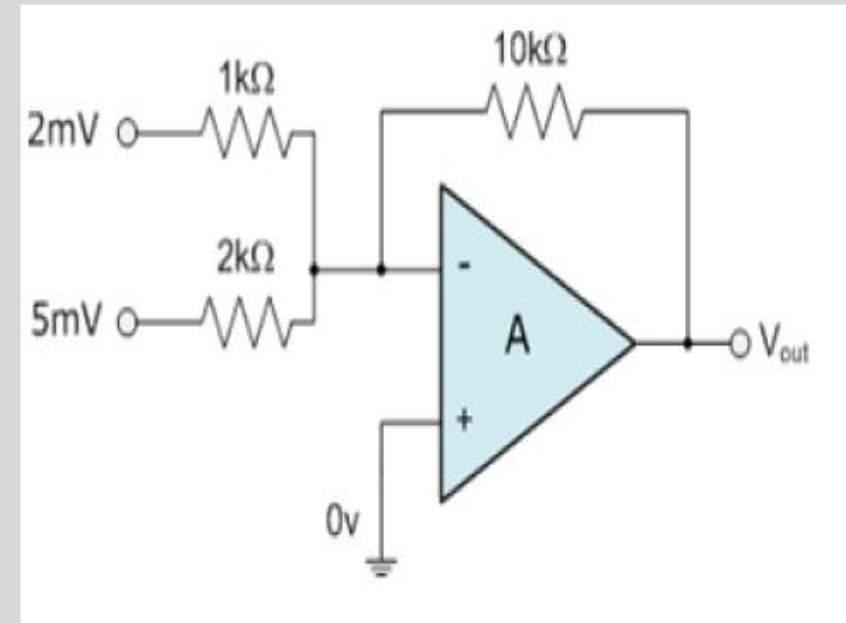
$$\begin{aligned} V_o &= (-10(2mV)) + (-5(5mV)) \\ &= -45mV \end{aligned}$$



Difference Amplifier

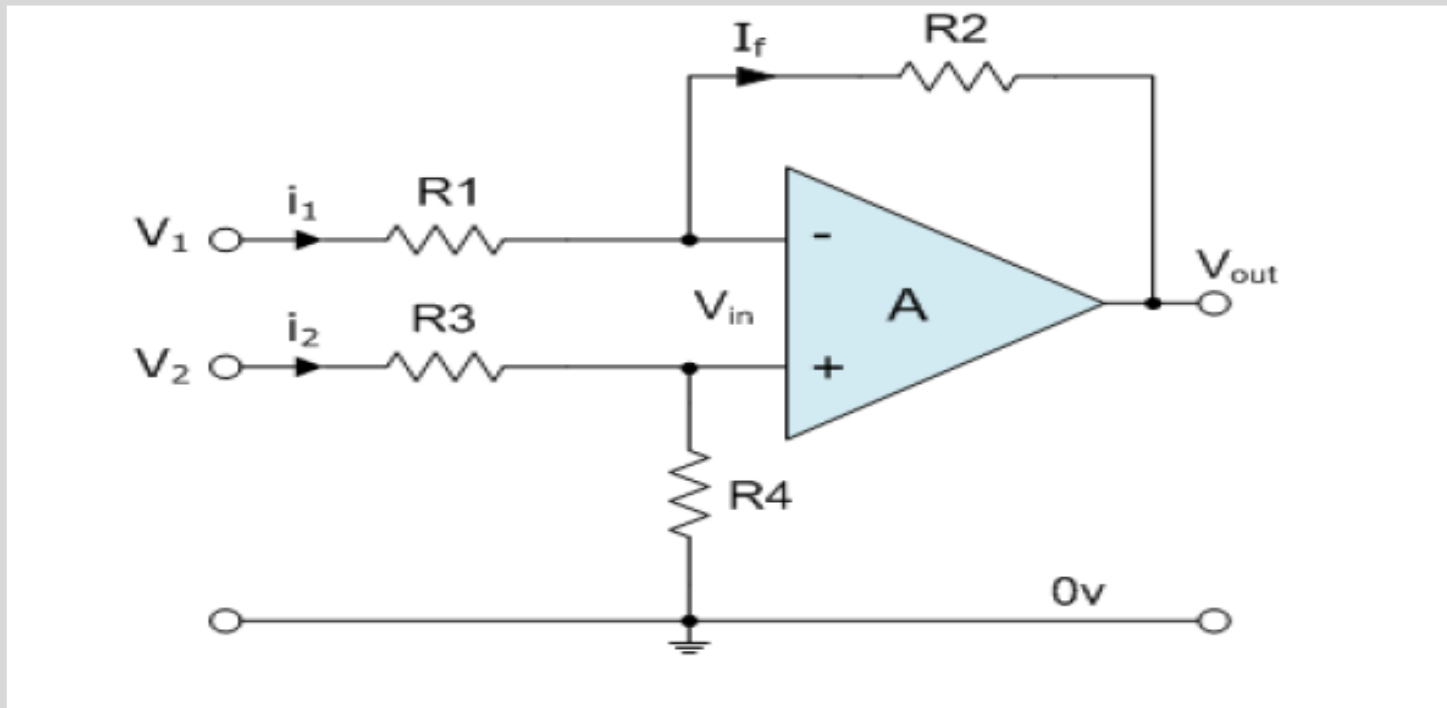- If connect signals to both of the inputs at the same time producing another common type of operational amplifier circuit called a differential amplifier.
- The resultant output voltage will be proportional to the "Difference" between the two input signals, V_1 and V_2 . This type of circuit can also be used as a subtractor.



Contd..

- The transfer function for a differential amplifier circuit is given as


$$V_o = -\frac{R_2}{R_1}V_1 + (1 + \frac{R_2}{R_1})(\frac{R_4}{R_3 + R_4})V_2$$

- When $R_1 = R_3$ and $R_2 = R_4$ the transfer function formula can be modified to

$$V_o = \frac{R_2}{R_1}(V_2 - V_1)$$

- If all the resistors are all of the same ohmic value the circuit will become a **Unity Gain Differential Amplifier** and the gain of the amplifier will be 1 or Unity.
- One major limitation of this type of amplifier design is that its input impedances are lower compared to that of other operational amplifier configurations.
- Each input voltage source has to drive current through an input resistance, which has less overall impedance than that of the op-amps input alone.
- One way to overcome this problem is to add a *Unity Gain Buffer Amplifier* such as the voltage follower.

Derivation

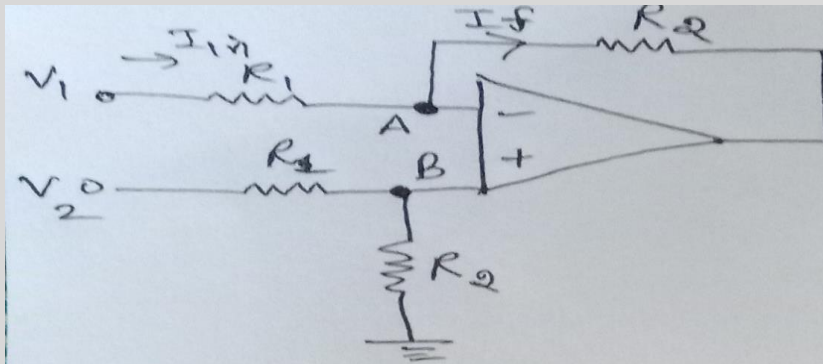

$$V_0 = A_{CL}(V_1 - V_2)$$

Due to virtual Concept

$$V_A = V_B \quad - (1)$$

and apply KCL at node A

$$I_{in} = I_f \quad - (2)$$

Voltage at node B is V_B

$$V_B = \frac{R_2}{R_1 + R_2} \cdot V_2 \quad - (3)$$

$$I_{in} = \frac{V_1 - V_A}{R_1}$$

$$I_f = \frac{V_A - V_0}{R_2}$$

Put value of $I_{in} + I_f$ in eq (2)

$$\frac{V_1 - V_A}{R_1} = \frac{V_A - V_0}{R_2}$$

Contd..

$$\frac{V_1}{R_1} - \frac{V_A}{R_1} = \frac{V_A}{R_2} - \frac{V_0}{R_2}$$

$$\frac{V_1}{R_1} - \frac{V_A}{R_1} - \frac{V_A}{R_2} = -\frac{V_0}{R_2}$$


$$\frac{V_1}{R_1} - V_A \left(\frac{R_1 + R_2}{R_1 R_2} \right) = -\frac{V_0}{R_2}$$

$$\frac{V_1}{R_1} - \left(\frac{R_2}{R_1 + R_2} \right) \left(\frac{R_1 + R_2}{R_1 R_2} \right) V_2 = -\frac{V_0}{R_2}$$

$$\frac{1}{R_1} (V_1 - V_2) = -\frac{V_0}{R_2} \quad \text{Gain} \rightarrow$$

$$V_0 = -\frac{R_2}{R_1} \underbrace{(V_1 - V_2)}_{\text{difference}} \rightarrow$$

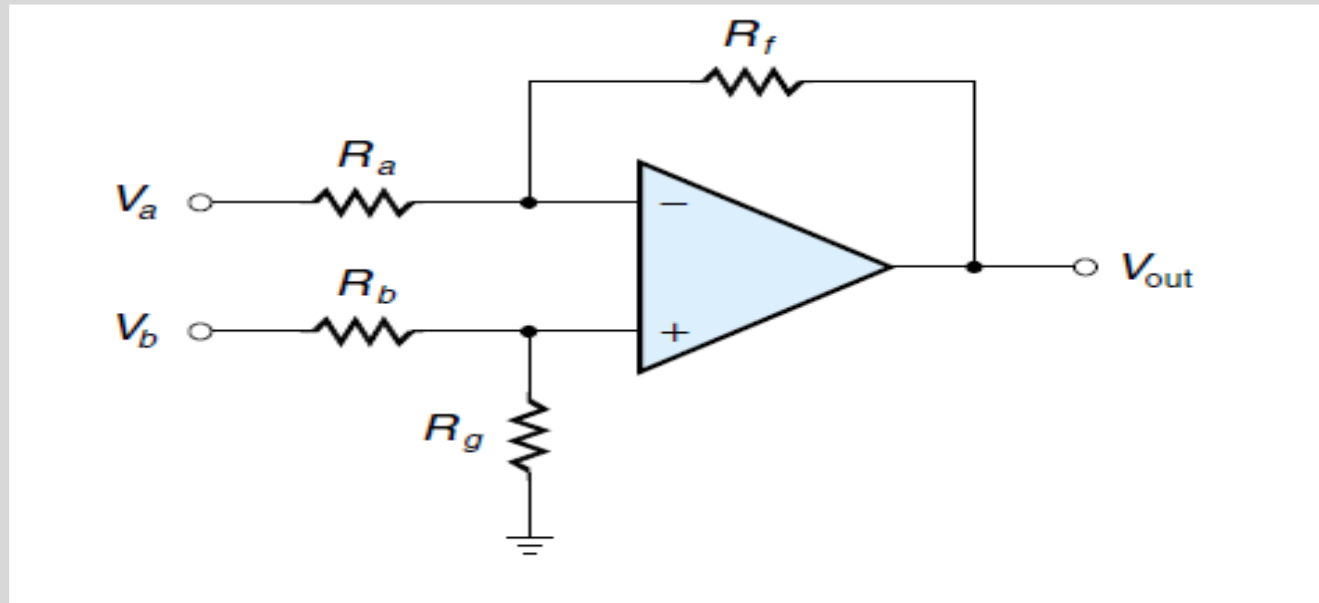Q2. A differential amp is needed to amplify the voltage difference between two temperature sensors. The sensors have an internal resistance of $50\text{ k}\Omega$, and the maximum voltage difference between the sensors will be 2 V . Design the differential amp circuit to have an output of 12 V when the difference the inputs is 2 V .



Solution


$$A_V = \frac{V_{\text{out}}}{V_{\text{in}}} = \frac{12\text{V}}{2\text{V}} = 6$$

$$R_a = R_b \text{ and } R_f = R_g$$

$$A_V = \frac{R_f}{R_a} = 6$$

$$R_f = R_a \times 6$$
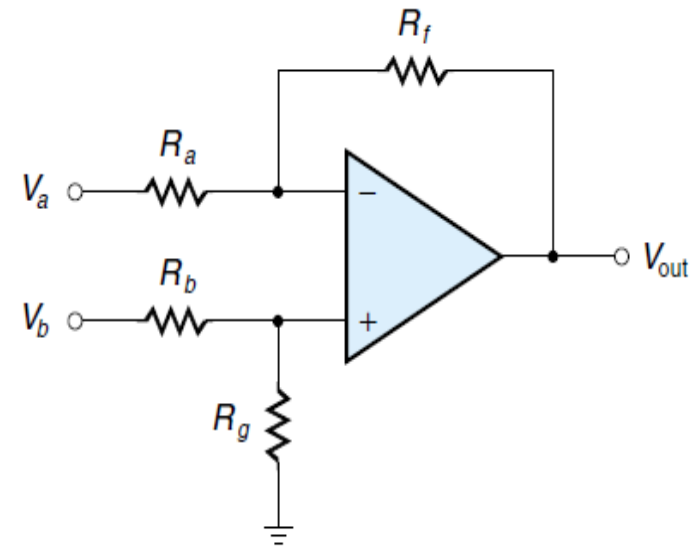
$$= 50 \text{ k}\Omega \times 6 = 300 \text{ k}\Omega$$



References

- ❖ *Coughlin, R.F., Operational Amplifiers and Linear Integrated Circuits, Pearson Education (2006).*
- ❖ *Gayakwad, R.A., Op-Amp and Linear Integrated Circuits, Pearson Education (2002).*
- ❖ *Franco, S., Design with Operational Amplifier and Analog Integrated circuit, McGraw Hill (2016).*
- ❖ *Terrell, D., Op Amps Design Application and Troubleshooting, Newness (1996).*