

TUTE-09
Network Analysis and Synthesis (UEE 503)
Department of Electrical and Instrumentation Engineering

- Q1. Find the pole zero locations of the current transfer ratio I_1/I_2 in s-domain for the network shown in Fig. 1. (0 or -200)

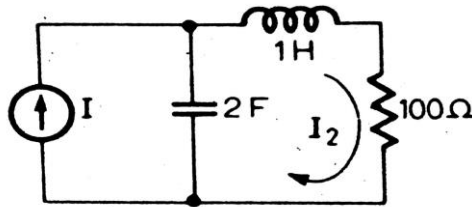


Fig. 1

- Q2. In the network shown in Fig. 2 find voltage transfer ratio $[G_{12}(s)]$ and pole zero plot.
 $(-10s/(20s+2+s^2))$.

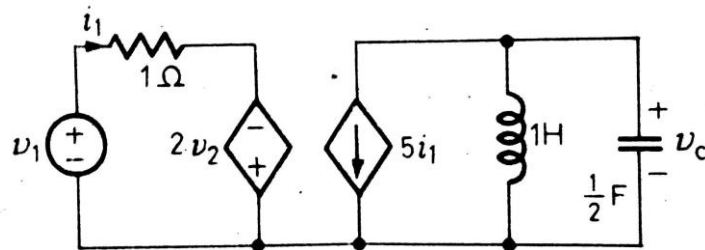


Fig. 2

- Q3. For the network shown in Fig. 3 Find driving point impedance and its pole zero plots.
 $[5(s+0.001)(s+0.04)/s(s+0.03)]$

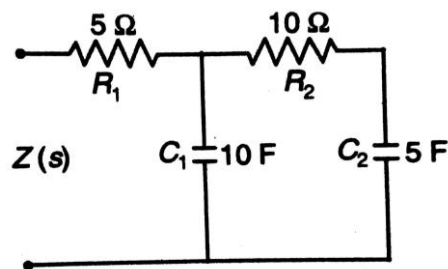


Fig. 3