
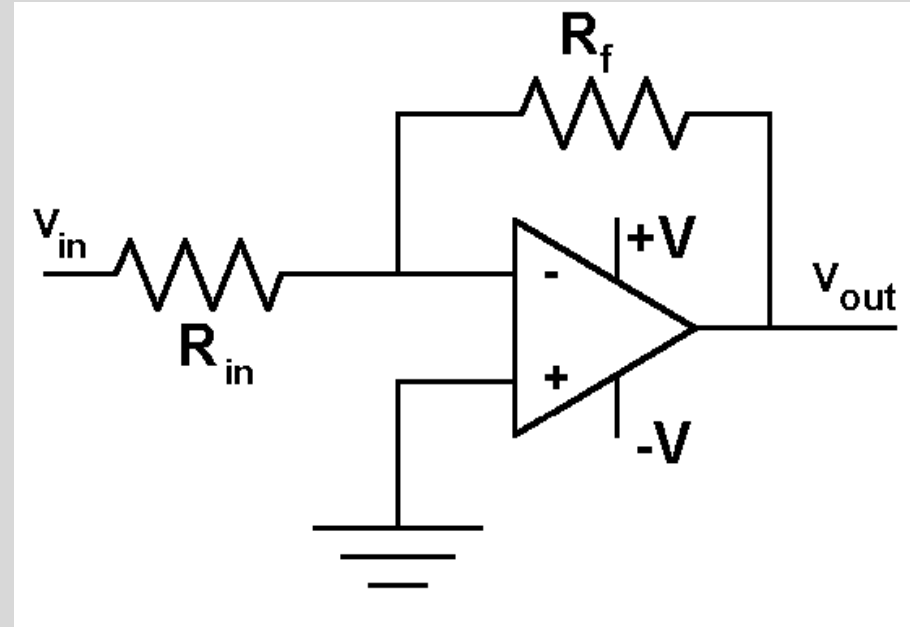


OP-AMP BASED SIGNAL CONDITIONING CIRCUITS

Op-Amp Circuits


- Op-Amps circuits can perform mathematical operations on input signals:
 - Addition and subtraction
 - Multiplication and Division
 - Differentiation and integration
- Other common uses include:
 - Impedance buffering
 - Active filters
 - Active controllers
 - Analog-digital interfacing
 - Rectifiers

Inverting Amplifier

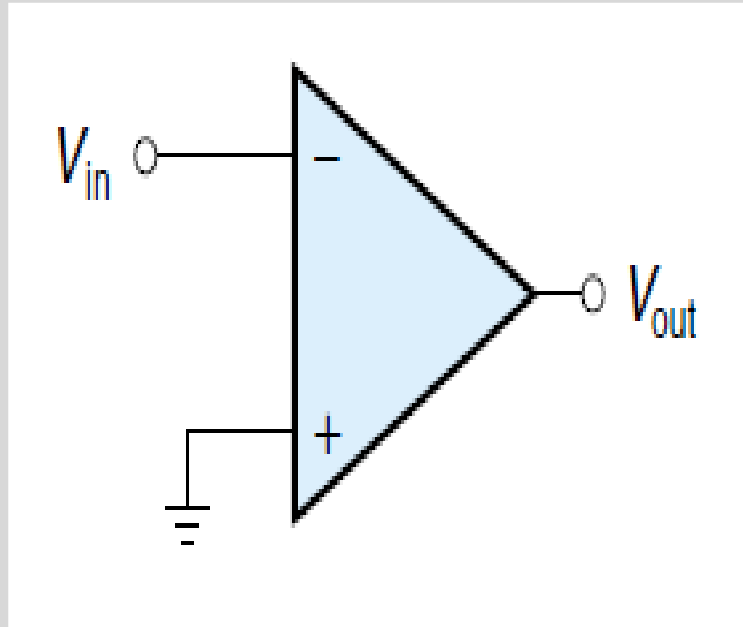

$$V_{out} = -\frac{R_f}{R_{in}} V_{in} \quad A = -\frac{R_f}{R_{in}}$$

Contd..

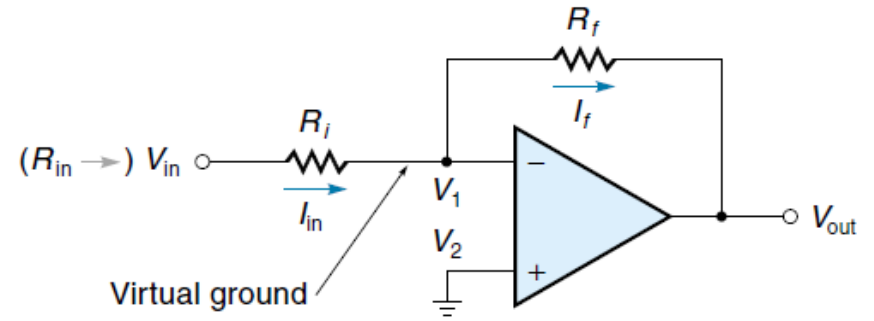

- Most op-amp circuits incorporate **negative feedback**. This means that a portion of the output signal is fed back and subtracted from the input.
- Negative feedback results in a very stable and predictable operation at the expense of lowered gain.
- From the Ohm's law

$$I_{in} = \frac{V_{in}}{R_i}$$

$$I_{in} = I_f = \frac{0 - V_{out}}{R_f}$$

$$A_v = \frac{-R_f}{R_i}$$

$$\frac{V_{in}}{R_i} = \frac{0 - V_{out}}{R_f}$$



$$\frac{V_{out}}{V_{in}} = \frac{-R_f}{R_i}$$

- This result shows us that the voltage gain of the inverting amp is simply the ratio of the two resistors R_f and R_i .
- The minus sign indicates that the output is inverted.
- The gain derived is called the **closed-loop gain** and is always lower than the (open-loop) gain of the op-amp by itself.

An inverting amp is to have a gain of 10. The signal source is a sensor with an output impedance of 1 k Ω ($R_{in}=10\text{Kohm}$). Draw a circuit diagram of the completed amplifier.

$$R_i = 10 \text{ k}\Omega.$$
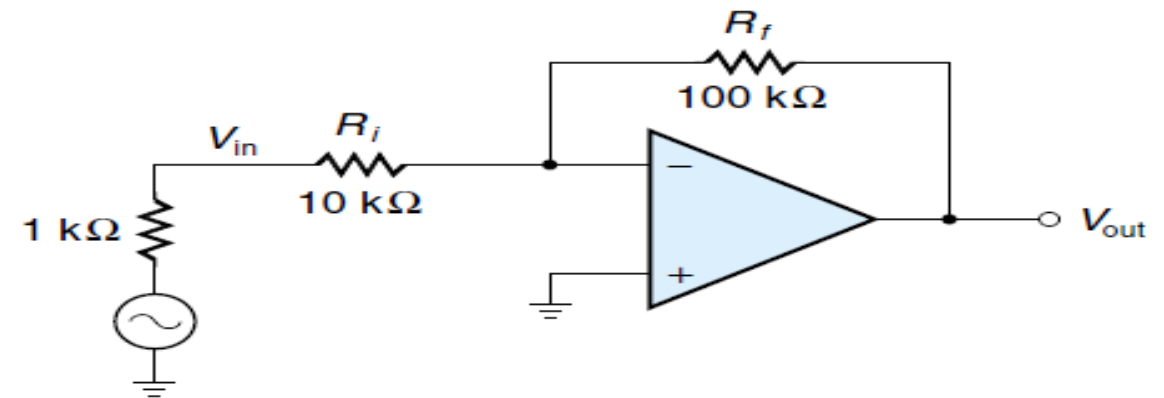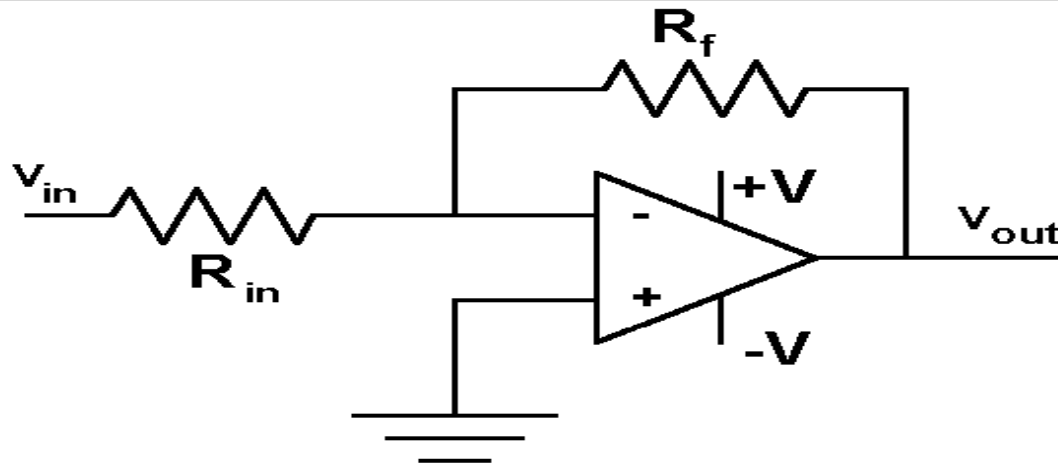
$$\begin{aligned} R_f &= -AR_i \\ &= -(-10) \times 10 \text{ k}\Omega = 100 \text{ k}\Omega \end{aligned}$$




Unity Gain Inverter


- If the two resistors are of equal value, $R_{in} = R_f$ then the gain of the amplifier will be -1 producing a complementary form of the input voltage at its output as $V_{out} = -V_{in}$.
- This type of inverting amplifier configuration is generally called a Unity Gain Inverter or simply an *Inverting Buffer*.

$$A_v = \frac{-R_f}{R_i}$$

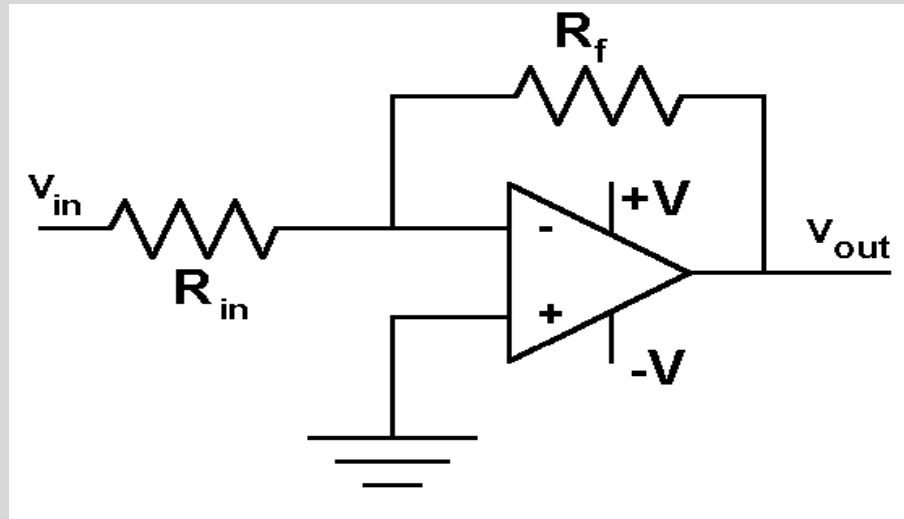
$$\frac{V_{out}}{V_{in}} = \frac{-R_f}{R_i}$$




Non-inverting Amplifier

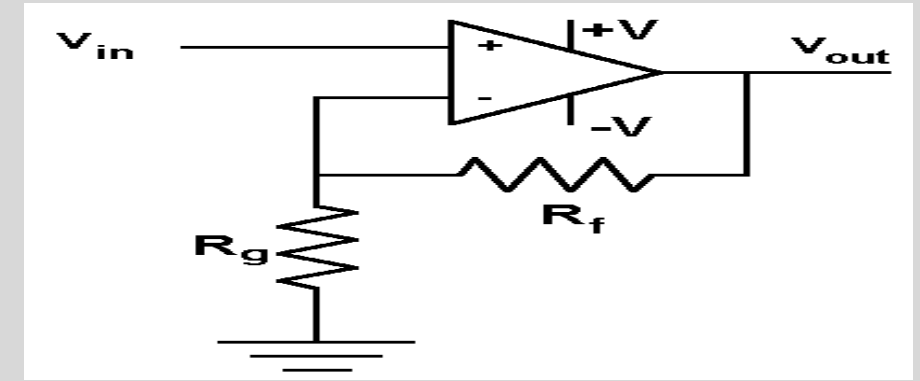


- A non-inverting Op-Amp circuit is one whose output is in phase with the input.
- The inverting terminal is connected through a resistor R_1/R_g to the ground.
- R_f is the feedback resistor. Many applications requires only amplification that does not invert the output.
- The output of a thermocouple might be such that as the temperature goes up, the voltage goes up. In such applications there is no requirement of phase shift.
- It is similar to the inverting amp except the input signal V_{in} now goes directly to the noninverting input and R_i is grounded.
- Notice that the noninverting amp has an almost infinite input impedance (R_i) because V_{in} connects only to the opamp input.

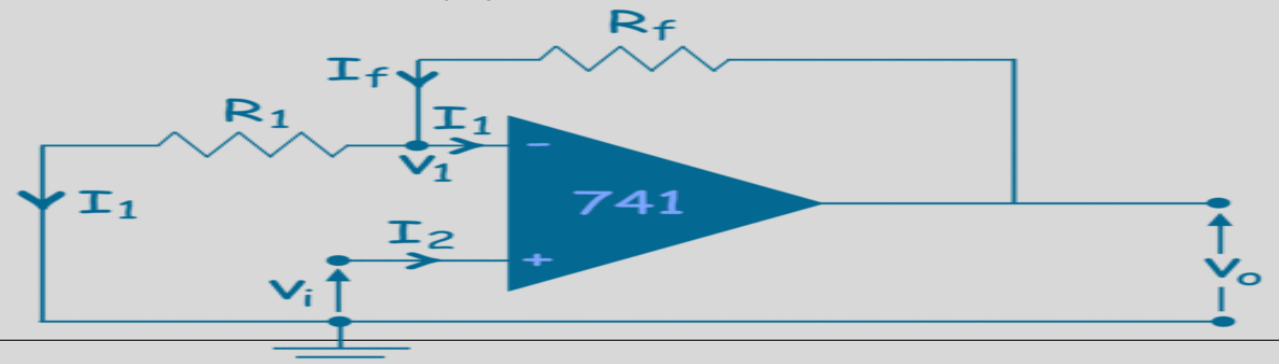

CIRCUIT DIAGRAM

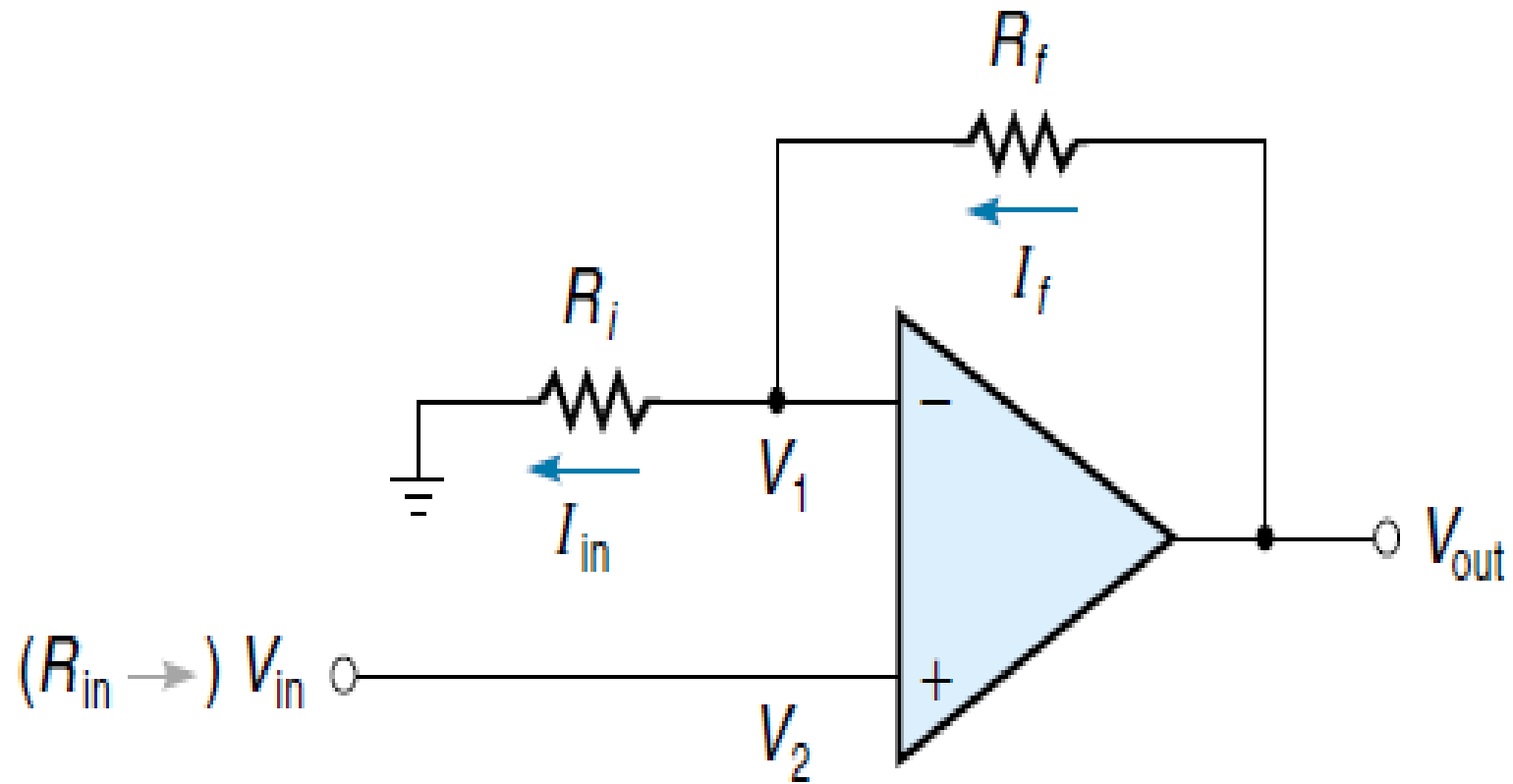

Contd..

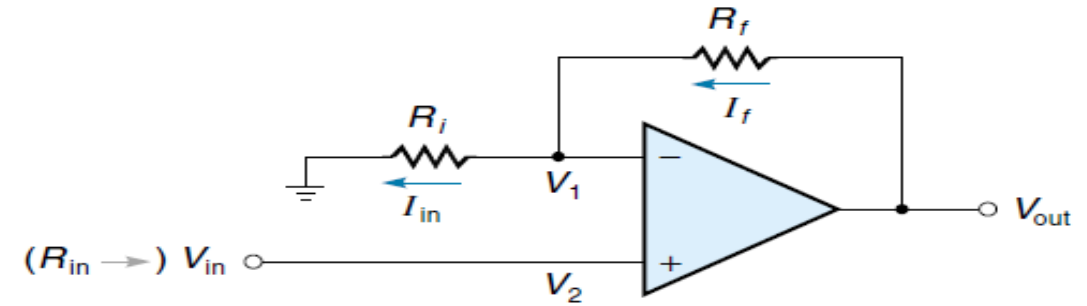

- If V_1 is virtually the same as V_2 , then the voltage input (V_{in}) appears across R_i . Applying Ohm's law to R_i ,

$$I_{in} = \frac{V_{in} - 0}{R_i}$$

- The current in R_f can also be calculated using Ohm's law. We know the voltage across R_f is the difference between V_{in} and V_{out} . Therefore,

$$I_f = \frac{V_{out} - V_{in}}{R_f}$$

$$I_{in} = I_f$$

$$I_{in} = I_f = \frac{V_{in} - 0}{R_i} = \frac{V_{out} - V_{in}}{R_f}$$

Contd..

$$V_{\text{out}} - V_{\text{in}} = \frac{R_f V_{\text{in}}}{R_i}$$
$$V_{\text{out}} = \frac{R_f V_{\text{in}}}{R_i} + V_{\text{in}} = V_{\text{in}} \left(\frac{R_f}{R_i} + 1 \right)$$
$$\frac{V_{\text{out}}}{V_{\text{in}}} = \frac{R_f}{R_i} + 1$$

$$A_v = \frac{R_f}{R_i} + 1$$


where

A_v = voltage gain for the noninverting amp

R_f = value of the feedback resistor

R_i = value of the input resistor

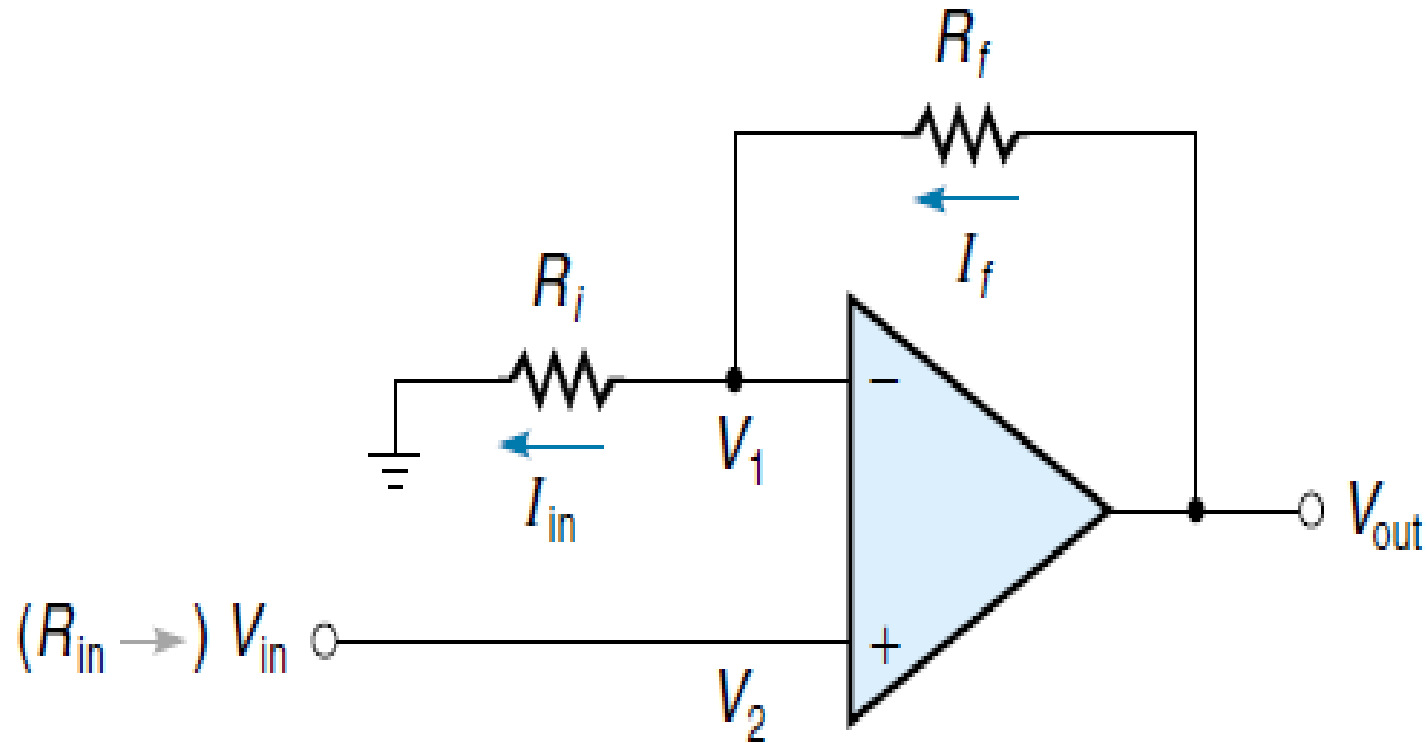Draw the circuit diagram of a noninverting amp with a gain of 20 ($R_i=2\text{ K}\Omega$).




Solution

$$A_V = 20 = \frac{R_f}{R_i} + 1$$

$$\frac{R_f}{R_i} = 19 \quad \text{or} \quad R_f = 19 \times R_i$$
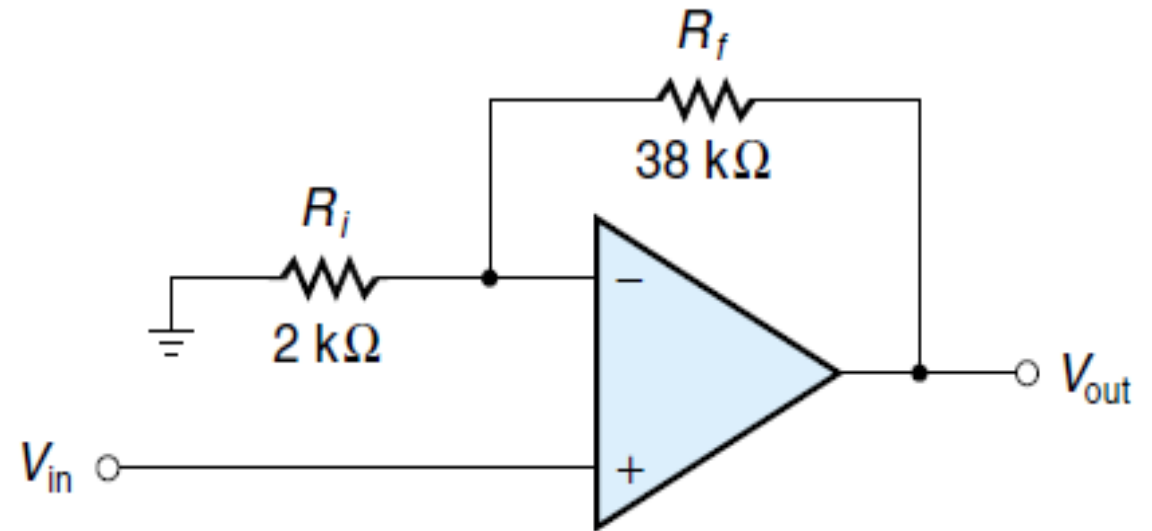
$$R_f = 19 \times R_i = 19 \times 2 \text{ k}\Omega = 38 \text{ k}\Omega$$



Steps in Analyzing Op-Amp Circuits

- 1) Remove the op-amp from the circuit and draw two circuits (one for the + and one for the – input terminals of the op amp).
- 2) Write equations for the two circuits.
- 3) Simplify the equations using the rules for op amp analysis and solve for V_{out}/V_{in}

- **Rule 1: $V_A = V_B$**

- The output attempts to do whatever is necessary to make the voltage difference between the inputs zero.
- The op-amp “looks” at its input terminals and swings its output terminal around so that the external feedback network brings the input differential to zero.

- **Rule 2: $I_A = I_B = 0$**

- The inputs draw no current
- The inputs are connected to what is essentially an open circuit

References

- *Coughlin, R.F., Operational Amplifiers and Linear Integrated Circuits, Pearson Education (2006).*
- *Gayakwad, R.A., Op-Amp and Linear Integrated Circuits, Pearson Education (2002).*
- *Franco, S., Design with Operational Amplifier and Analog Integrated circuit, McGraw Hill (2016).*
- *Terrell, D., Op Amps Design Application and Troubleshooting, Newness (1996).*