

# Analog and Digital Systems (UEE505)

## Lecture # 10

### Butterworth filters using op amp -II



THAPAR INSTITUTE  
OF ENGINEERING & TECHNOLOGY  
(Deemed to be University)

Deptt. Of Electrical & Instrumentation Engineering  
Thapar Institute of Engineering & Technology Patiala, India

# Designing Steps of LPF

- **Step 1:** Select or choose required cutoff frequency. Suppose we want to pass all the frequencies below 15 KHz that means frequencies that human can hear. Thus  $f_c = 15 \text{ KHz}$
- **Step 2:** Assume the required value of capacitor. It should be less than 0.1 micro Farad. This is required for better frequency stability.
- **Step 3:** calculate the value of resistance from equation.

$$f_L = \frac{1}{2\pi RC}$$

- **Step 4:** Choose required pass band gain and find the value of  $R_f$  &  $R_1$


$$A_F = \left(1 + \frac{R_f}{R_1}\right)$$

Select values of  $R_f$  &  $R_1$  as or around  $10\text{K}\Omega$ .

# Example

Design a non-inverting active low pass filter circuit that has a gain of ten at low frequencies, a high frequency cut-off or corner frequency of 159Hz and an input impedance of 10K $\Omega$ .

# LPF Circuit

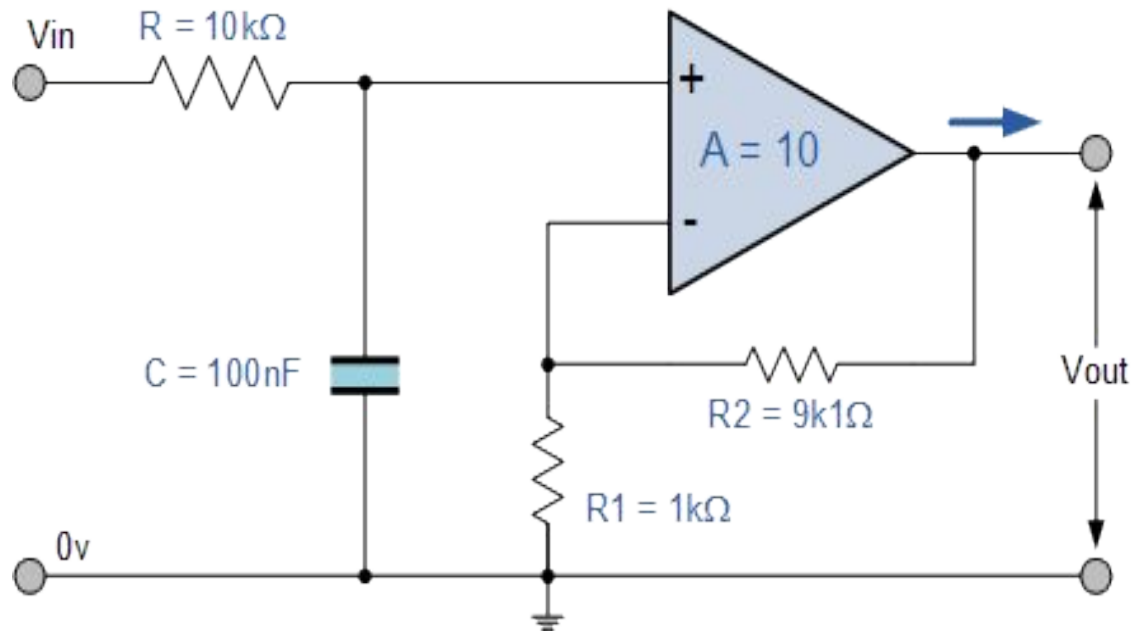

# Designing of High Pass Filter(HPF)


## Ist order Butterworth HPF

$$V_A = V_{in} \left[ \frac{R}{R - jX_C} \right]$$

$$V_A = V_{in} \left[ \frac{R}{-jX_C \left( \frac{R}{-jX_C} + 1 \right)} \right]$$

$$V_A = V_{in} \left[ \frac{\left( -\frac{R}{jX_C} \right)}{\left( -\frac{R}{jX_C} \right) + 1} \right]$$
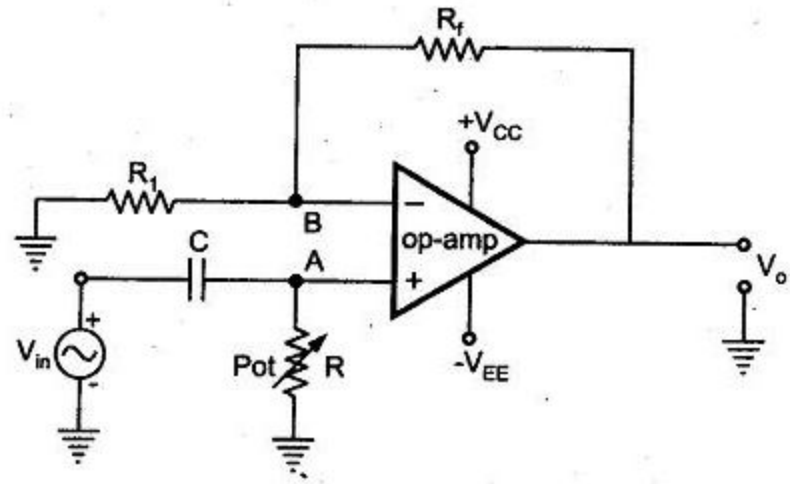
$$\begin{aligned} \text{Or } \frac{1}{-jX_C} &= \frac{j}{X_C} = \frac{j}{\left( \frac{1}{2\pi fC} \right)} \\ &= j2\pi fC \end{aligned}$$



$$\text{Therefore, } V_A = V_{in} \left[ \frac{j2\pi fRC}{1 + j2\pi fRC} \right]$$

$$V_A = V_{in} \left[ \frac{j \left( \frac{f}{f_L} \right)}{1 + j \left( \frac{f}{f_L} \right)} \right]$$

Where  $f_L = \frac{1}{2\pi RC}$  = low cut off frequency

$$V_o = A_F V_A$$


where

$V_A$  = Voltage at the non inverting input

and

$A_F = \left( 1 + \frac{R_f}{R_l} \right)$  = gain of op-amp in pass band
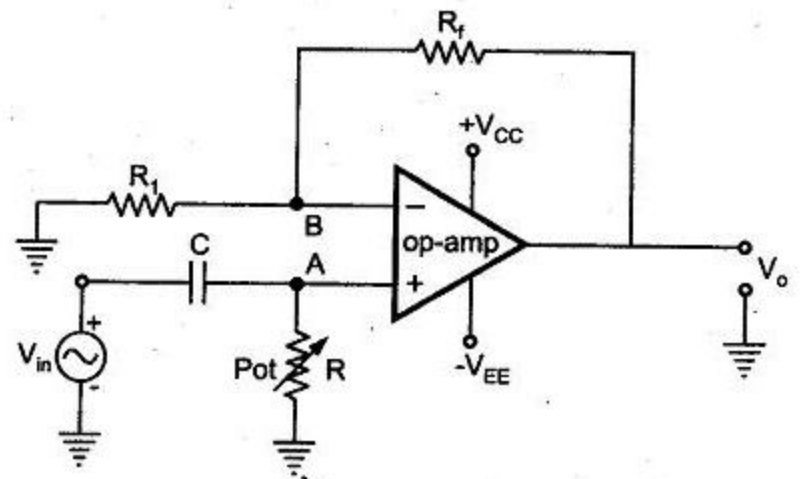
$$V_o = A_F V_{in} \left[ \frac{j \left( \frac{f}{f_L} \right)}{1 + j \left( \frac{f}{f_L} \right)} \right]$$



Thus, 
$$\frac{V_o}{V_{in}} = A_F \left[ \frac{j \left( \frac{f}{f_L} \right)}{1 + j \left( \frac{f}{f_L} \right)} \right]$$

# Frequency Response of HPF

$$\left| \frac{V_0}{V_{in}} \right| = \frac{A_F \left( \frac{f}{f_L} \right)}{\sqrt{1 + \left( \frac{f}{f_L} \right)^2}}$$

Now to observe the change in gain magnitude with the change in the frequency of the input signal, consider three cases:

1) At low frequencies, i.e.  $f < f_L$


$$\left| \frac{V_0}{V_{in}} \right| < A_F$$

2) At  $f = f_L$

$$\left| \frac{V_0}{V_{in}} \right| = 0.707 A_F \text{ i.e. 3 dB down from the level of } A_F$$

3) At  $f > f_L$ , i.e. high frequencies, 1 can be neglected as compared to  $\left( \frac{f}{f_L} \right)$  from denominator.

$$\left| \frac{V_0}{V_{in}} \right| \cong A_F \text{ i.e. constant}$$

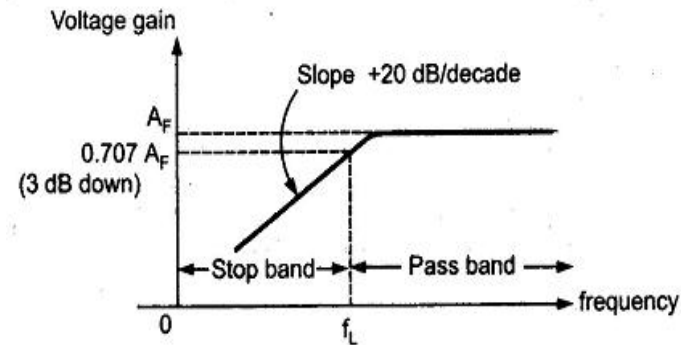

# Designing Steps of HPF

- **Step 1:** select or choose required cut off frequency.  
Suppose we want to suppress all the frequencies below 100 Hz. Thus  $f_c = 100 \text{ Hz}$
- **Step 2:** Assume the required value of capacitor. It should be less than 0.1 micro Farad. This is required for better frequency stability.
- **Step 3:** calculate the value of resistance from equation.

$$f_L = \frac{1}{2 \pi R C} = \text{low cut off frequency}$$

- **Step 4:** Choose required pass band gain and find the value of  $R_f$  &  $R_1$   $A_F = \left(1 + \frac{R_f}{R_1}\right)$  Select values of  $R_f$  &  $R_1$  as or around 10K $\Omega$ .



# References

- ❖ For more details, refer to:
  - *Boylestad R. L., Electronic Devices and Circuit Theory, Pearson Education*
  - *Op-Amps and Linear Integrated Circuits, Ramakant A. Gayakwad*
  - *Neamen, Donald A., Electronic Circuit Analysis and Design, McGraw Hill*