

# Analog and Digital Systems (UEE505)

## Lecture # 16 Code Converters



THAPAR INSTITUTE  
OF ENGINEERING & TECHNOLOGY  
(Deemed to be University)

Deptt. Of Electrical & Instrumentation Engineering  
Thapar Institute of Engineering & Technology Patiala, India

# Code Converters

- A conversion circuit must be inserted between the two systems if each uses different codes for the same information.
- Logic circuit whose inputs are bit patterns representing numbers(or characters) in one code and whose outputs are the corresponding representations in different code.
- Changes data presented in one type of binary code to another code of binary code
- These are usually multiple output circuits.

# Code Converters

- The following are some of the most commonly used code converters:
  - i. Binary-to-BCD
  - ii. BCD-to-Excess-3
  - iii. Excess-3-to-BCD
  - iv. Binary-to-Gray code
  - v. Gray-to-Binary code
  - vi. BCD-to-binary

**Note:** Be careful to determine the input combinations if any, those will never occur and consider that as don't cares.

# 4 bit Binary to BCD Code Converter

## Truth Table:

Decimal	Binary Code				BCD Code				
	D	C	B	A	B <sub>4</sub>	B <sub>3</sub>	B <sub>2</sub>	B <sub>1</sub>	B <sub>0</sub>
0	0	0	0	0	0	0	0	0	0
1	0	0	0	1	0	0	0	0	1
2	0	0	1	0	0	0	0	1	0
3	0	0	1	1	0	0	0	1	1
4	0	1	0	0	0	0	1	0	0
5	0	1	0	1	0	0	1	0	1
6	0	1	1	0	0	0	1	1	0
7	0	1	1	1	0	0	1	1	1
8	1	0	0	0	0	1	0	0	0
9	1	0	0	1	0	1	0	0	1
10	1	0	1	0	1	0	0	0	0
11	1	0	1	1	1	0	0	0	1
12	1	1	0	0	1	0	0	1	0
13	1	1	0	1	1	0	0	1	1
14	1	1	1	0	1	0	1	0	0
15	1	1	1	1	1	0	1	0	1

- $B_0 = \sum m(1, 3, 5, 7, 9, 11, 13, 15)$
- $B_1 = \sum m(2, 3, 6, 7, 12, 13)$
- $B_2 = \sum m(4, 5, 6, 7, 14, 15)$
- $B_3 = \sum m(8, 9)$
- $B_4 = \sum m(10, 11, 12, 13, 14, 15)$

For B<sub>0</sub>

DC \ BA	00	01	11	10
00	0	1	1	0
01	0	1	1	0
11	0	1	1	0
10	0	1	1	0


$B_0 = A$

# 4 bit Binary to BCD Code Converter

❖ Using K-map, the logical expression can be obtained as:

- $B_0 = A$
- $B_1 = DCB' + D'B$
- $B_2 = D'C + CB$
- $B_3 = DC'B'$
- $B_4 = DC + DB$

# Logic Diagram

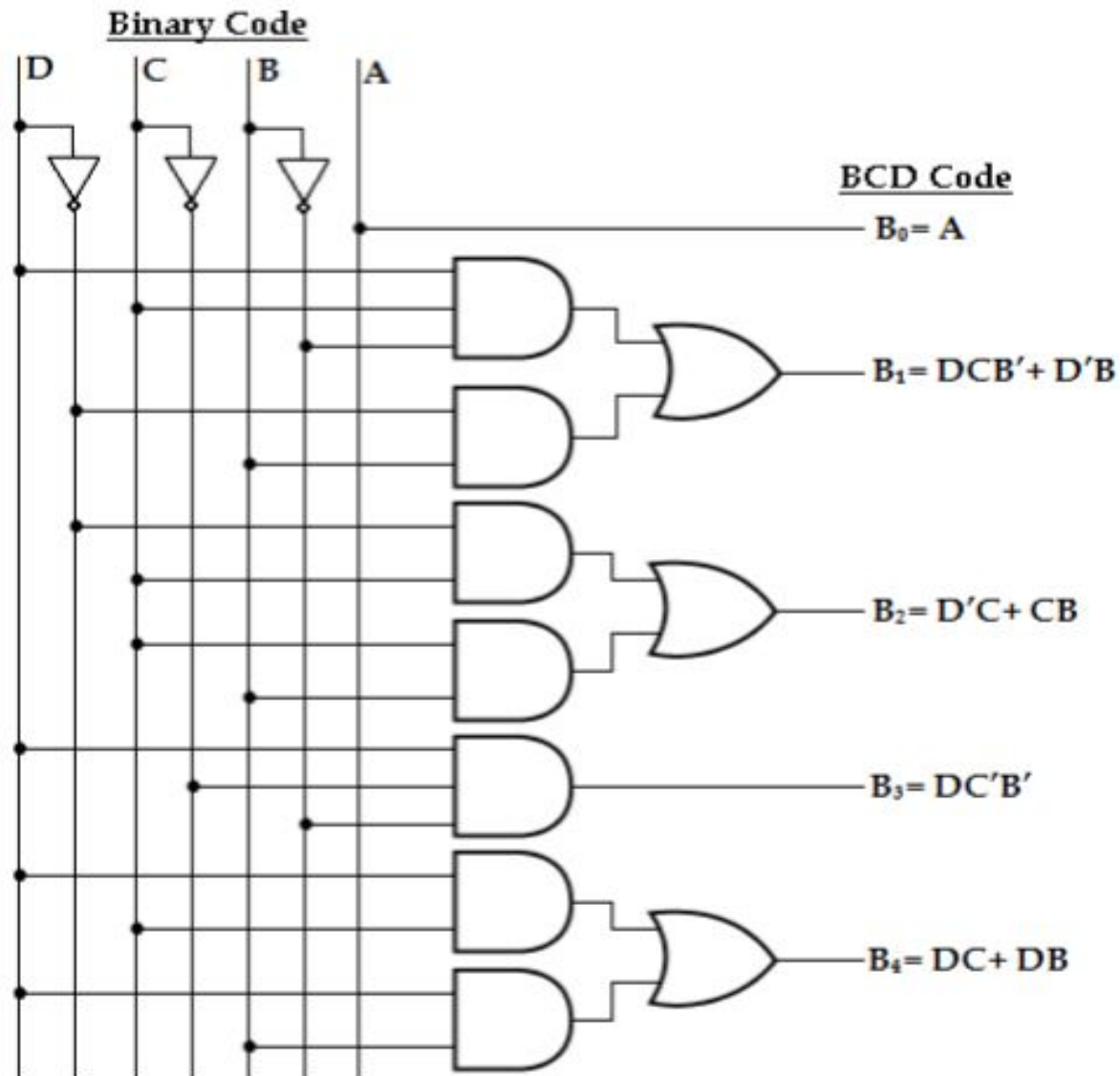

Design 4 bit BCD to Excess 3 code converter.

# References

- ❖ *Floyd, T.L. and Jain, R. P., Digital Fundamentals, Pearson Education.*
- ❖ *Tocci, R. and Widmer, N., Digital Systems: Principles and Applications, Pearson Education.*
- ❖ *Mano, M. M. and Ciletti, M., Digital Design, Pearson Education.*
- ❖ *Kumar, A., Fundamentals of Digital Circuits, Prentice Hall.*