

Analog Electronic Circuits (UEC301)

By



Dr. Mayank Kumar Rai
Associate Professor,
ECED, TIET, Patiala

Thapar Institute of Engineering & Technology
(Deemed to be University)
Bhadson Road, Patiala, Punjab, Pin-147004
Contact No. : +91-175-2393201
Email : info@thapar.edu

ti
THAPAR INSTITUTE
OF ENGINEERING & TECHNOLOGY
(Deemed to be University)

Subject: Analog Electronic Circuits (UEC301)

Faculty names: (1) Dr. Mayank Kumar Rai (Associate Professor & Course Coordinator)

(Topic of today's Lecture : Multistage Transistor Amplifiers)

Key points

- ✓ **Multistage Transistor Amplifier**
- ✓ **Purpose of coupling device**
- ✓ **Types of Coupling**
- ✓ **Important Terms**(Gain, frequency response and bandwidth)
- ✓ **R-C Coupled Amplifier**

Contents of this lecture are based on the following books:

- *Jacob Milman & and C.C.Halkias, “Integrated Electronics Analog and Digital Circuit and Systems”Second Edition.*
- *Adel S. Sedra & K. C. Smith, “MicroElectronic Circuits Theory and Application” Fifth Edition.*
- *Robert L. Boylestad & L. Nashelsky, “Electronic Devices and Circuit Theory” Eleventh Edition.*



Multistage Transistor Amplifier

➤ *A transistor circuit containing more than one stage of amplification is known as multi-stage transistor amplifier.*

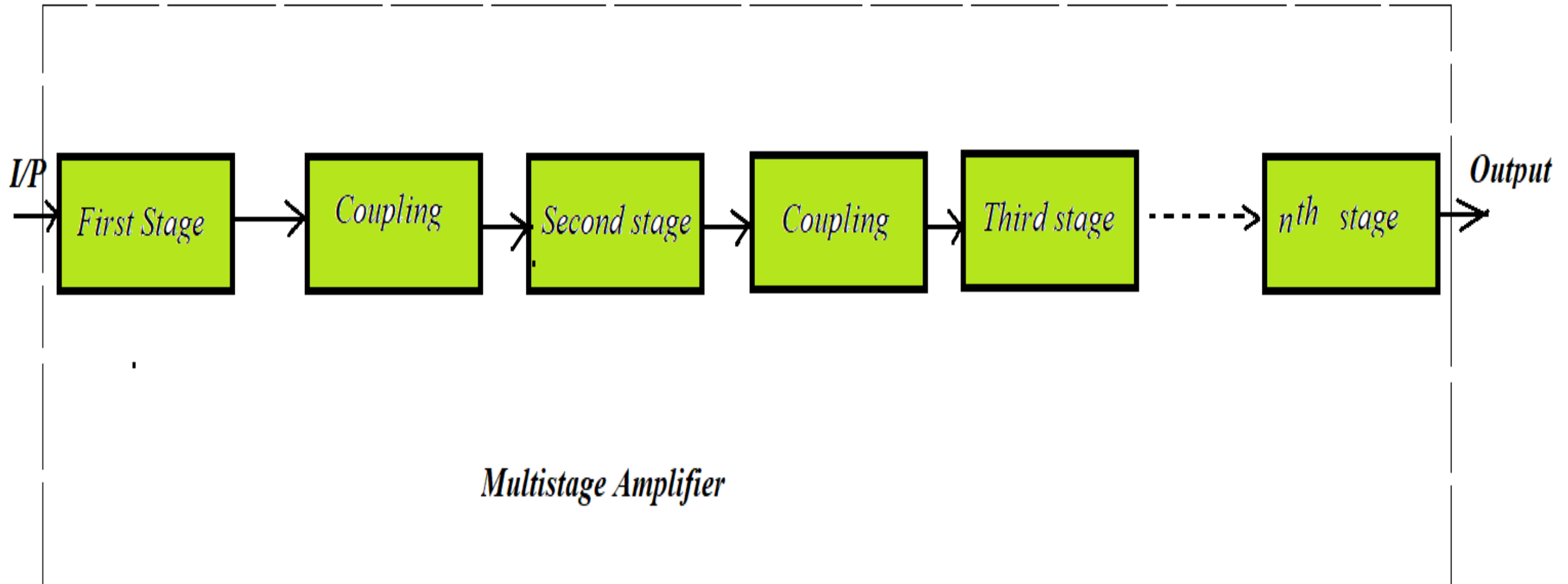


Figure 1: Multistage Amplifier.

Purpose of coupling device

- i. Transfer a.c. Output of one stage to the input of the next stage.*
- ii. Isolate the d.c. Conditions of one stage from the next stage.*

Types of Coupling

- i. R-C coupling*
- ii. Transformer coupling*
- iii. Direct Coupling*

Important Terms

- i. *Gain*
- ii. *Frequency response*
- iii. *Band width*

i. **Gain** The ratio of the output to the input one of the amplifier is called gain.

$$A_V = A_{v1} \cdot A_{v2} \cdot A_{v3} \cdot A_{v4} \dots A_{vn}$$

If v_{in} is the input of first stage then

Output of first stage = $A_{v1} v_{in}$

Output of second stage = $(A_{v1} v_{in}) \cdot A_{v2}$

Output of third stage = $(A_{v1} \cdot A_{v2} \cdot v_{in}) A_{v3}$

Output of n^{th} stage = $(A_{v1} \cdot A_{v2} \cdot A_{v3} \dots A_{v(n-1)}) v_{in}$



ii. Frequency response:

The curves between voltage gain and the signal frequency of an amplifier is known as frequency response.

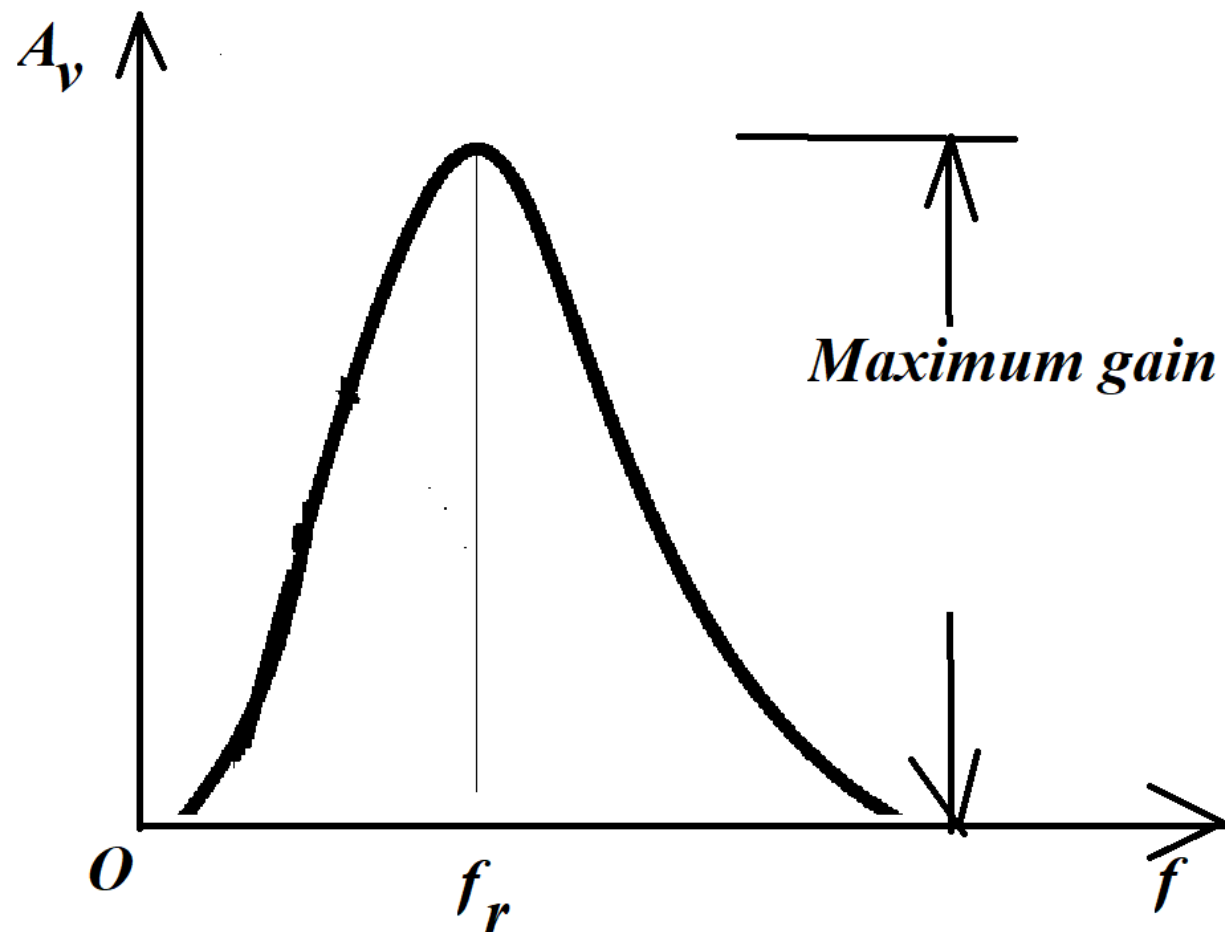


Figure 2: Frequency response.

iii. Band width:

The range of frequency over which the gain is equal to or greater than 70.7% of the maximum gain is known as band width.

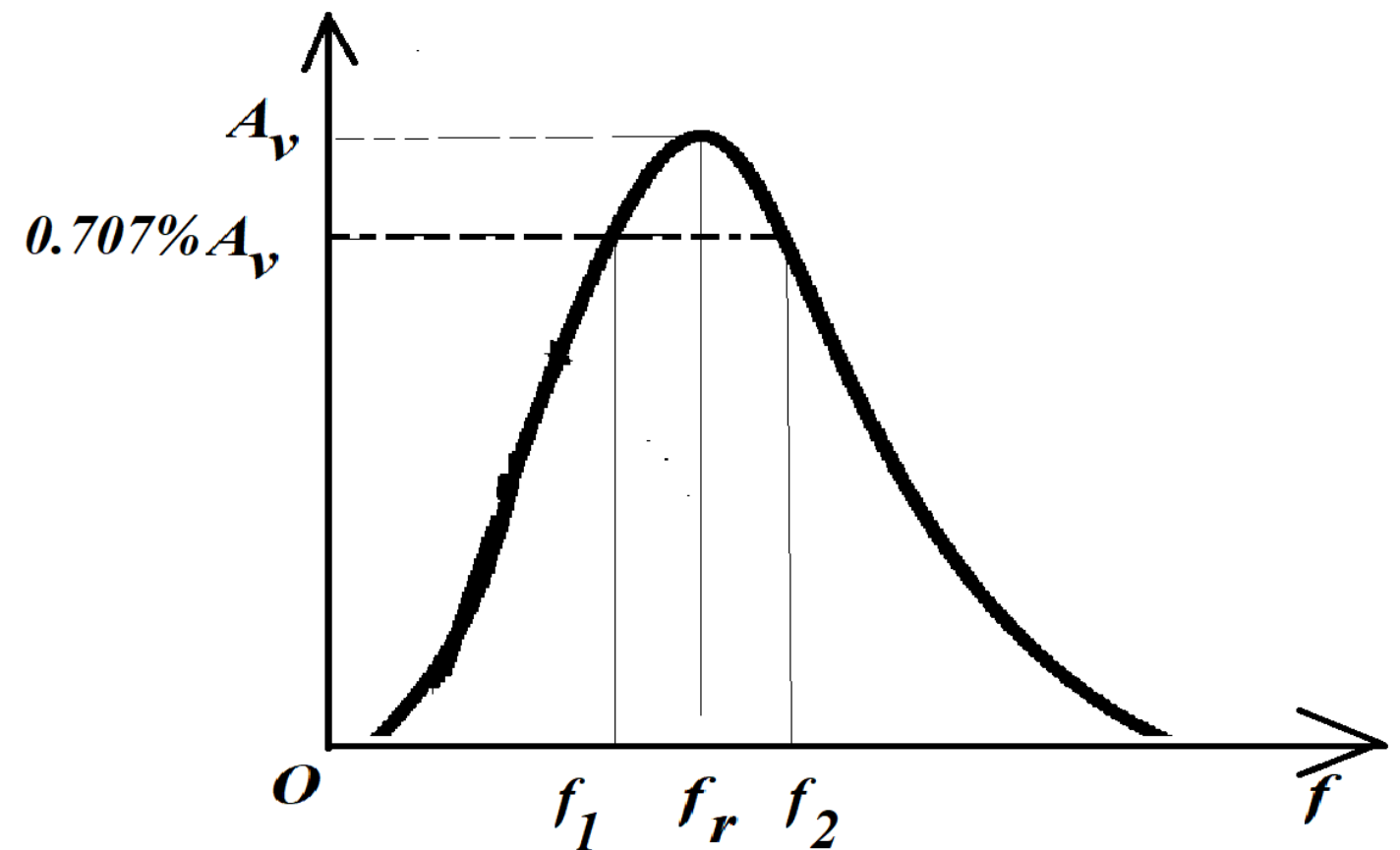


Figure 3: Bandwidth.

R-C Coupled Amplifier

Circuit Details:

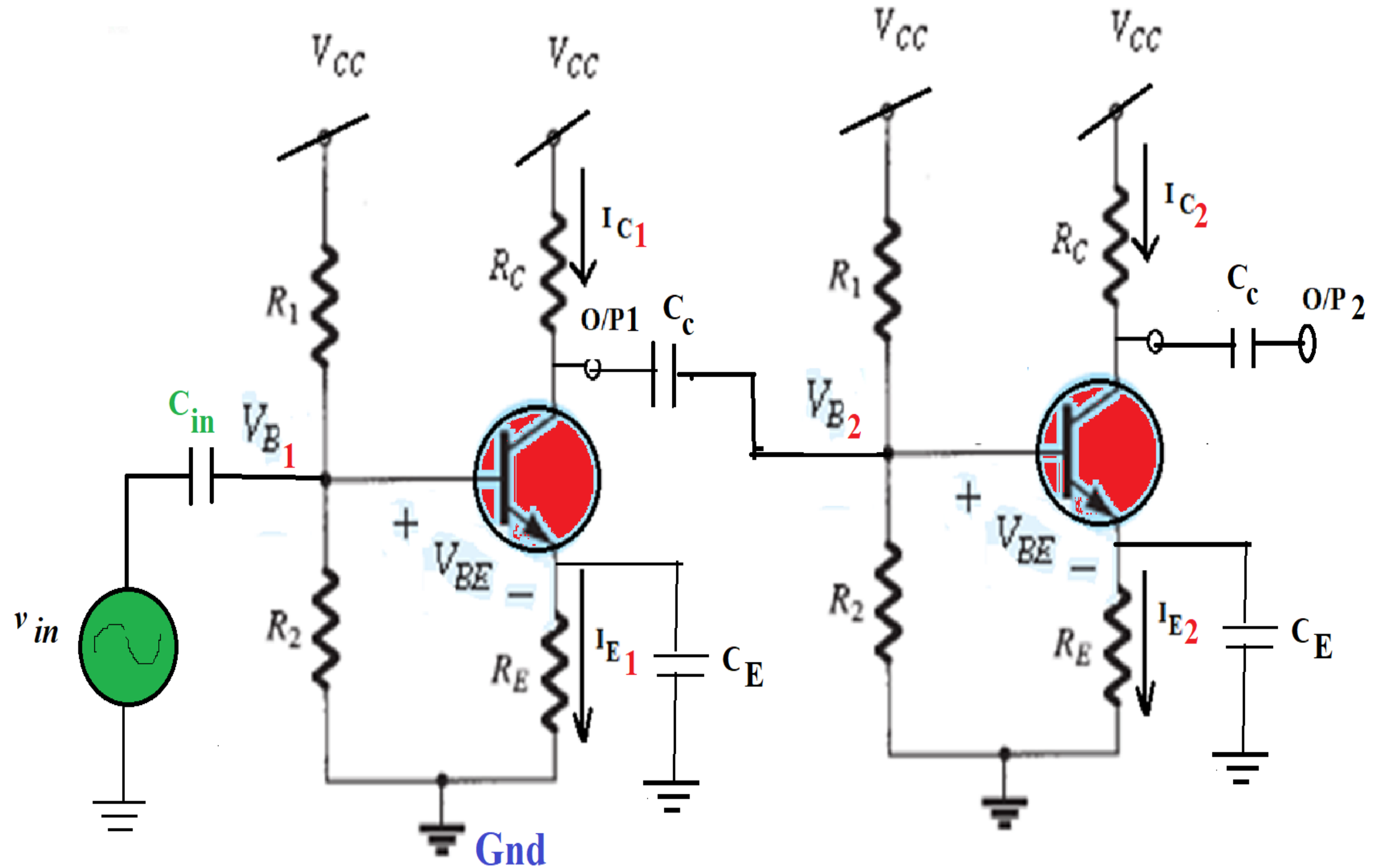


Figure 4: R-C coupled transistor Amplifier.

Operation

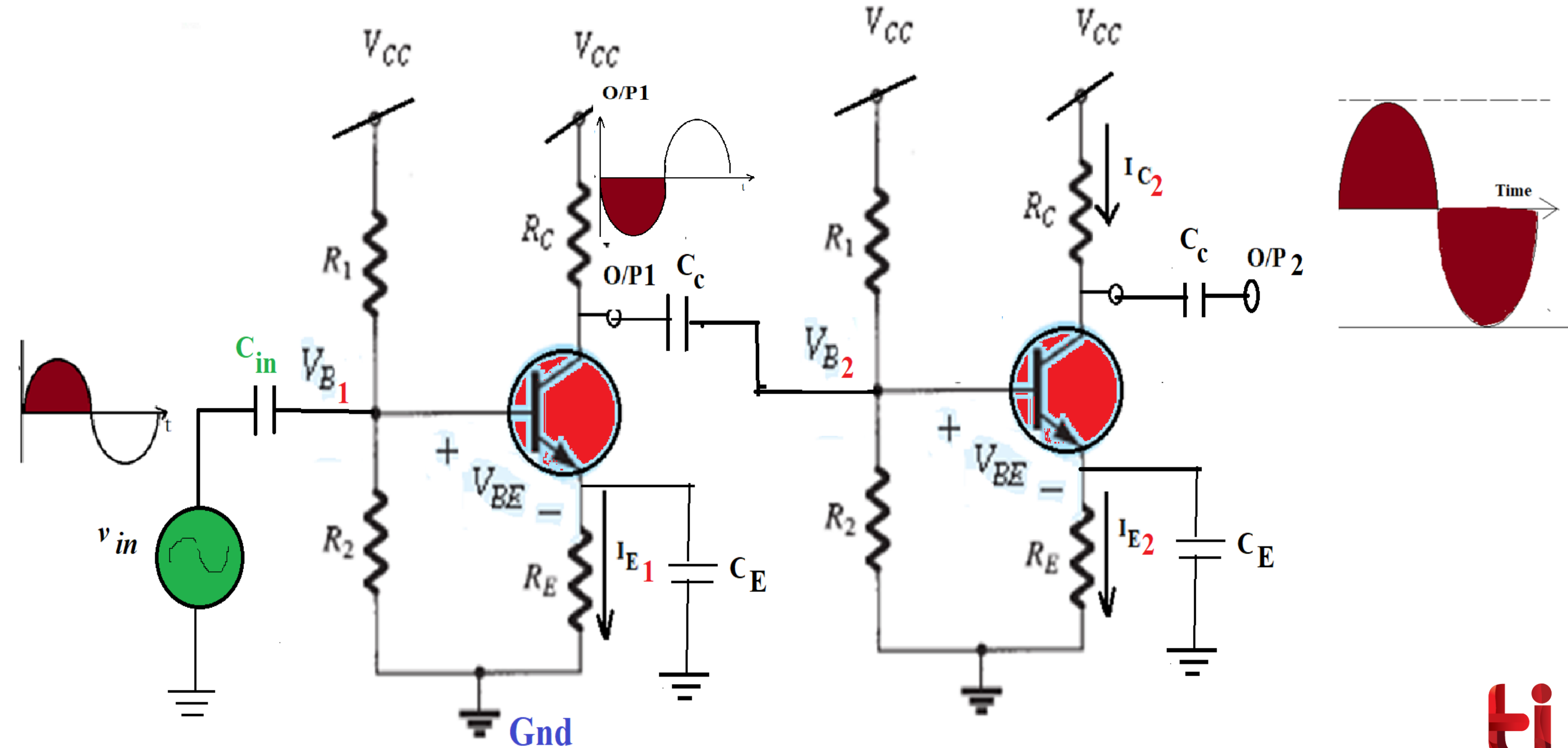



Figure 5: R-C coupled transistor Amplifier with input and output.



Frequency Response:

- At low frequencies(<f₁)

X_{Cc} ↑  very small part of signal will pass from one stage to the next stage.

- At high frequencies(>f₂)

X_{Cc} ↓  it behaves as a short circuit

X_{BE} ↓  I_B ↑  β ↓

- At mid frequencies(f₁- f₂)

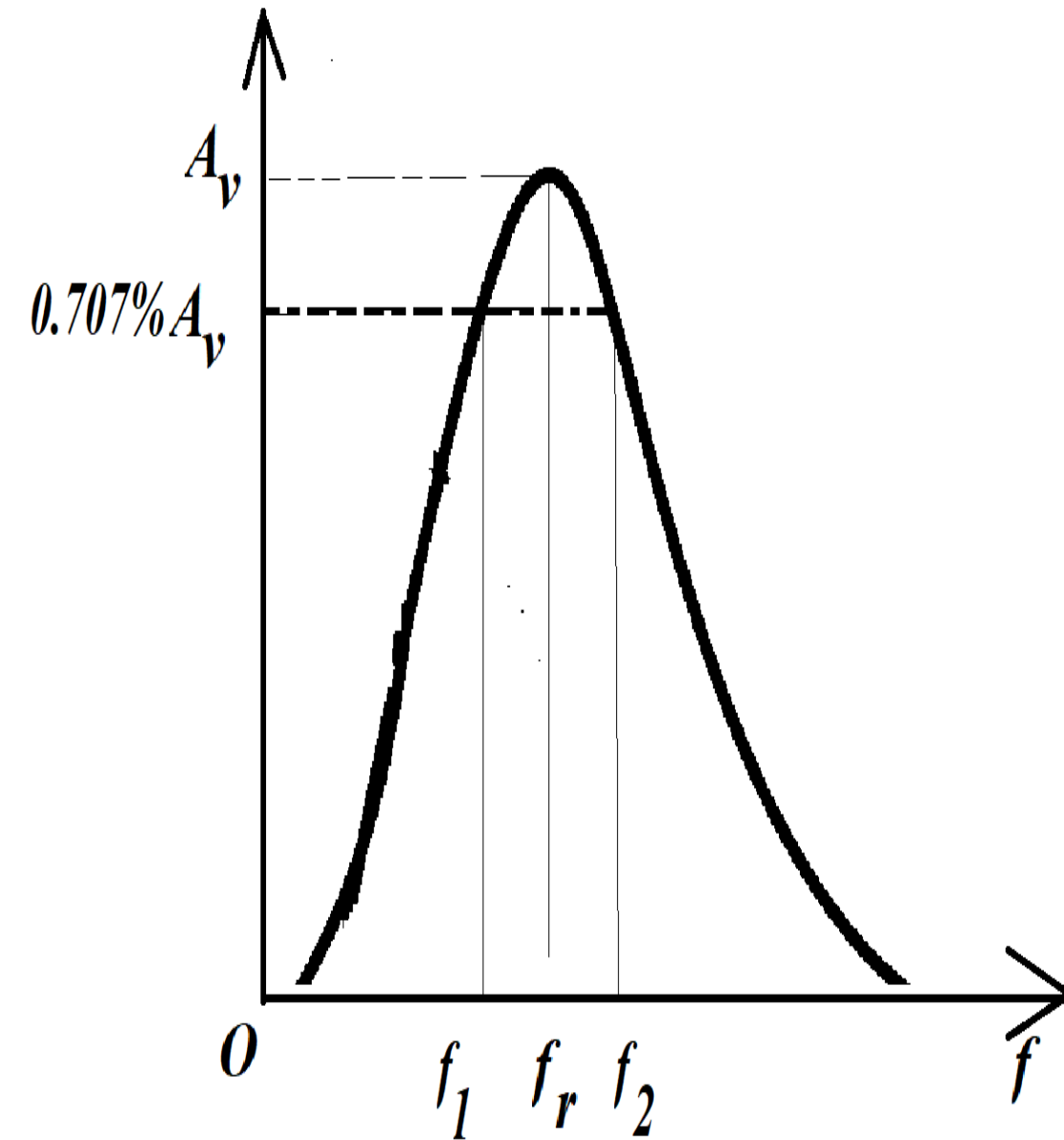


Figure 6: Frequency response of R-C coupled Amplifier.

Low frequency analysis of R-C Coupled Amplifier

$$A_v = A_1 * A_2 \rightarrow (1)$$


$$A_1 = A_{v1} = \frac{v_{o1}}{v_{in}}$$

$$A_2 = A_{v2} = \frac{v_o}{v_{in2}} = \frac{v_o}{v_{o1}}$$


$$A_v = \frac{v_{o1}}{v_{in}} \times \frac{v_o}{v_{o1}}$$

$$A_v = \frac{v_o}{v_{in}}$$
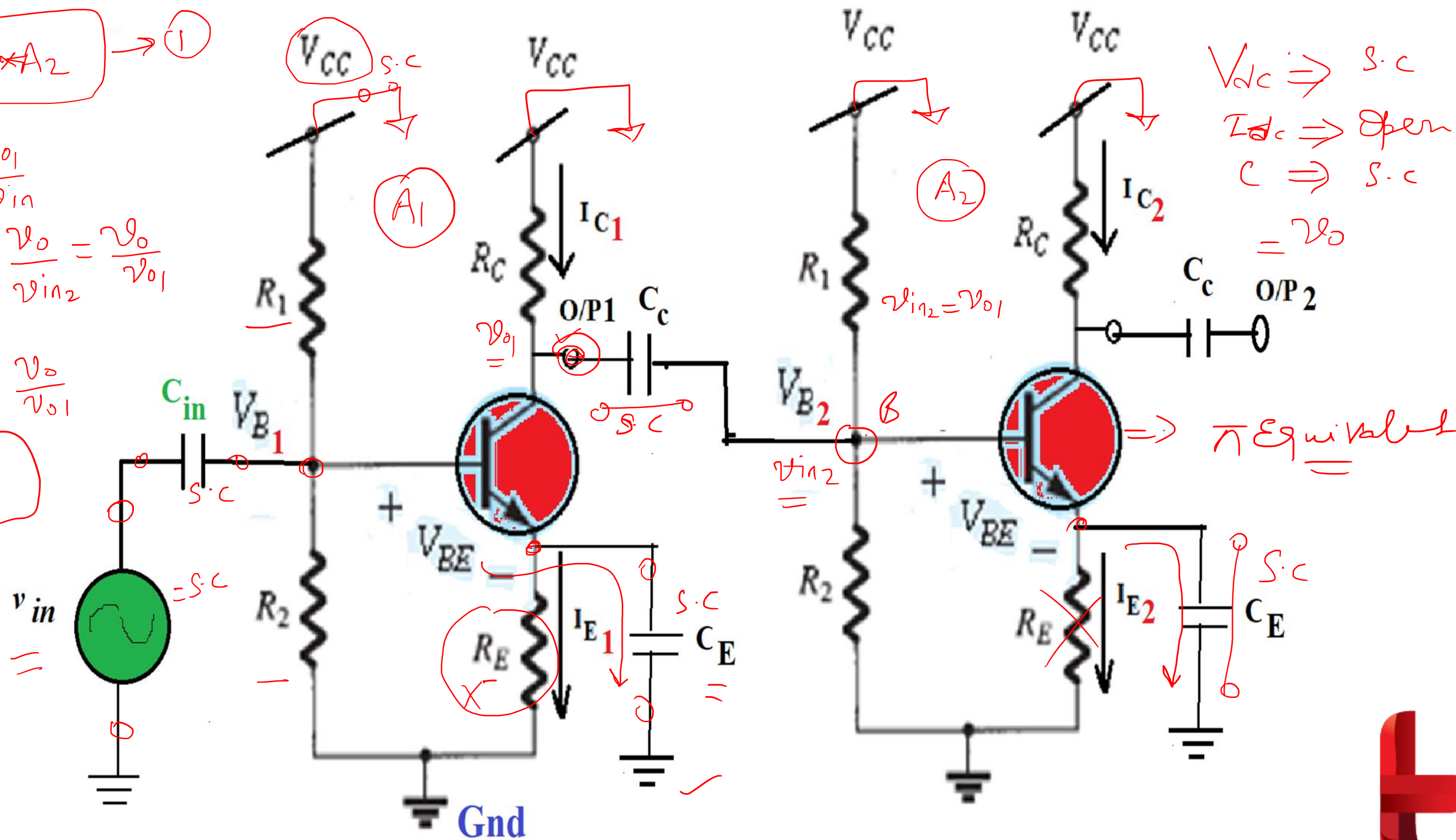
$$v_{in} = v_{in} + v_{in} \Rightarrow s.c$$



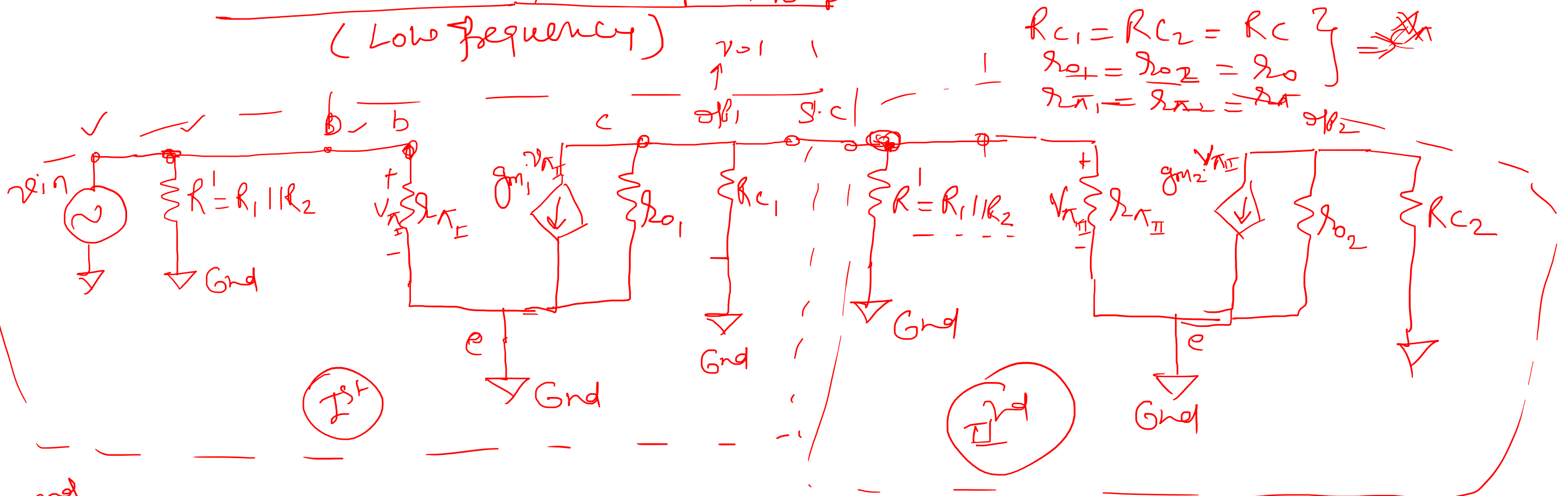Small Signal Model of RC Coupled amp (Low frequency)



IId

$$A_{v2} = -g_{m2} R_{o2} \Rightarrow R_{o2} = r_{o2} || R_{C2} \approx R_{C2} \quad \left. \begin{array}{l} v_{o2} = -g_{m2} v_{\pi} R_{o2}, v_{\pi} = v_{o1} \\ \frac{v_{o2}}{v_{o1}} = A_{v2} = -g_{m2} R_{o2} \approx -g_{m2} R_{C2} \end{array} \right\}$$

$$\boxed{A_{v2} \approx -g_{m2} R_{C2}} \rightarrow (1)$$

I^{st}

$$v_{o1} = -g_{m1} v_{\pi 1} R_{o1} \Rightarrow R_{o1} = r_{o1} || R_{C1} || R'$$

$$v_{\pi 1} = v_{in} \Rightarrow v_{o1} = -g_{m1} v_{in} R_{o1} \Rightarrow \boxed{\frac{v_{o1}}{v_{in}} = -g_{m1} R_{o1} = A_{v1}} \rightarrow (11)$$

$$A_{re} = A_v = A_{v1} \cdot A_{v2}$$

$$= -g_{m1} R_{o1} \{-g_{m2} \cdot R_{o2}\}$$

$$\left. \begin{aligned} R_{c1} &= R_{c2} = R_C \\ R_{o1} &= R_{o2} = R_o \end{aligned} \right\}$$


$$A_v = g_{m1} \cdot g_{m2} \cdot R_{o1} \cdot R_{o2}$$

$$A_{re} = +g_{m1} \cdot g_{m2} \cdot \{R_{o1} \parallel R_{c1} \parallel R'\} \cdot \{R_{c2}\}$$

\Rightarrow

\rightarrow +ve

in

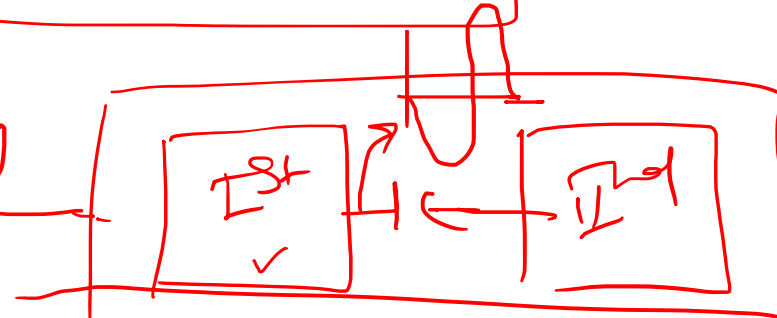

o/p $\underline{V_{GS}} = \underline{0}$ pleas shift

$R' =$ o/p back resistance at IInd stage output

R_C coupled

$$= R_1 \parallel R_2 = \frac{R_1 \cdot R_2}{R_1 + R_2}$$

Advantages:

- It has excellent frequency response.
- It has lower cost.

Disadvantages:

- The R-C coupled amplifiers have low voltage and power gain.
- Impedance matching is poor.



Thank You

