

Roll No. _____

Thapar University, Patiala
Electrical & Instrumentation Engineering Department

B.E. Third Year (ELE)

Dec. 10, 2016

End Semester Test

UEE503: NETWORK ANALYSIS AND SYNTHESIS

Time: 3.00 hrs. ; M.M.: 100

Name of Faculty: NN, GRB

Note: (i) Attempt all questions in a given sequence only.
(ii) Assume suitable data if found missing.

- Q.1: (a) Verify the reciprocity theorem for the network shown in Fig. 1, (8)
by considering the current passes through $10\ \Omega$ resistance.

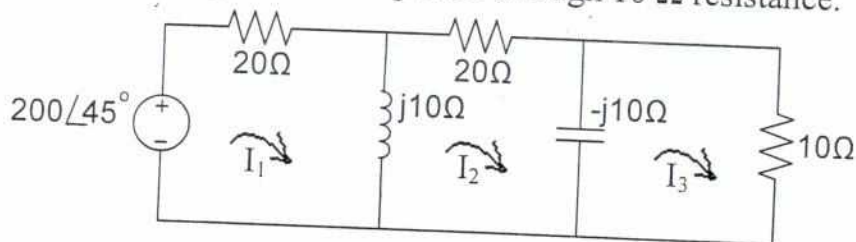


Fig. 1

- (b) Verify Tellegen's theorem for the network shown in Fig. 2, (8)
where the branch voltages and current have the following
values:

$$v_0 = 20, v_1 = 16, v_2 = 2, v_3 = 4, v_4 = 14, v_5 = 6 \quad (\text{in volts})$$
$$i_0 = -16, i_1 = 12, i_2 = 2, i_3 = 14, i_4 = 4, i_5 = 2 \quad (\text{in amperes})$$

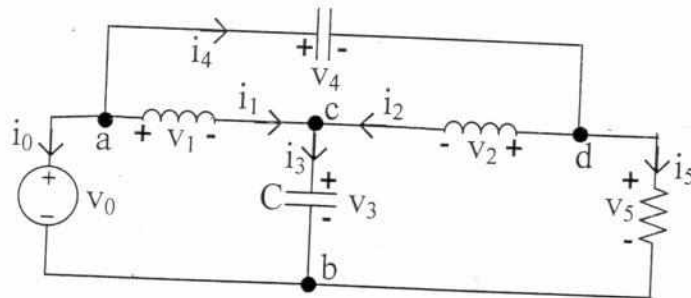


Fig. 2

- Q.2: (a) The circuit shown in Fig. 3 is two-stage transistor amplifier. (10)
The Z-parameters for each stages,

$$Z_1 = \begin{bmatrix} 350 & 2.667 \\ -10^6 & 6667 \end{bmatrix} \quad Z_2 = \begin{bmatrix} 1.0262 \times 10^6 & 6,790.8 \\ 1.0258 \times 10^6 & 6,793.5 \end{bmatrix}$$

- Determine I. Input Impedance
II. Overall Voltage Gain

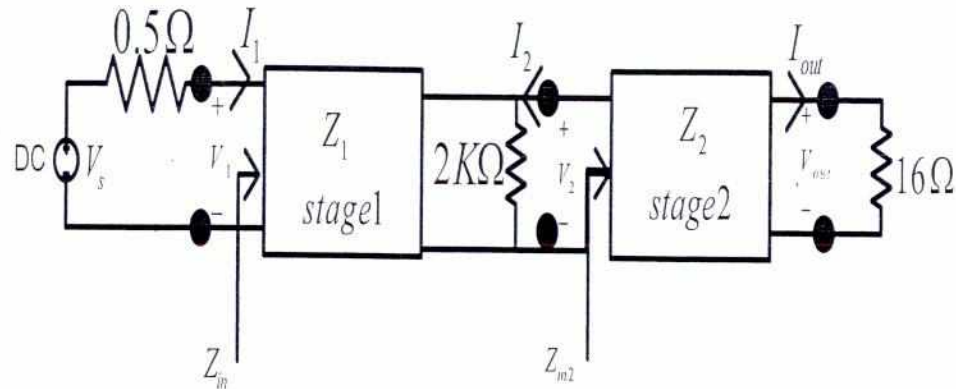


Fig. 3

- (b) Derive the condition for the network to be reciprocal. Use z- (4)
parameters or Transmission parameters.
- (c) A two port network is tested to determine the short-circuit (4)
parameters. The table below shows the recorded measurements.
Notations of the currents and voltages are as per standard
convention followed for a Y-parameters network.

S. No.	Port 1-1'		Port 2-2'	
	Voltage (V)	Current (mA)	Voltage (V)	Current (mA)
1	30	120	0	- 30
2	0	- 30	40	160

Determine the short-circuit parameters and draw the equivalent circuit of the two-port network.

- Q.3(a):** The circuit shown in Fig. 4 contains dependent sources. Calculate (10)
its voltage gains.

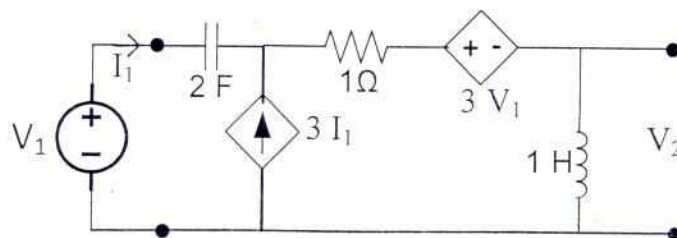


Fig. 4

- 3(b):** For the given network as shown in Fig. 5, (10)
(i) Show that the input impedance at port-1 is 1-ohm with port-2
open.
(ii) Find $V_2(s)/V_1(s)$?
All the elements of the circuit follow conventional units.

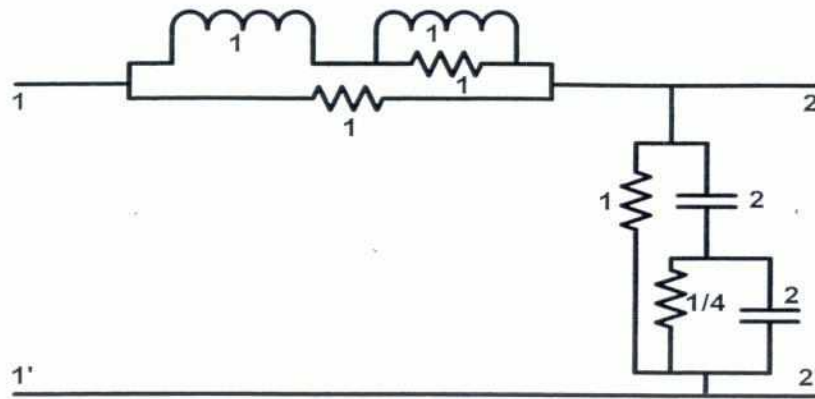


Fig. 5

Q.4(a): An inductor L in series with a resistor R of $9\text{-}\Omega$ resistance is connected in parallel to a capacitor C . The driving point impedance of the parallel combination has a zero at $s = -3$ and two poles at $s = -1.5 \pm \frac{j1}{2}\sqrt{111}$. Calculate the value of L and C . (8)

4(b): Show that $\frac{I_2(s)}{V_1(s)} = \frac{K(s+1)}{(s+2)(s+4)}$ and find the value of 'K' in the given expression for the network shown in Fig. 6. (10)

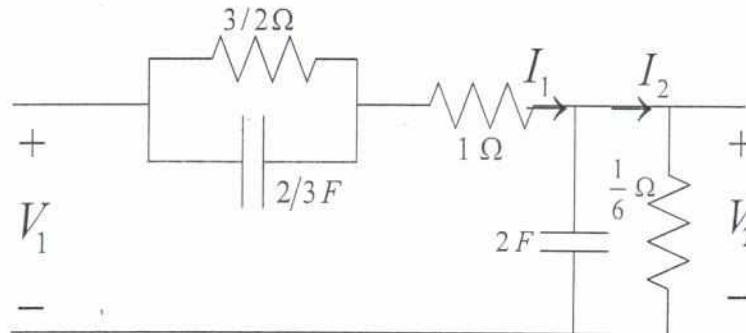


Fig. 6

Q.5(a): (i) Check whether the impedance function, $Z(s)$ is of LC/RL/RC type or not? (4)

$$Z(s) = \frac{s^4 + 8s^2 + 15}{s^5 + 10s^3 + 24s}$$

(ii) State the necessary and sufficient conditions for the function to be positive real (PR) function. (4)

5(b): Synthesize the given admittance function using following methods: (5 + 5)

$$Y(s) = \frac{s^2 + 5s + 4}{2s^2 + 14s + 20}$$

- (i) Foster Form - I
- (ii) Foster Form - II

5(c): Synthesize the given impedance function using following methods: (5 + 5)

$$Z(s) = \frac{s(s+4)(s+8)}{(s+2)(s+6)}$$

(i) Cauer Form – I

(ii) Cauer Form – II

NOTE: Your answer sheets will be shown on the day Tuesday, dated: 13th of December, 2016. You are advised to visit group wise as per schedule:

- Group 1 – 3: 12:30 PM to 01:30 PM
- Group 4 – 6: 01:30 PM to 2:30 PM