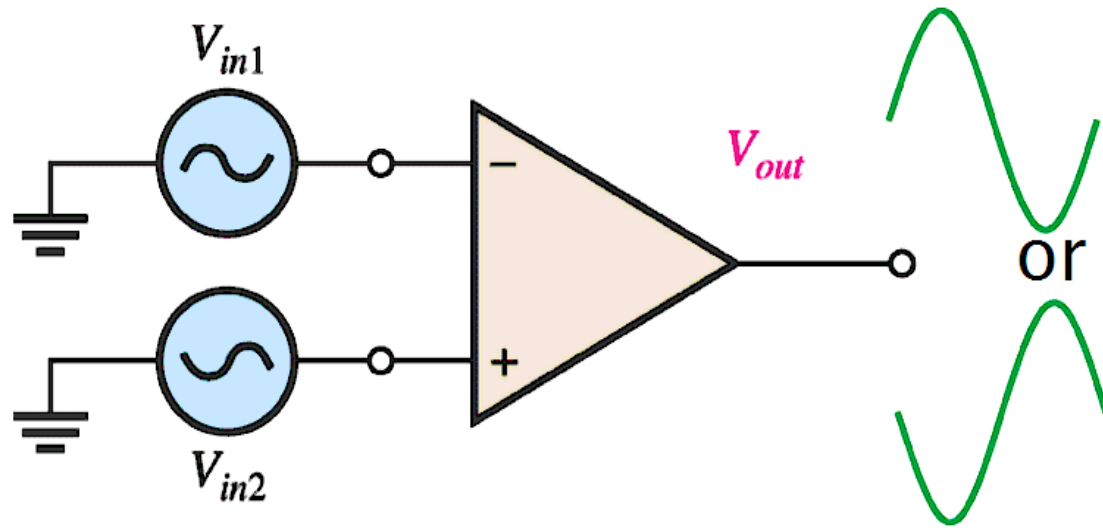


OP AMP Characteristics


Op-Amp Differential Mode



$$V_{out} = A_d V_d$$
$$V_d = V_{in1} - V_{in2}$$

In this mode two out-of-phase signals are applied with the difference of the two amplified is produced at the output.

The Op-Amp Transfer Curve

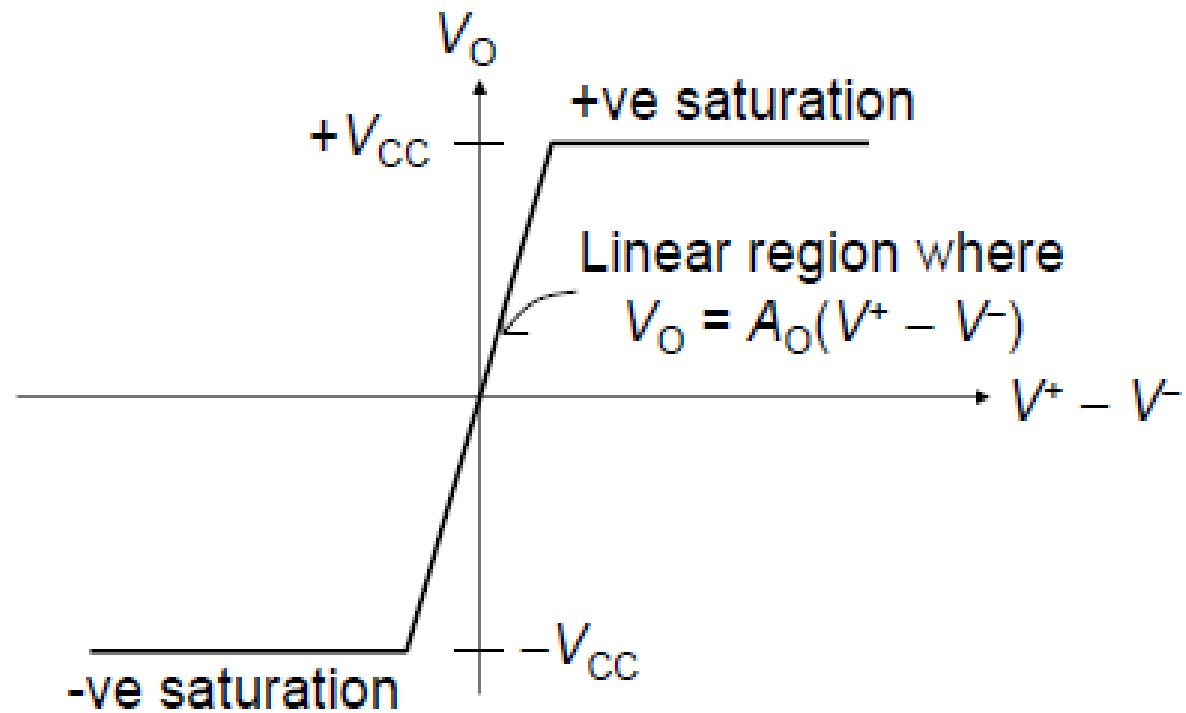

Op-Amp Specifications


DC Offset Parameters

Even when the input voltage is zero, there will be an output called **offset**.

1. Input Offset Voltage


- Ideally, output of an op-amp is 0 Volt if the input is 0 Volt.
- Realistically, a small dc voltage will appear at the output when no input voltage is applied.
- Thus, differential dc voltage is required between the inputs to force the output to zero volts.
- This is called the Input Offset Voltage, V_{os} . Range between 2 mV or less.
- However, due to manufacturing process, the differential input transistors of real op-amps may not be exactly matched.
- This causes the output to be zero at a non-zero value of differential input, called the input offset voltage.
- This can be reduced to several microvolts if nulled using the IC's offset null pins or using higher-quality or laser-trimmed devices.
- However, the input offset voltage value may drift with temperature or age.

2. Input Impedance

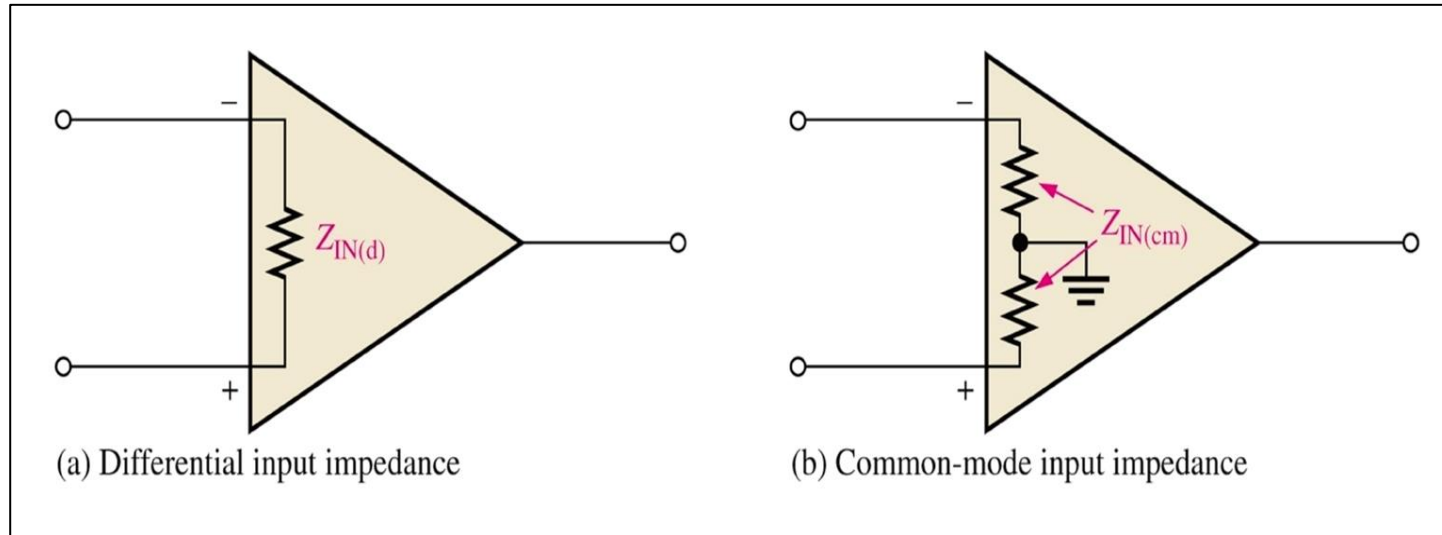

- It is the total resistance between the inverting and non-inverting inputs.
- Differential input impedance : total resistance between the inverting and non-inverting inputs
- Common-mode input impedance: total resistance between each input and ground

3. Input Offset Current

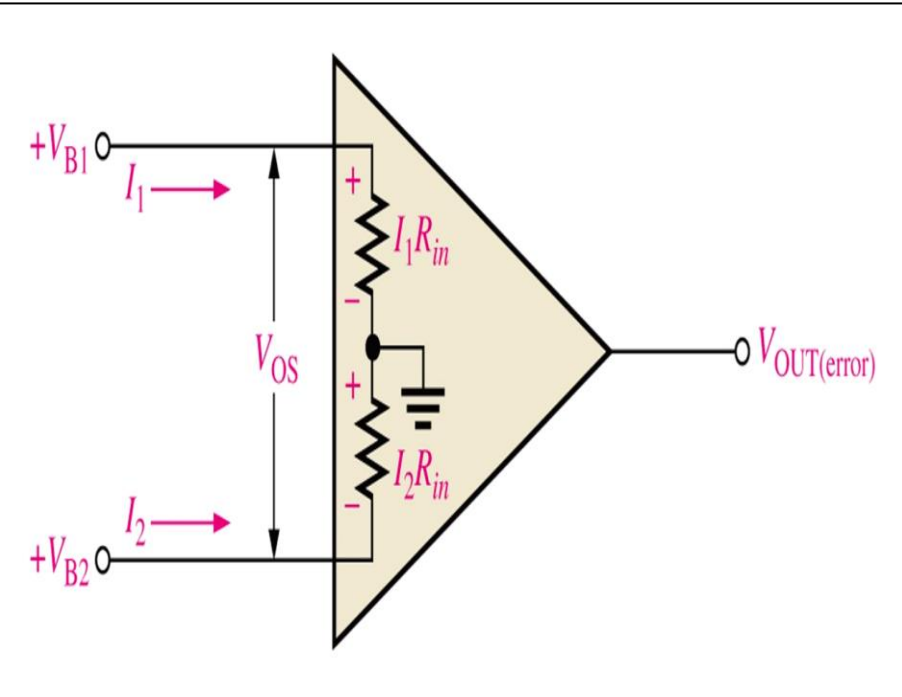

Input Offset Current

It is the difference of input bias currents.

Input offset current

$$I_{os} = |I_1 - I_2|$$

Thus, error


$$V_{out(error)} = A_v I_{os} R_{in}$$

Offset voltage

$$V_{os} = I_1 R_{in} - I_2 R_{in} = (I_1 - I_2) R_{in}$$


$$V_{os} = I_{os} R_{in}$$

Input Bias Current

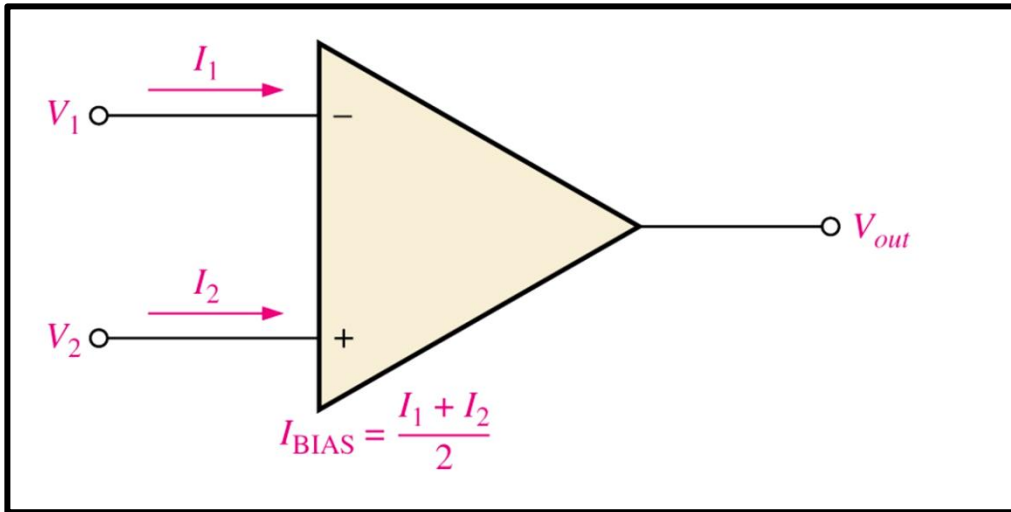

- Ideally should be zero
- The current required by the inputs of the amplifier to properly operate the first stage.
- Is the average of both input currents

Output Impedance

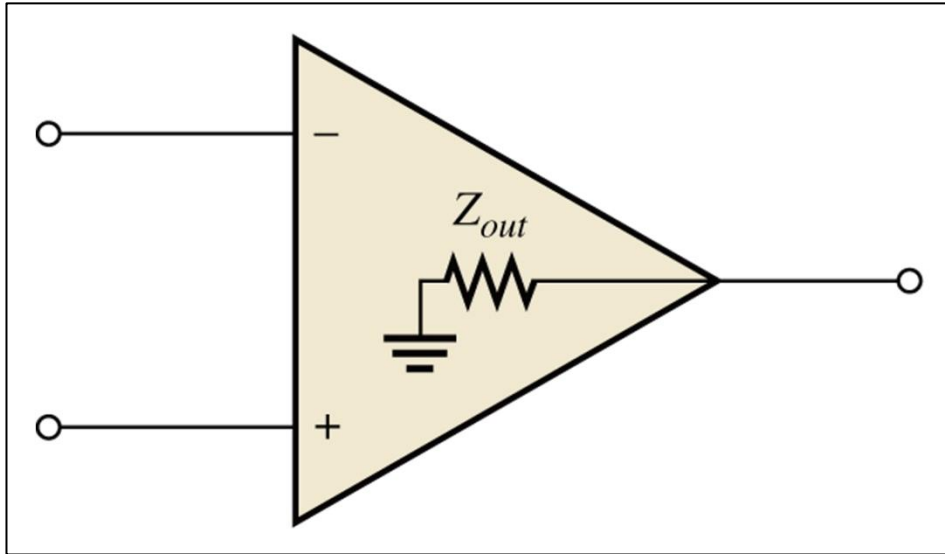

- Ideally should be zero
- Is the resistance viewed from the output terminal of the op-amp.
- In reality, it is non-zero.

Common-Mode Rejection Ratio (CMRR)

One rating worth mentioning that is unique to op-amps is CMRR or **common-mode rejection ratio**.

Because the op-amp has two inputs that are opposite in phase (inverting input and the non-inverting input) any signal that is common to both inputs will be cancelled.

A measure of the ability to cancel out common signals is called CMRR.

- The higher the CMRR, the better, in which the open-loop gain is high and common-mode gain is low.
- CMRR is usually expressed in dB & decreases with frequency

$$CMRR = \frac{A_{ol}}{A_{cm}}$$


$$CMRR = 20 \log \left(\frac{A_{ol}}{A_{cm}} \right)$$

OP AMP Frequency Characteristics

An op-amp is a wide-bandwidth amplifier.

The following affect the bandwidth of the op-amp:

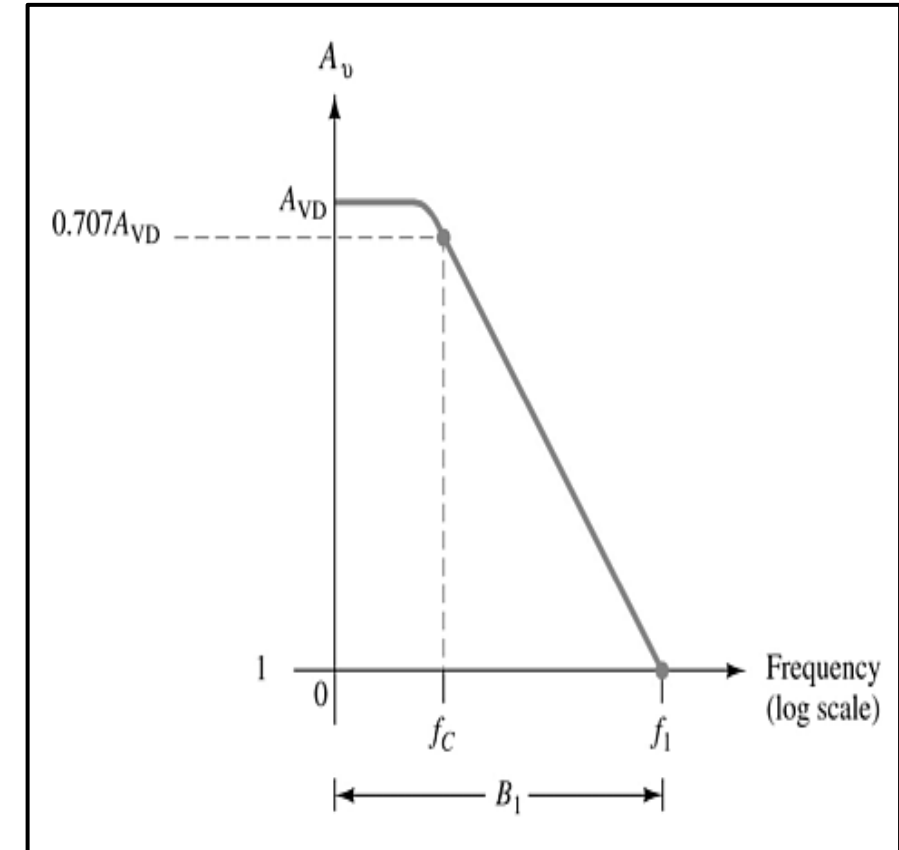- Gain
- Slew rate
- The op-amp's high frequency response is limited by internal circuitry.
- The plot is for an open loop gain (A_{OL} or A_{VD}).
- This means that the op-amp is operating at the highest possible gain with no feedback resistor.
- In the open loop, the op-amp has a narrow bandwidth.
- The bandwidth widens in closed loop operation, but the gain is lower.




Slew Rate



- It is the maximum rate at which an op-amp can change output without distortion.
- Slew Rate is independent of the closed-loop gain of the op-amp.
- It's a measure of how fast the output can “**follow**” the input signal.
- The SR rating is given in the specification sheets **V/s** as **V/μs**.

$$SlewRate = \frac{\Delta V_{out}}{\Delta t}$$
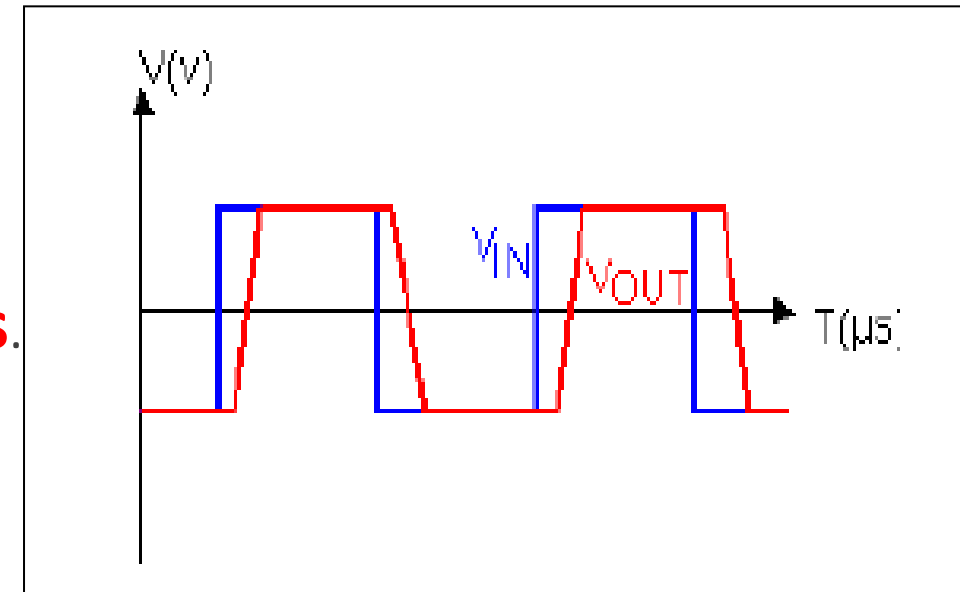
$$\text{where } \Delta V_{out} = +V_{max} - (-V_{max})$$



Contd..

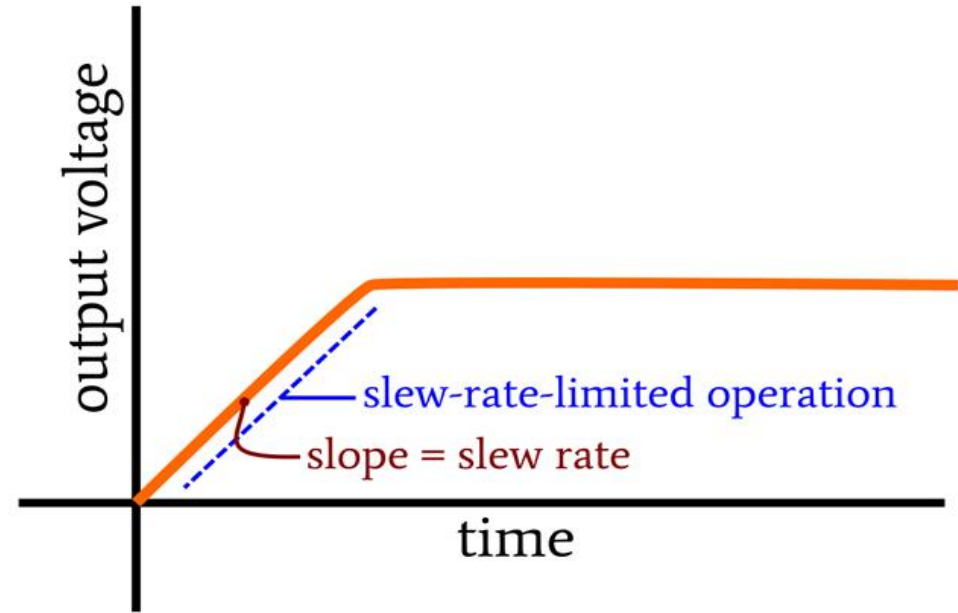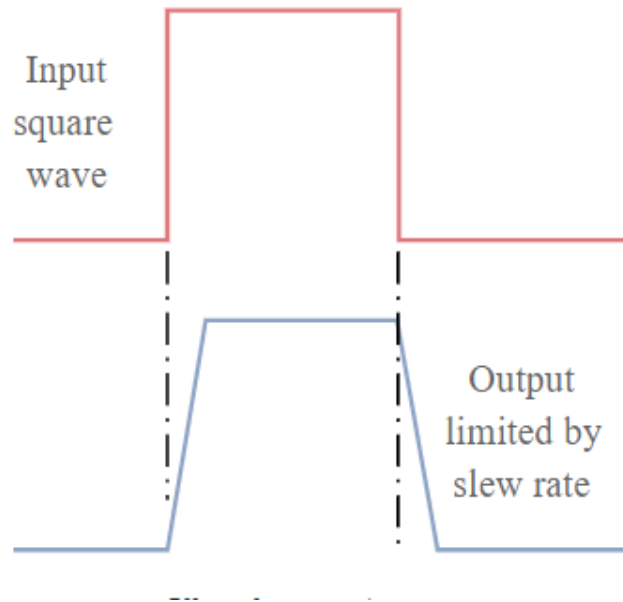


Maximum Signal Frequency

The slew rate determines the highest frequency of the op-amp without distortion.

$$f \leq \frac{SR}{2\pi V_p}$$

An op-amp has $SR = 0.60\text{V}/\mu\text{s}$ and a supply voltage $\pm 15\text{V}$. What is the maximum frequency before distortion occur?

Determine the Slew rate?

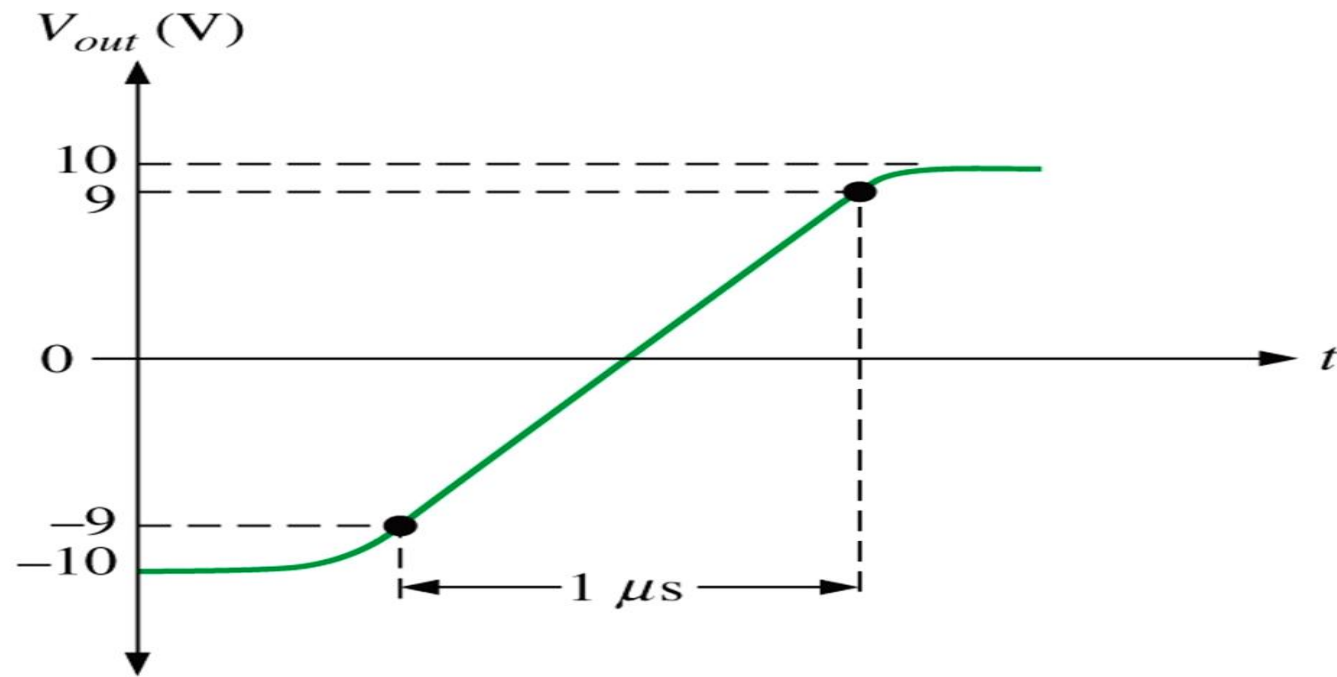

$$f \leq \frac{SR}{2\pi V_p}$$

Slew Rate of Common OP AMPS

Op amp	Slew Rate (typ)
OPA369	0.005 V/ μ s
OPA333	0.16 V/ μ s
OPA277	0.8 V/ μ s
OPA129	2.5 V/ μ s
OPA350	22 V/ μ s
OPA211	27 V/ μ s
OPA827	28 V/ μ s
OPA835	110 V/ μ s
OPA847	850 V/ μ s

References

- ❖ *Coughlin, R.F., Operational Amplifiers and Linear Integrated Circuits, Pearson Education (2006).*
- ❖ *Gayakwad, R.A., Op-Amp and Linear Integrated Circuits, Pearson Education (2002).*
- ❖ *Franco, S., Design with Operational Amplifier and Analog Integrated circuit, McGraw Hill (2016).*
- ❖ *Terrell, D., Op Amps Design Application and Troubleshooting, Newness (1996).*