



Analog Electronic Circuits (UEC301)

By
Dr. Mayank Kumar Rai
Associate Professor
ECED, TIET

Thapar Institute of Engineering & Technology
(Deemed to be University)

Bhadson Road, Patiala, Punjab, Pin-147004

Contact No. : +91-175-2393201

Email : info@thapar.edu






THAPAR INSTITUTE
OF ENGINEERING & TECHNOLOGY
(Deemed to be University)

Subject: Analog Electronic Circuits (UEC301)


Lecture topic : Load Line analysis





Key points

- **Load Line**

- **Three different points**

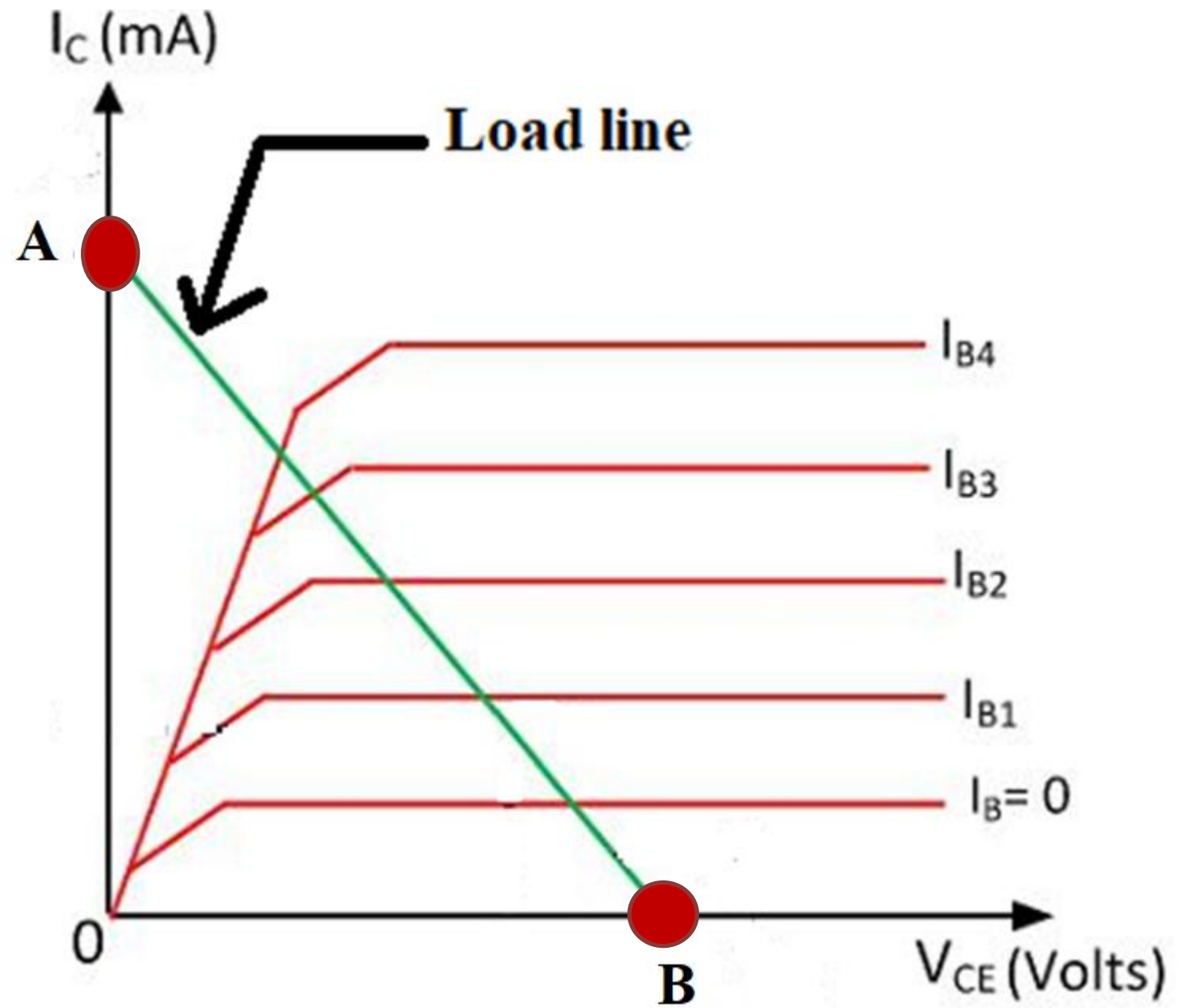 - ❖ Cut-off point
 - ❖ Saturation point
 - ❖ Operating point
- **Three different Regions**

 - ❖ Saturation Region
 - ❖ Active Region
 - ❖ Cut-off Region

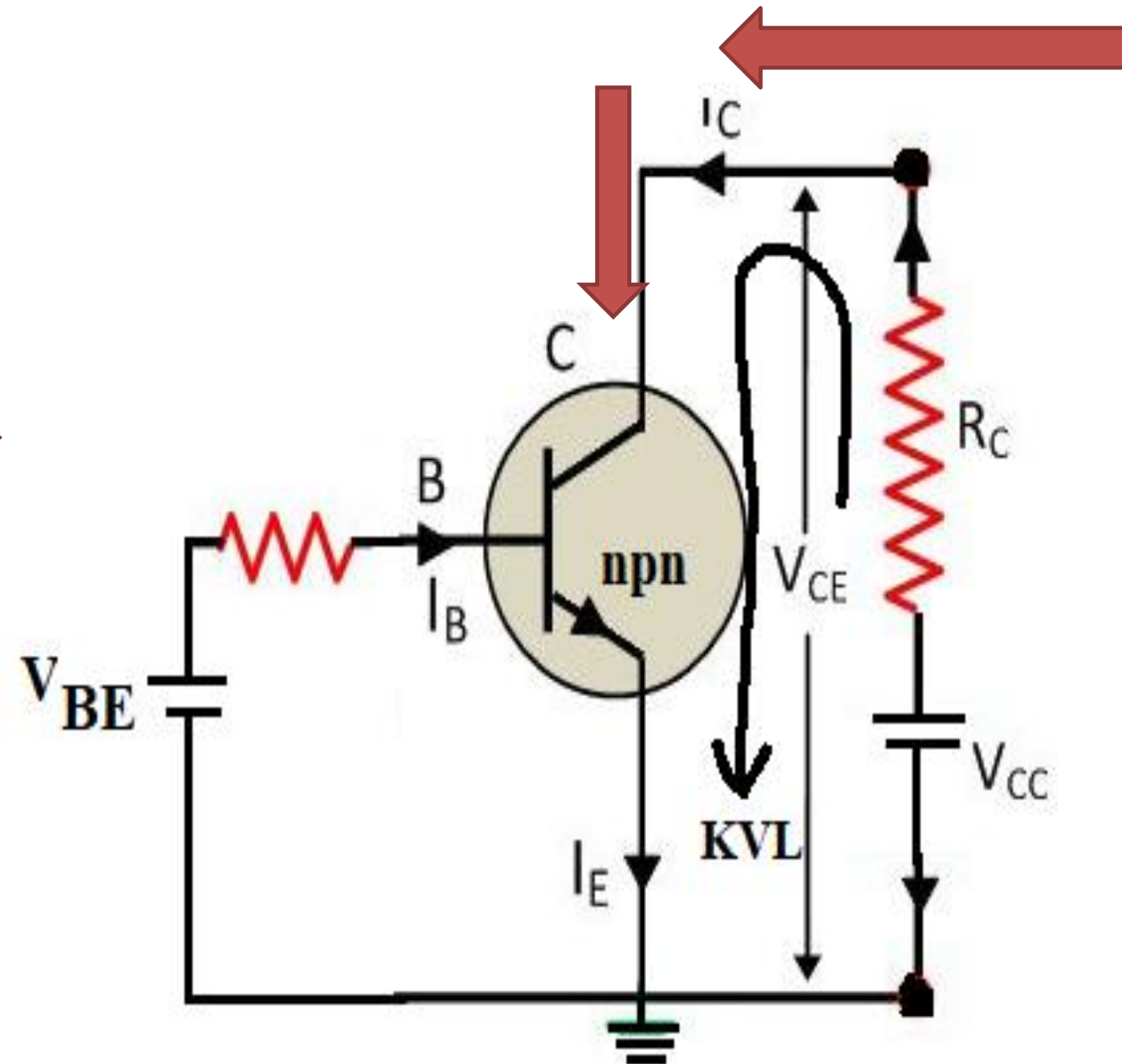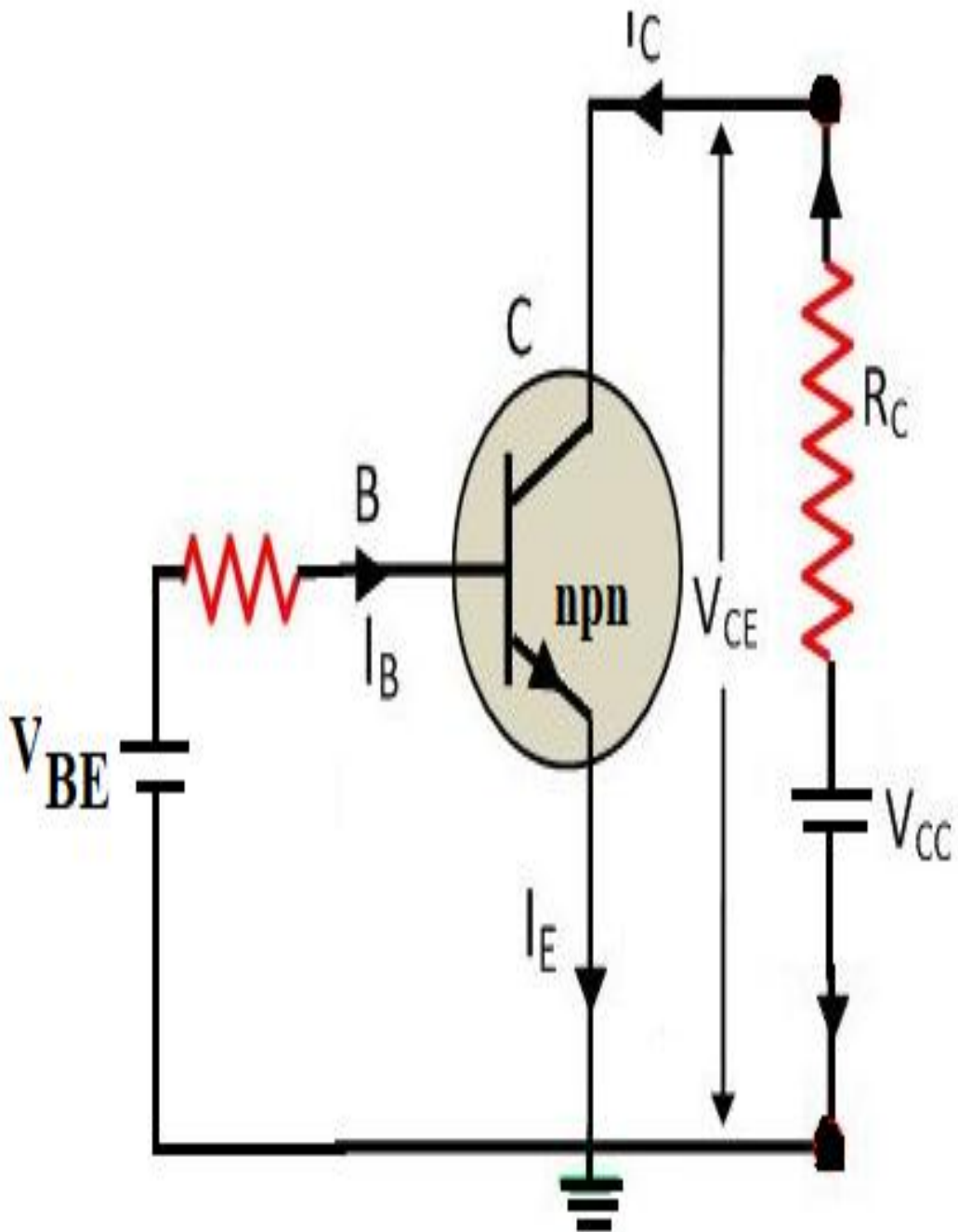
Load Line



Cont..



Cont..

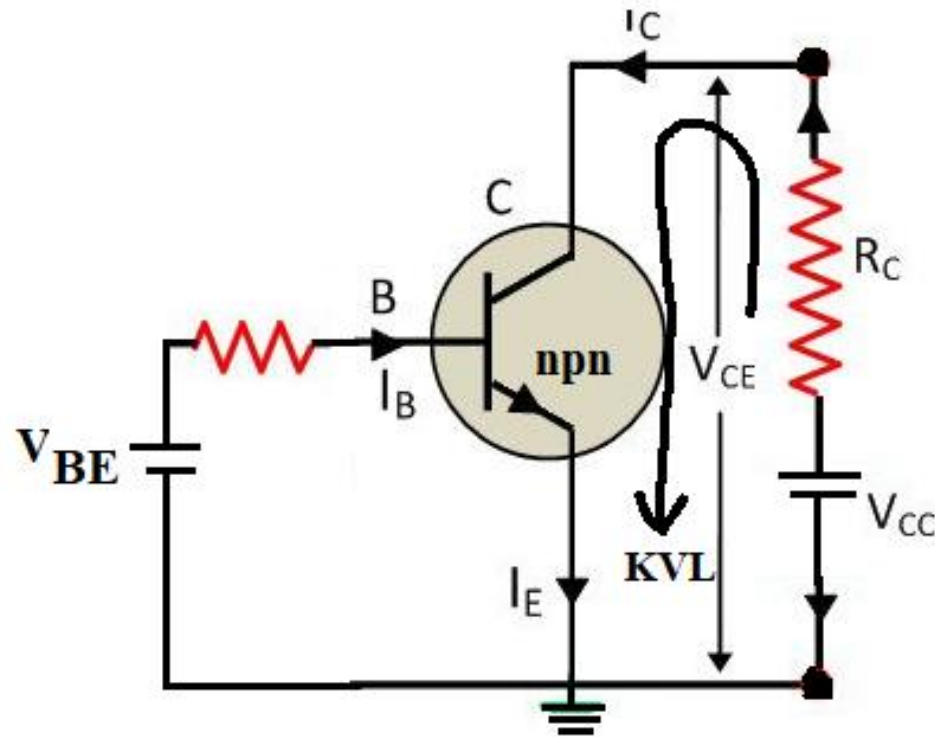

$$V_{CC} = V_{CE} + I_C R_C \quad (1)$$


The end point of the line are located as

1. V_{CE} is maximum when $I_C = 0$ then from the equation (1)

$$V_{CE} = V_{CC}$$



2. I_C becomes maximum when $V_{CE} = 0$ then from the equation (1)

$$I_C = V_{CC} / R_C$$

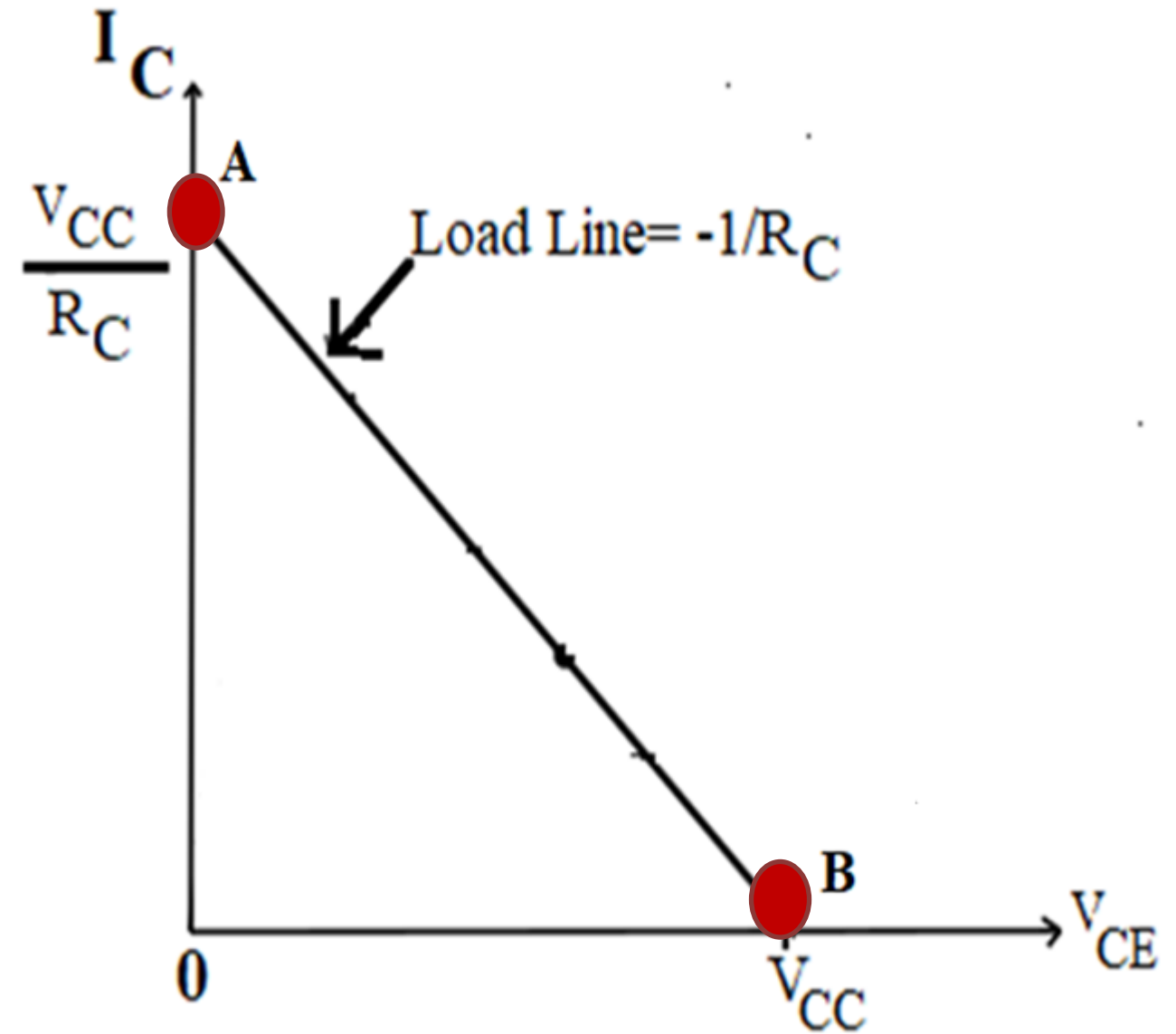


Different points and Regions

- Saturation
- Active
- Cut-off

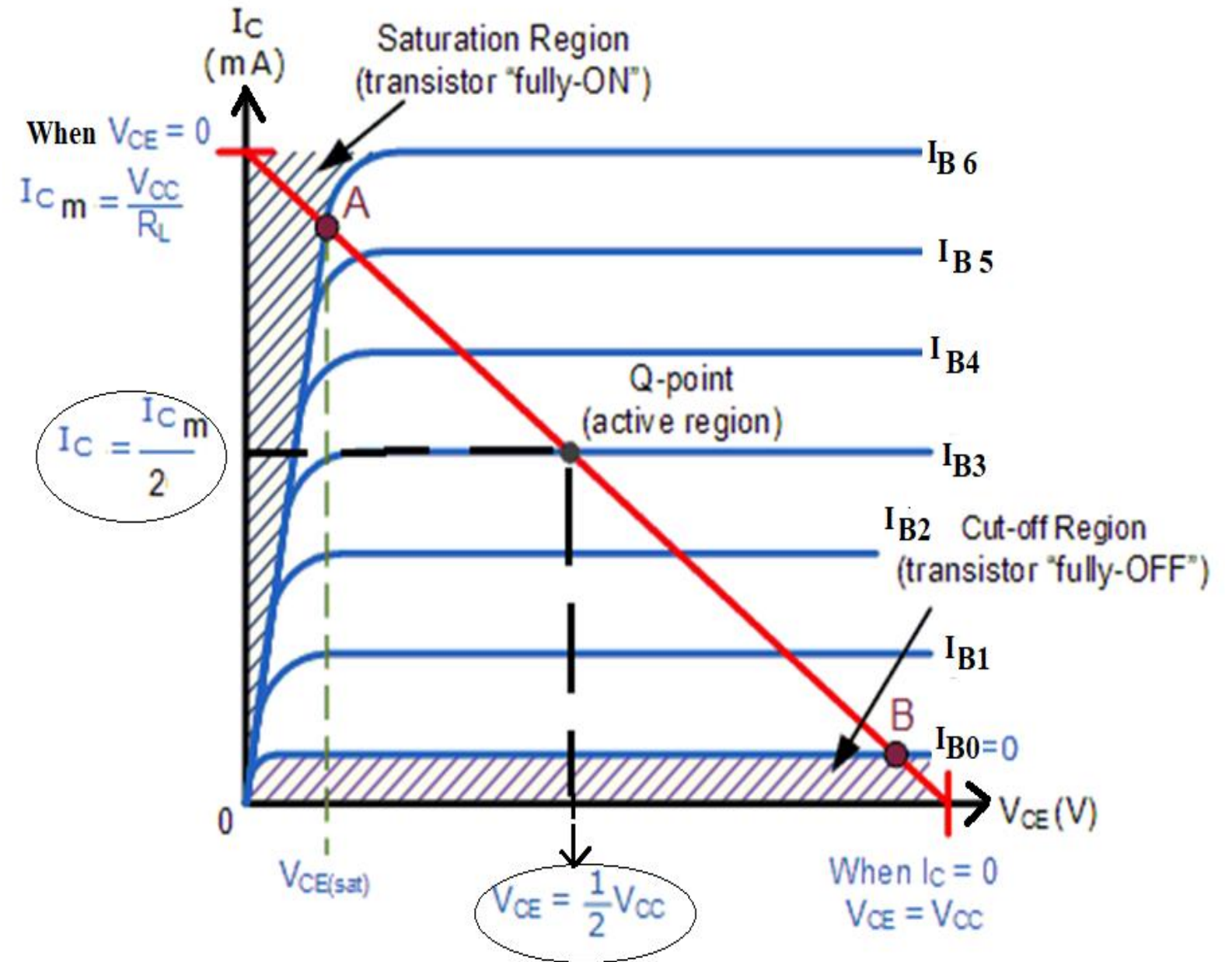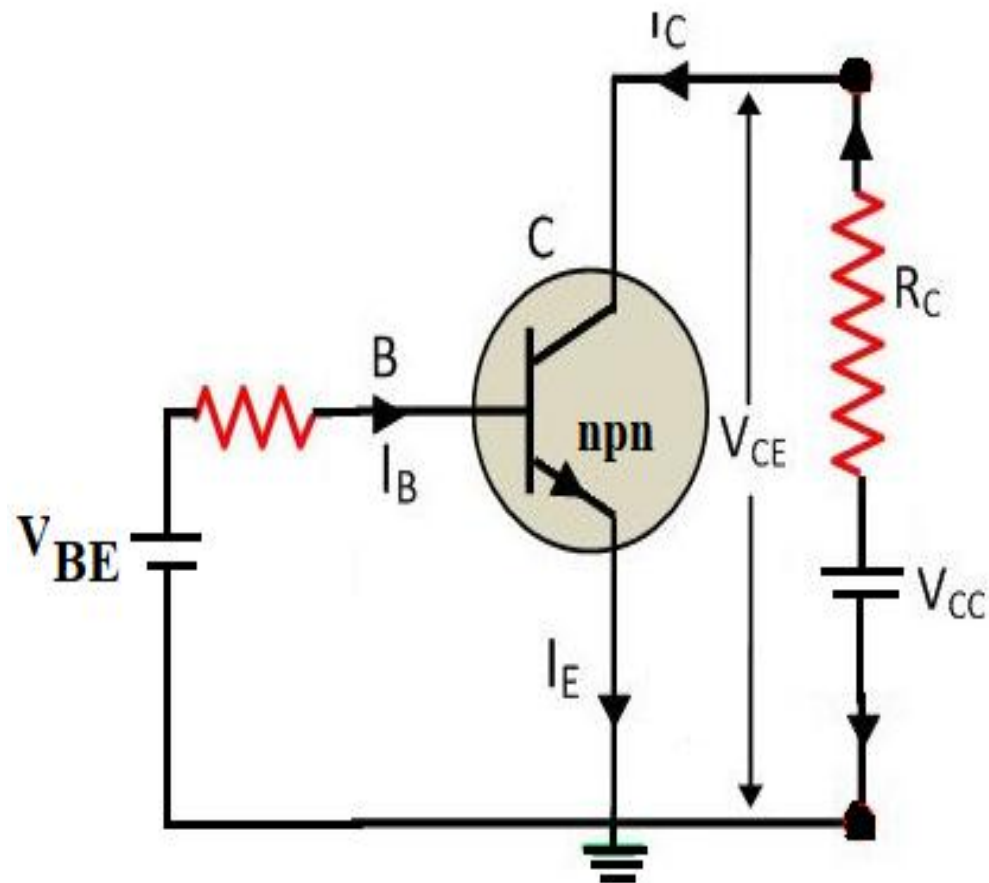

Saturation, Active and Cut-off Regions

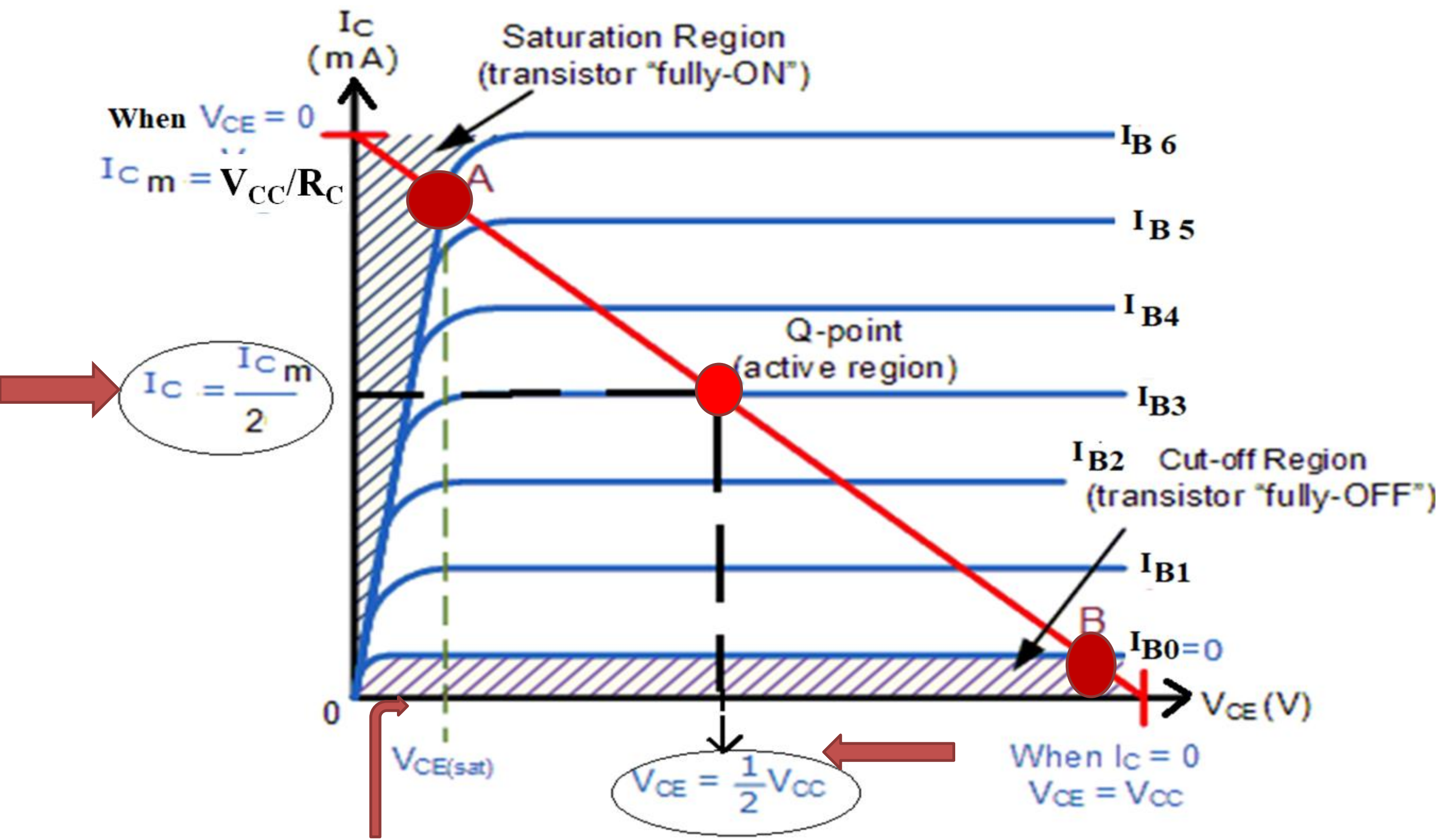

Thank You