

# Analog Electronic Circuits (UEC301)

By



**Dr. Mayank Kumar Rai**  
**Associate Professor,**  
**ECED, TIET, Patiala**

Thapar Institute of Engineering & Technology  
(Deemed to be University)  
Bhadson Road, Patiala, Punjab, Pin-147004  
Contact No. : +91-175-2393201  
Email : [info@thapar.edu](mailto:info@thapar.edu)

**ti**  
**THAPAR INSTITUTE**  
OF ENGINEERING & TECHNOLOGY  
(Deemed to be University)



# Subject: Analog Electronic Circuits (UEC301)

Faculty name: Dr. Mayank Kumar Rai ( Associate Professor & Course Coordinator)

Topic of today's Lecture : Multivibrator-I &II

## Key points

- ✓ **Switching Action of a BJT**
- ✓ **Multivibrator**
- ✓ **Types of Multivibrator**
- ✓ **Astable (Free running) Multivibrator**
- ✓ **Monostable Multivibrator**
- ✓ **Bistable Multivibrator**

**Contents of this lecture are based on the following books:**

- *Jacob Milman & C.C.Halkias, “Integrated Electronics Analog and Digital Circuit and Systems” Second Edition.*
- *Adel S. Sedra & K. C. Smith, “MicroElectronic Circuits Theory and Application” Fifth Edition.*
- *Robert L. Boylestad & L. Nashelsky, “Electronic Devices and Circuit Theory” Eleventh Edition.*



# Switching Action of a BJT

➤ A transistor which is used as a switch is known as a switching transistor.

i. OFF Region or cut off region

Power loss = (Output voltage) X (Output current)

$$\text{Power loss} = V_{CC} \cdot I_{CEO}$$

ii. ON Region or Saturation Region

$$V_{CE} = V_{CC} - I_{C\text{sat}} R_C \quad \text{where } V_{CE} = V_{knee}$$

$$I_{C\text{sat}} = \frac{V_{CC} - V_{knee}}{R_C}$$

$$\text{Power loss} = V_{knee} \cdot I_{C\text{sat}}$$

iii. Active Region

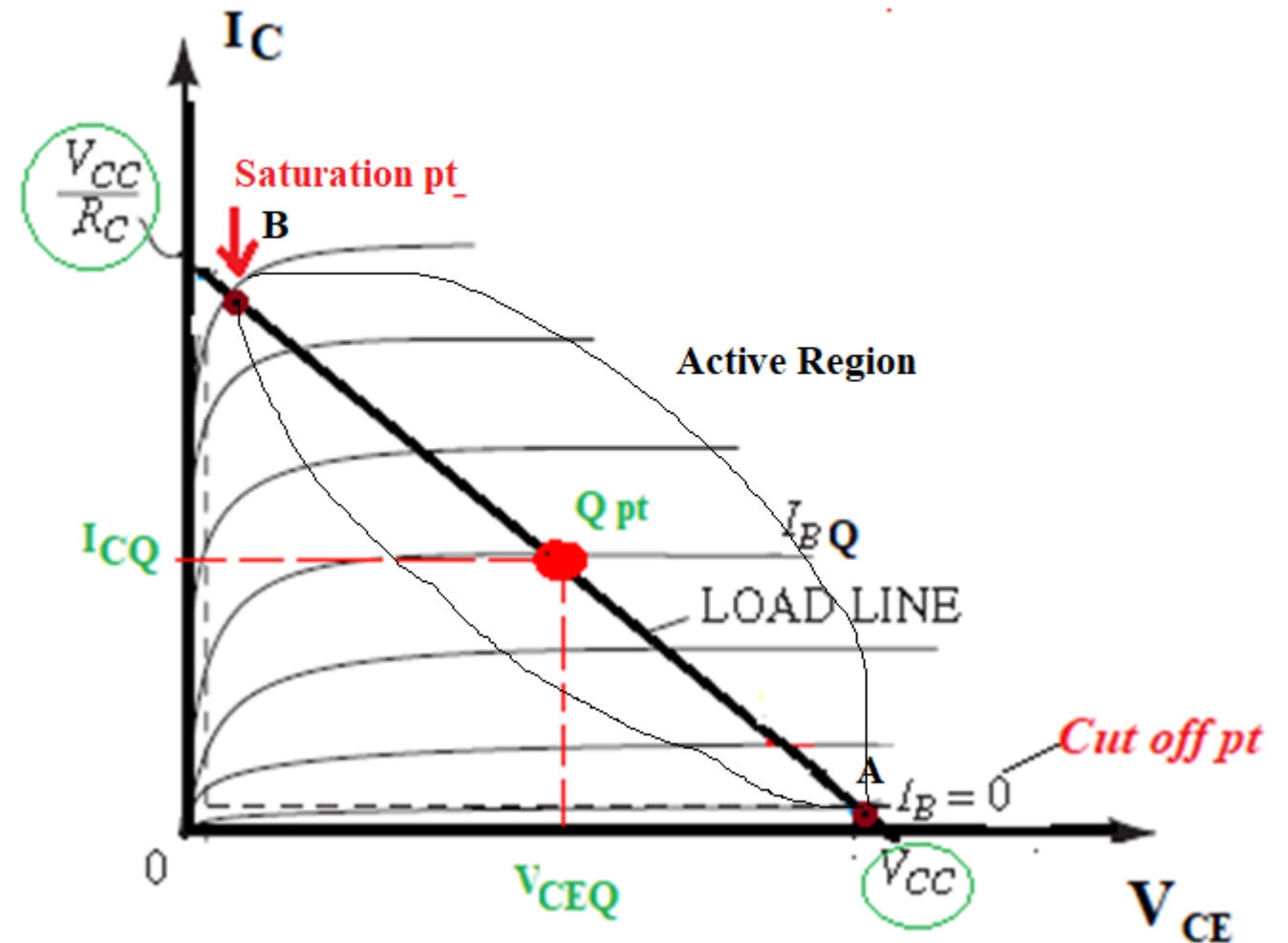


Figure 1: Output characteristics. Of npn transistor.

# Multivibrator

*A electronic circuit that generates square waves or other non-sinusoidal such as rectangular ,saw-tooth waves is known as a **Multivibrator**.*

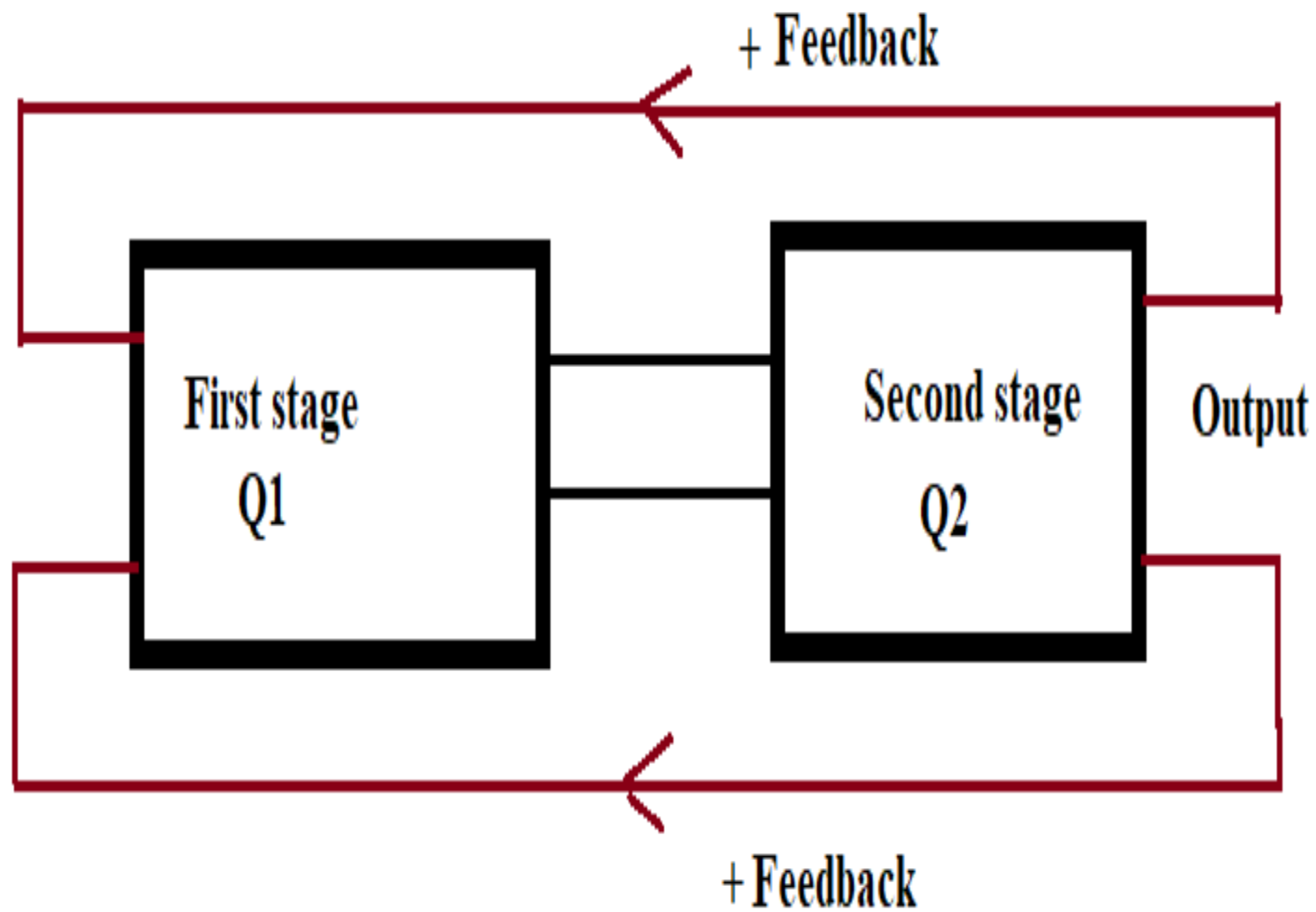


Figure 2: Block diagram of multivibrator.

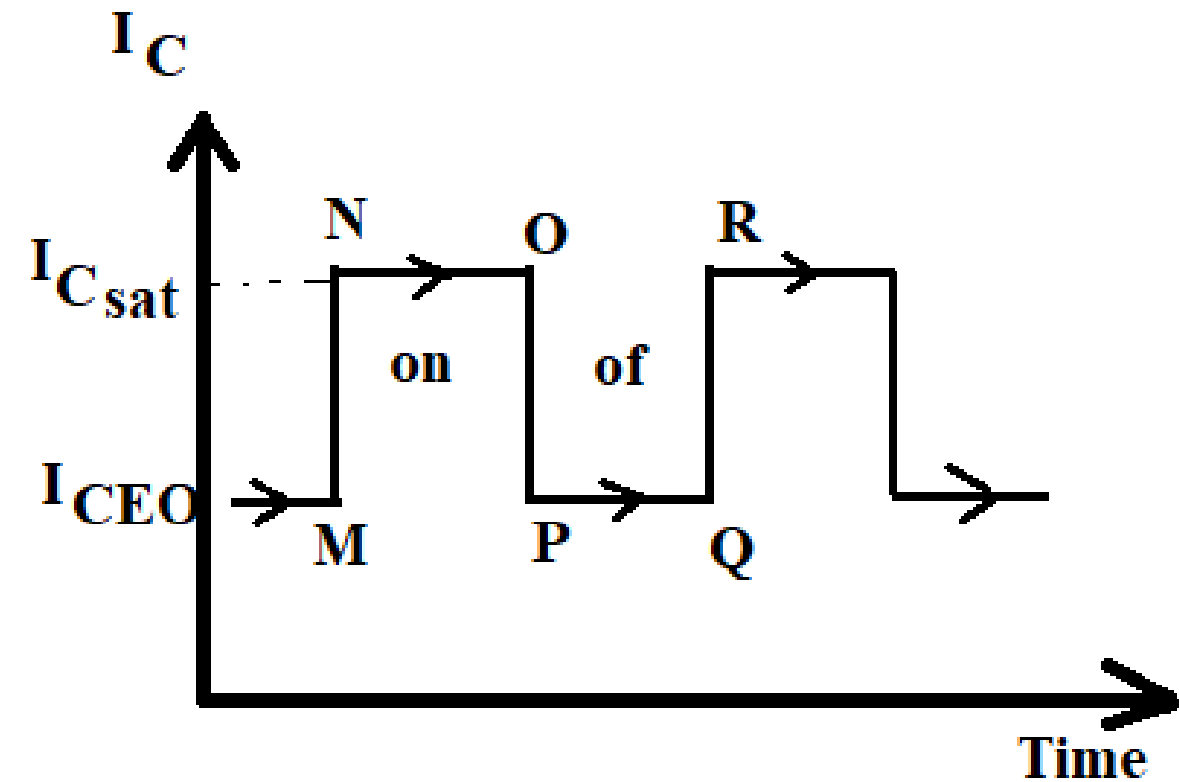


Figure 3:Waveform of Output current.

# Types of Multivibrator

State	On	OF
First state	Q1	Q2
Second state	Q2	Q1

- i. *Astable or free running multivibrator*
- ii. *Monostable or one-shot multivibrator*
- iii. *Bi-stable or flip flop multivibrator*

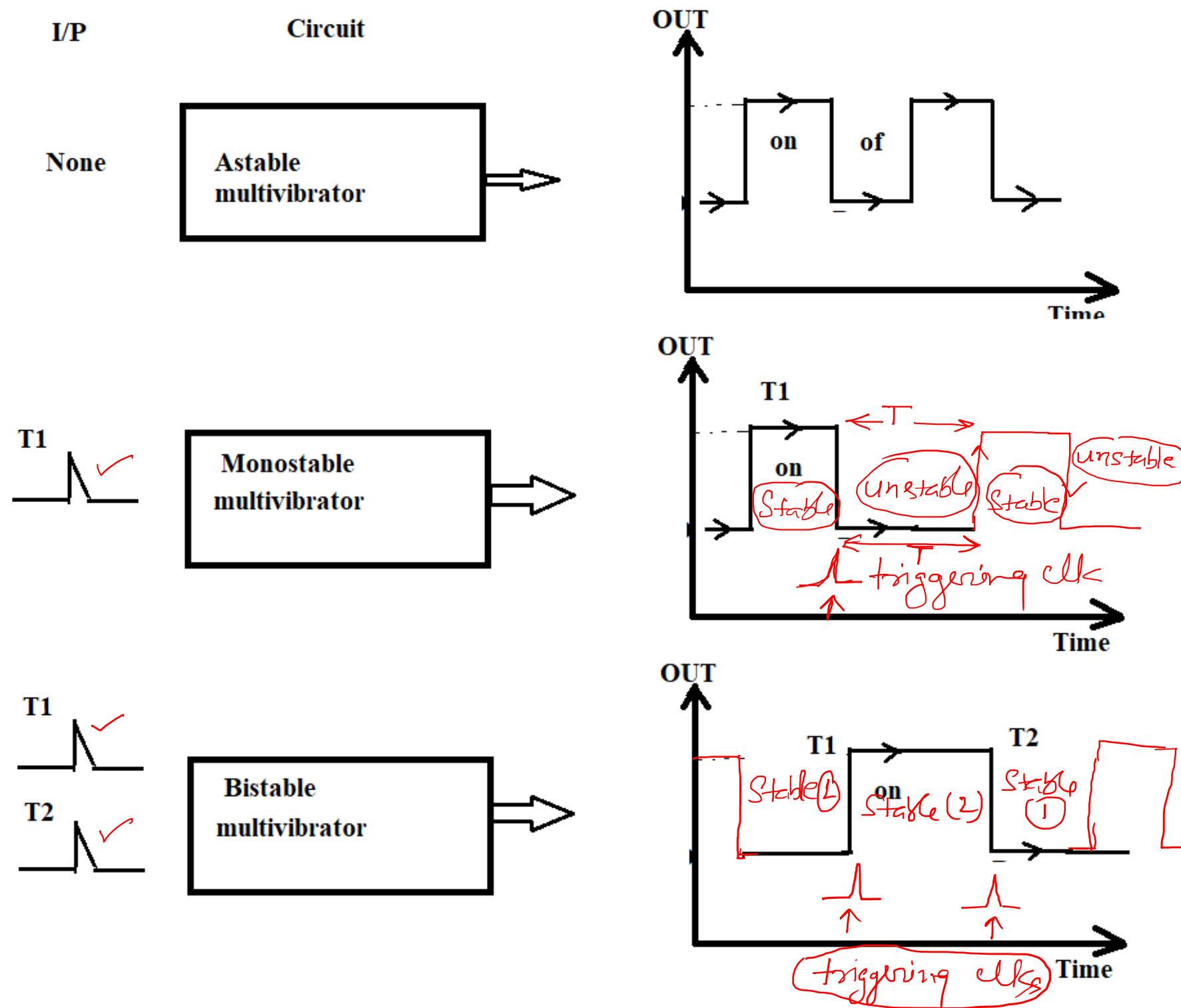


Figure 4: Input output relation of different types of multivibrator.

**Astable Multivibrator** : A multivibrator which generates square waves of its own is called as an astable or free running multivibrator.

*Circuit Details:*

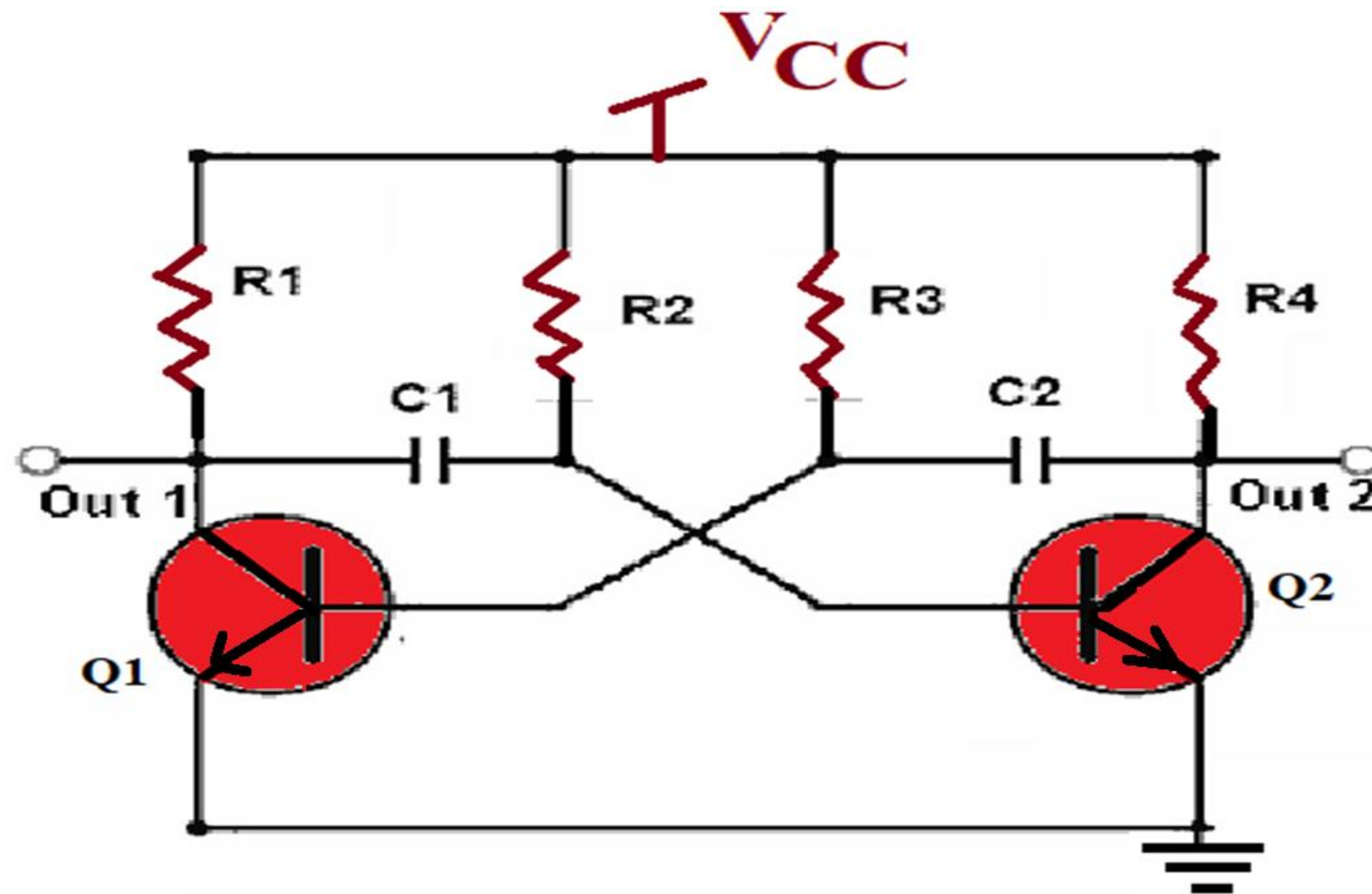


Figure 5: Astable multivibrator.

## Operation

**ON or OFF time:** *The time for which either transistor remain ON or OFF*

**ON time for  $Q_1$ :**

$$T_1 = 0.694 R_2.C_1$$

**OFF time for  $Q_1$ :**

$$T_2 = 0.694 R_3.C_2$$

**Total time period of the square wave:**

$$T = T_1 + T_2 = (0.694 R_2.C_1 + 0.694 R_3.C_2)$$

**Frequency of the square wave,**

$$f = \frac{1}{T}$$

**Monostable Multivibrator** : A multivibrator in which one transistor is always conducting and other is non conducting is called **monostable multivibrator**.

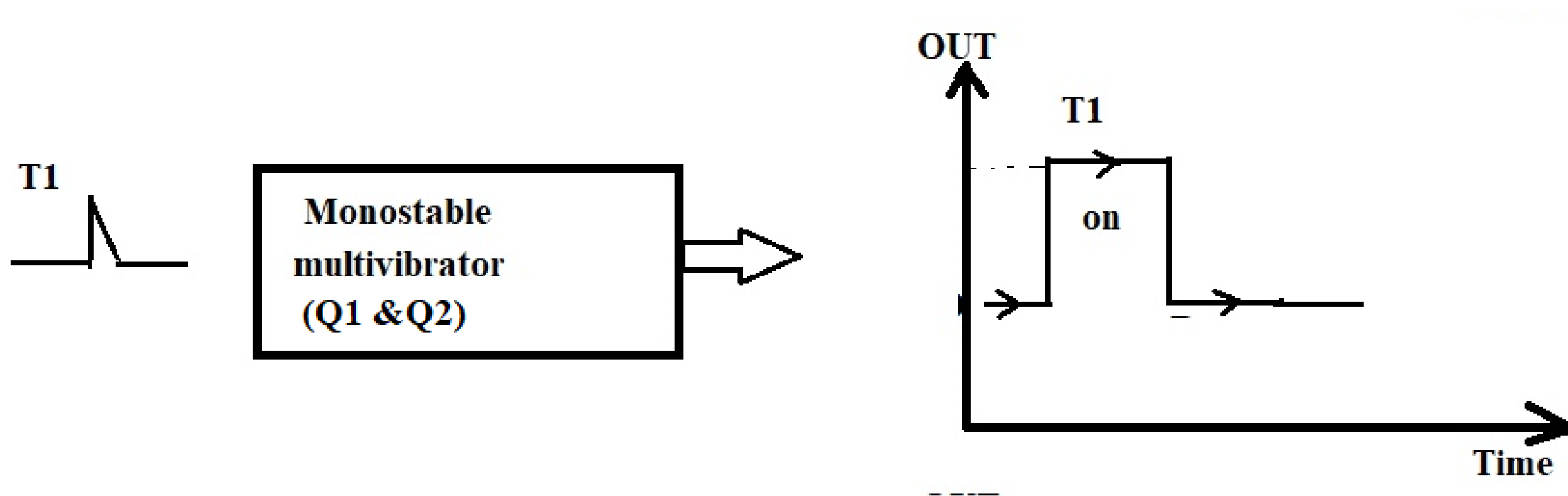


Figure 1: Circuit diagram of monostable multivibrator.



## Circuit Details:

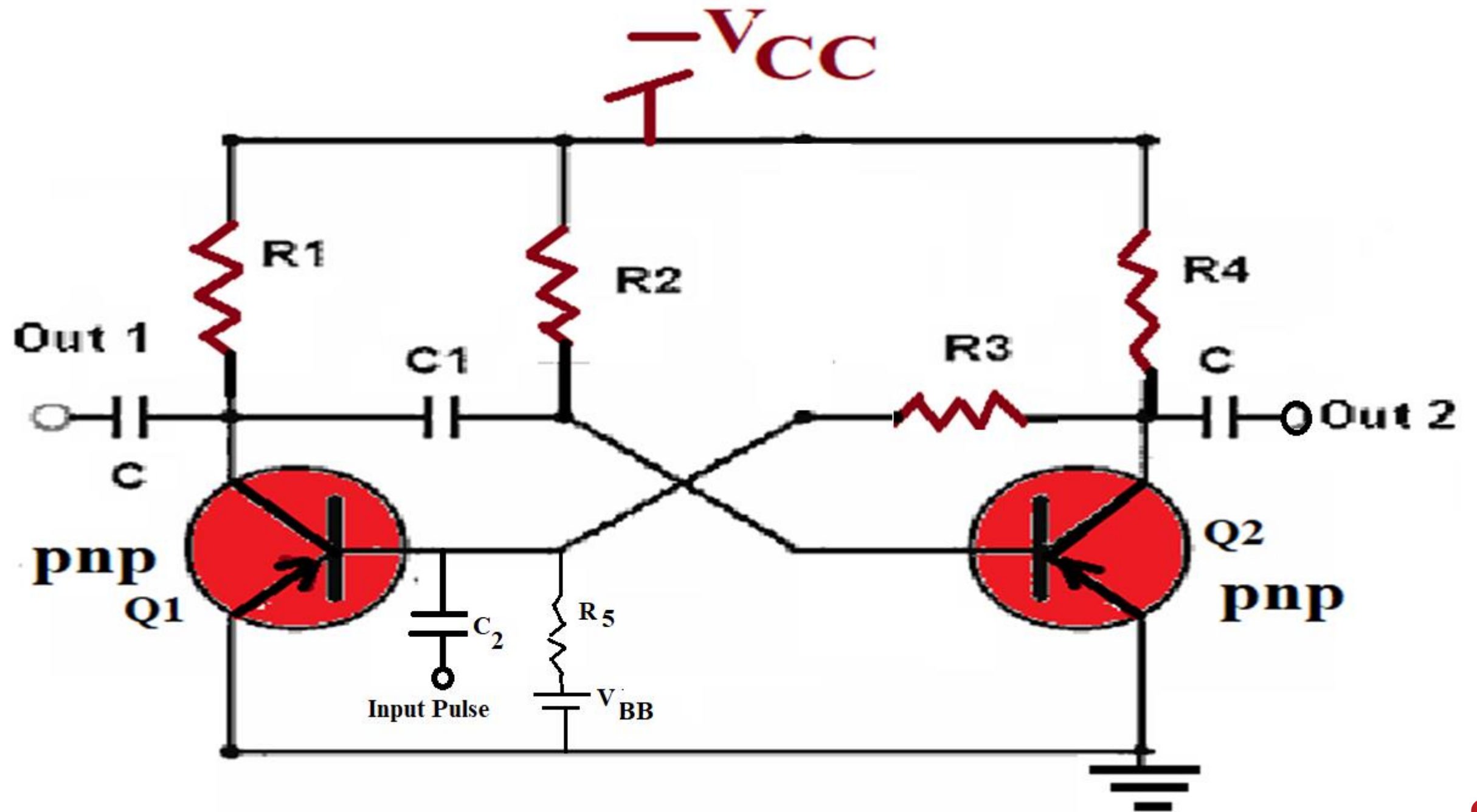


Figure 2: Circuit diagram of Monostable multivibrator.

## Operation:

### Step 1:

- ✓ Initially we assume that the  $Q1$  is at cut off and  $Q2$  is at saturation.
- ✓ We apply negative triggering pulse
- ✓  $C1$  is charged up to  $V_{cc}$ .

### Step 2:

- ✓  $C1$  is discharged
- ✓  $Q1$  is driven to saturation and  $Q2$  to cut off

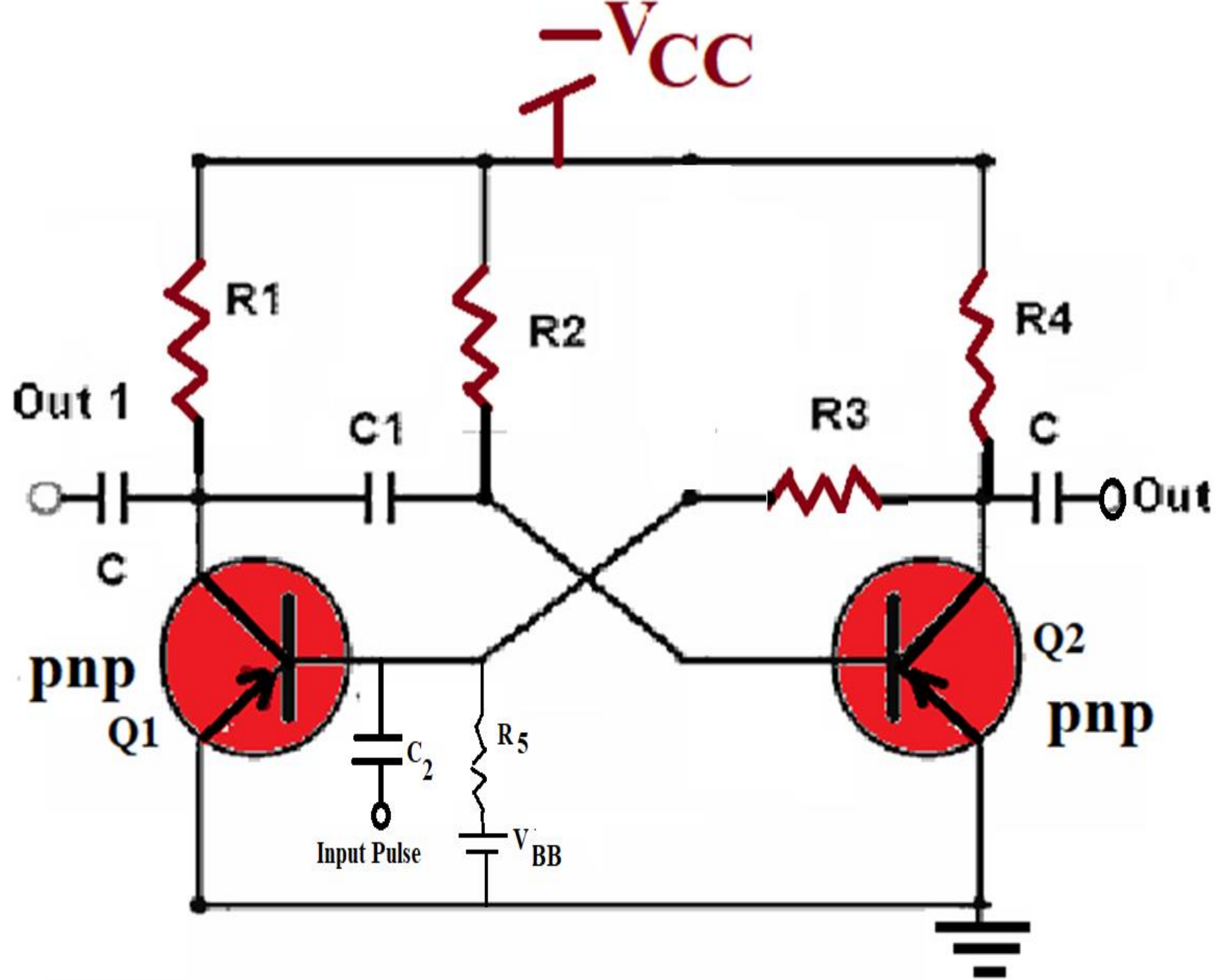


Figure 3: Operation of Monostable multivibrator.

**Bistable Multivibrator** : A multivibrator which has both the states stable is called **Bistable multivibrator**.

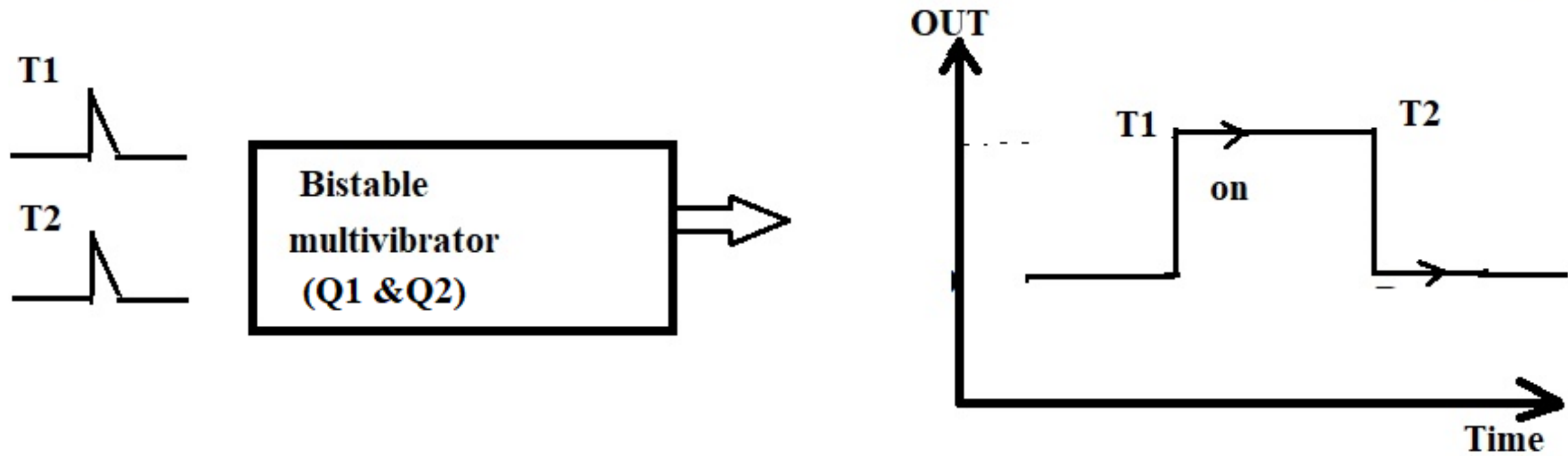


Figure 4: Block diagram of bistable multivibrator.

## Circuit Details

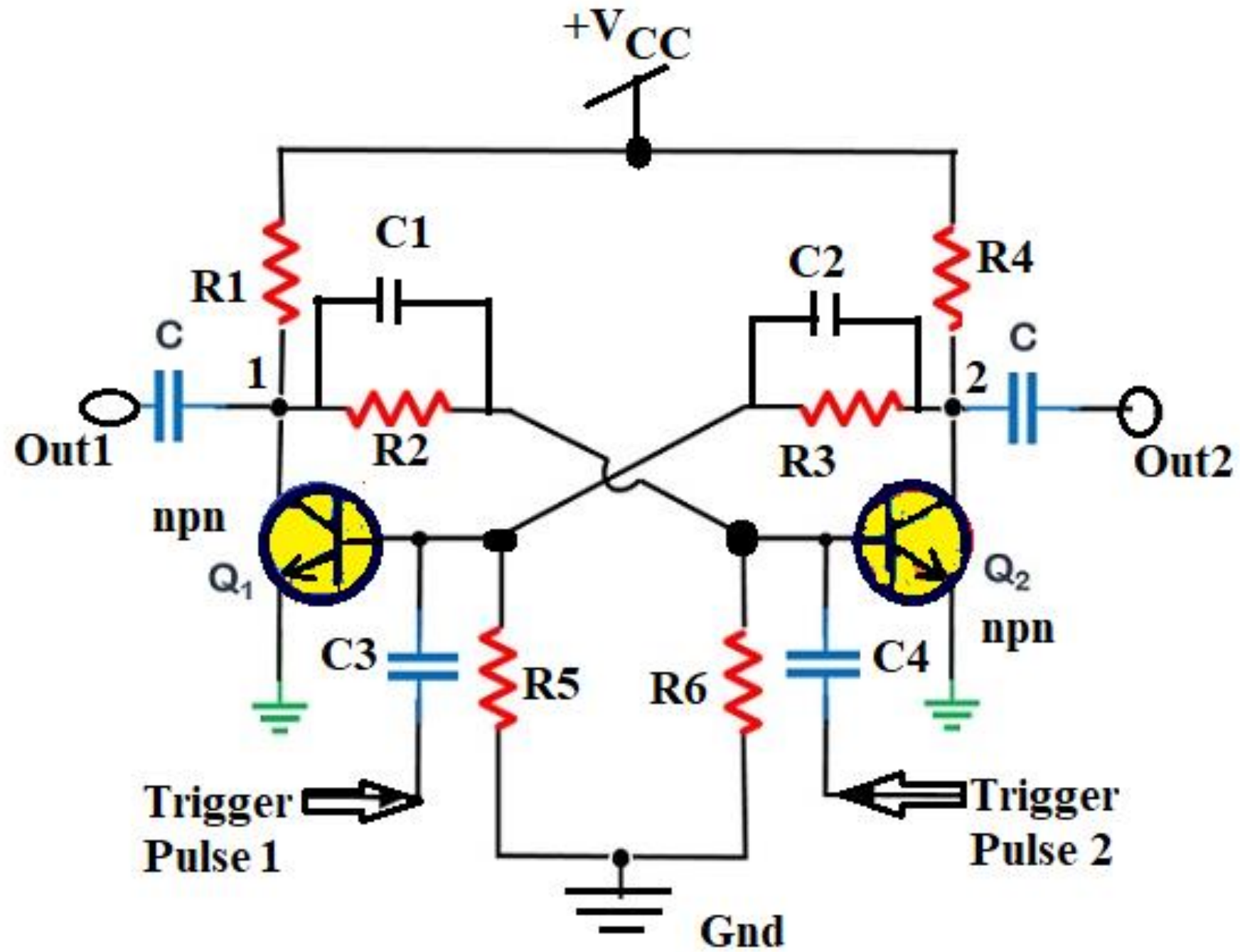


Figure 5: Circuit diagram of bistable multivibrator.



## Operation:

### Step 1:

- ✓ *Q1 is on and Q2 is off*
- ✓ *And we apply negative pulse to the base of Q1*
- ✓ *Q1 is driven to cut off and Q2 to saturation(on).*

### Step 2:

- ✓ *Another negative pulse is applied to the base of Q2*
- ✓ *Q1 & Q2 will come to original states. (i.e. Q1 is on and Q2 is off)*

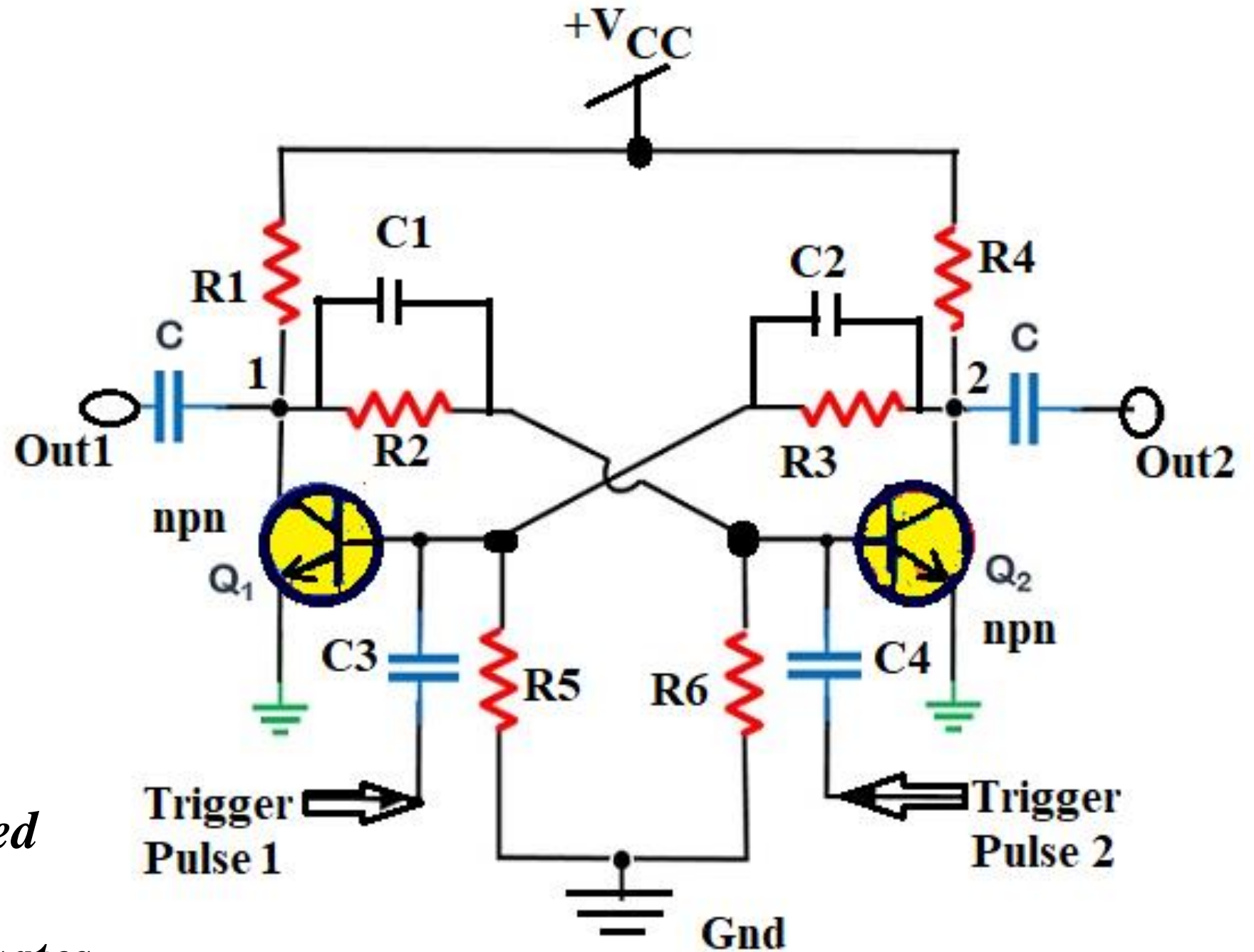


Figure 6: Operation of bistable multivibrator.

## ***Comparison:***

<b>S.No.</b>	<b>Astable Multivibrator</b>	<b>Monostable Multivibrator</b>	<b>Bistable Multivibrator</b>
<b>1.</b>	There are no stable states of output	There is only one stable state of output	There are two stable states of output
<b>2.</b>	Trigger input is not required	One trigger input is required for changing the state of output	Two trigger inputs are required for changing the state of output
<b>3.</b>	Used as rectangular, square wave or ramp generator	Used as timer	Used as flip flop
<b>4.</b>	Number of quasi stable state is two	Number of quasi stable state is one	No quasi stable state

***Thank You***

