

***Thapar Institute of Engineering & Technology, Patiala***

Department of Electronics and Communication Engineering  
**Course Code:** UEC-301; **Course Name:** Analog Electronic Circuits  
**B.E. (ENC) (III-Sem),**  
**“Tutorial Sheet No. - 1”**

[1]	Explain the role of diode and transistor in real-world application scenario.
[2]	Explain the meaning of each term in “ <i>Bipolar Junction Transistor</i> ”.
[3]	Name the three terminals available in NPN and PNP BJTs and explain the role of each of those terminals.
[4]	Draw the respective circuit symbols of BJTs available as well as insert proper biasing voltages, so that each of them works properly in their active region of operation.
[5]	Explain the four regions of operation of BJT.
[6]	Mention the mathematical relationship between $I_C$ and $I_{CBO}$ as well as the relation between the leakage currents $I_{CBO}$ and $I_{CEO}$ for BJT.
[7]	Explain the applications of BJT in four different operating regions.
[8]	Make yourself understand different input and output characteristics of various BJT configurations.
[9]	Explain the concept of current gains in CE and CB BJT configurations.