

Analog and Digital Systems (UEE505)

Lecture # 8 Introduction to Op Amp -II




THAPAR INSTITUTE
OF ENGINEERING & TECHNOLOGY
(Deemed to be University)

Deptt. Of Electrical & Instrumentation Engineering
Thapar Institute of Engineering & Technology Patiala, India

Example

For the non-inverting amplifier shown in the figure below, calculate

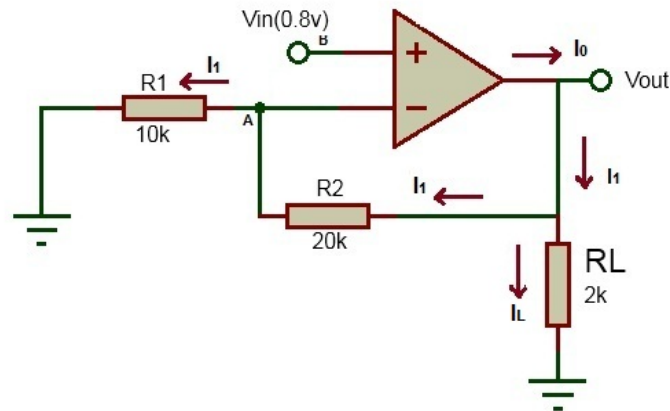- i) The gain of the amplifier, A_{CL}
- ii) The output voltage, V_O
- iii) The current through the load resistor, I_L .
- iv) The output current, I_O .



Solution

i) The gain of the non-inverting amplifier

$$\begin{aligned} A_{CL} &= 1 + (R_f/R_1) \\ &= 1 + (20k\Omega/10k\Omega) \\ &= 3 \end{aligned}$$

ii) The output voltage, $V_O = A_{CL} \cdot V_{IN}$


$$\begin{aligned} &= 3 (0.8V) \\ &= 2.4 V \end{aligned}$$

iii) Current through the load resistor, $I_L = V_O / R_L$


$$\begin{aligned} &= 2.4 / (2 \times 10^3\Omega) \\ &= 1.2 \text{ mA} \end{aligned}$$

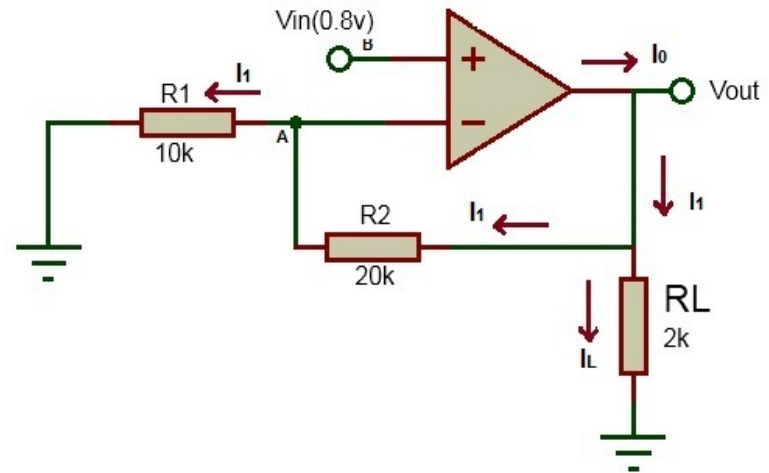iv) The output current, $I_O = I_1 + I_L$ (KCL)

$$\begin{aligned} &= 80\mu A + 1.2 \text{ mA} \\ &= 1.28 \text{ mA} \end{aligned}$$



Summing and Averaging Amplifier

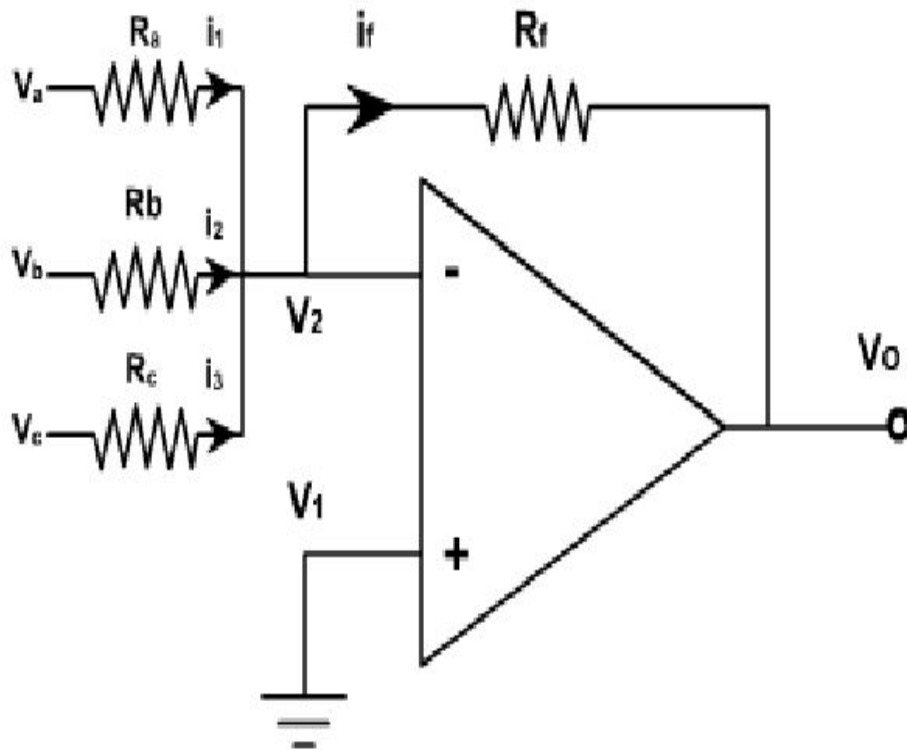

Apply KCL at v_2 node:

$$i_1 + i_2 + i_3 = i_f$$

$$\frac{V_a}{R_a} + \frac{V_b}{R_b} + \frac{V_c}{R_c} = \frac{V_o}{R_f}$$

$$V_o = -\left(\frac{R_f}{R_a} V_a + \frac{R_f}{R_b} V_b + \frac{R_f}{R_c} V_c\right)$$

If $R_a = R_b = R_c = R$, then

$$V_o = -\frac{R_f}{R} (V_a + V_b + V_c)$$

Note: If $R/R_f = n$ where n is number of inputs then the circuit behave like a averaging amplifier.

Example

Find the output voltage of the following *Summing Amplifier* circuit:

Solution:


$$\text{Gain (A}_v\text{)} = \frac{V_{\text{out}}}{V_{\text{in}}} = -\frac{R_f}{R_{\text{in}}}$$

$$A_1 = \frac{10\text{k}\Omega}{1\text{k}\Omega} = -10$$

$$A_2 = \frac{10\text{k}\Omega}{2\text{k}\Omega} = -5$$

$$V_{\text{out}} = (A_1 \times V_1) + (A_2 \times V_2)$$
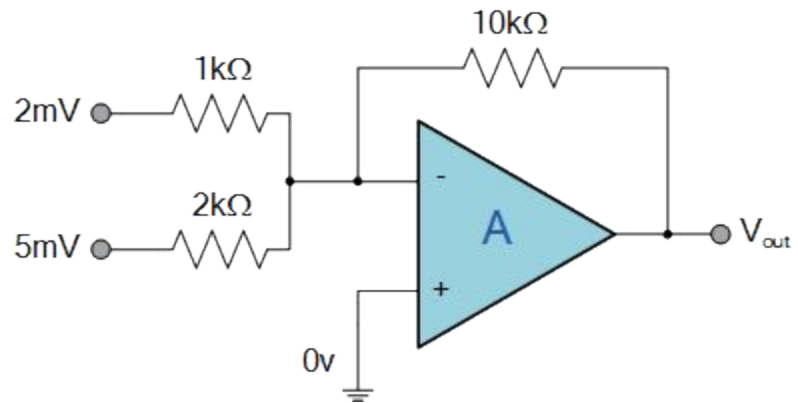
$$V_{\text{out}} = (-10(2\text{mV})) + (-5(5\text{mV})) = -45\text{mV}$$



Differentiator

A differentiator is an electronic circuit that produces an output equal to the first derivative of its input.


- useful in high-pass filter circuits.
- The nodal equation at the inverting input terminal's node is :

$$C \frac{d(0 - V_i)}{dt} + \frac{0 - V_0}{R} = 0$$

$$-C \frac{dV_i}{dt} = \frac{V_0}{R}$$

$$V_0 = -RC \frac{dV_i}{dt}$$

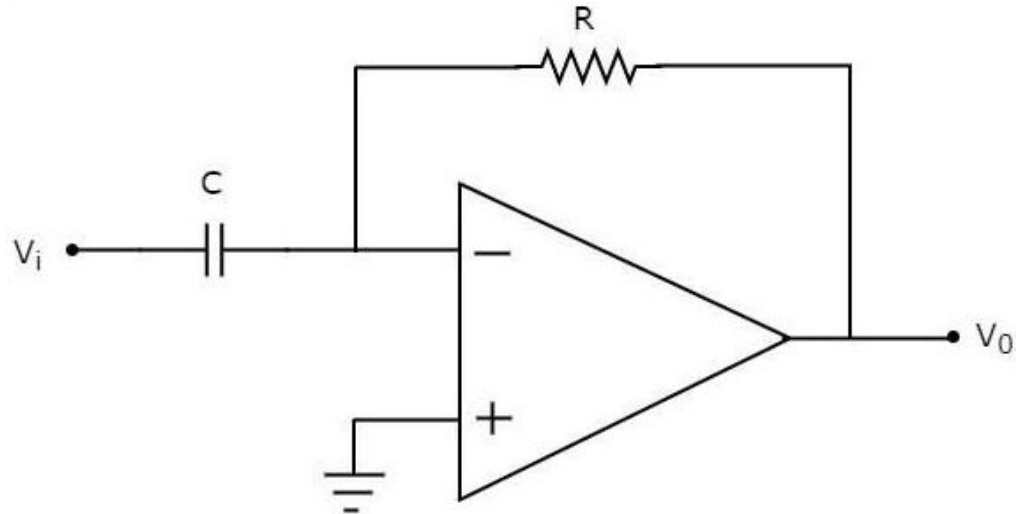If $RC = 1\text{sec}$, then $V_0 = -\frac{dV_i}{dt}$



Integrator

An integrator is an electronic circuit that produces an output that is the integration of the applied input.

- useful in low pass filter circuits and sensor conditioning circuits.
- The nodal equation at the inverting input terminal is:


$$\frac{0 - V_i}{R} + C \frac{d(0 - V_0)}{dt} = 0$$

$$\frac{-V_i}{R} = C \frac{dV_0}{dt}$$

$$\frac{dV_0}{dt} = -\frac{V_i}{RC}$$

$$dV_0 = \left(-\frac{V_i}{RC}\right) dt$$
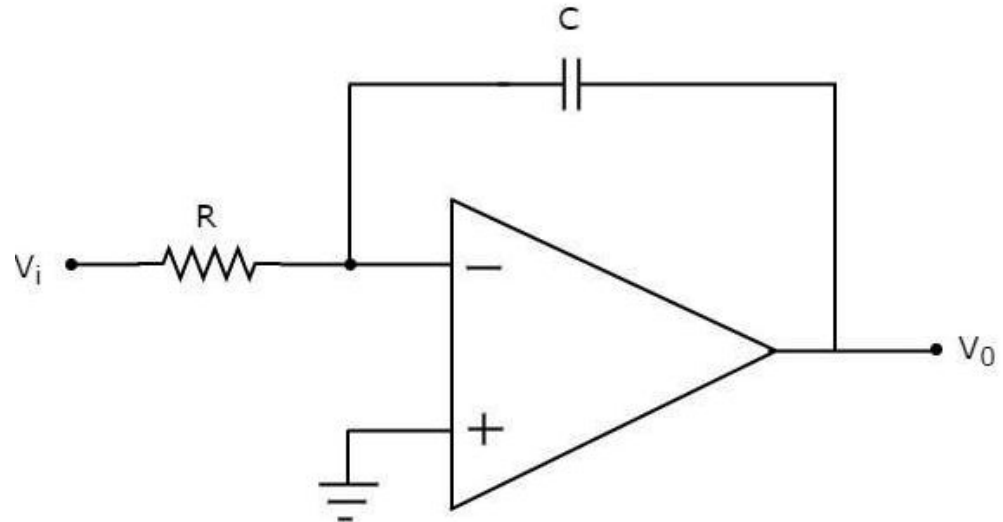
$$\int dV_0 = \int \left(-\frac{V_i}{RC}\right) dt$$




Therefore, $V_0 = -\frac{1}{RC} \int V_t dt$





For $RC = 1\text{sec}$, $V_0 = -\int V_i dt$

Comparator


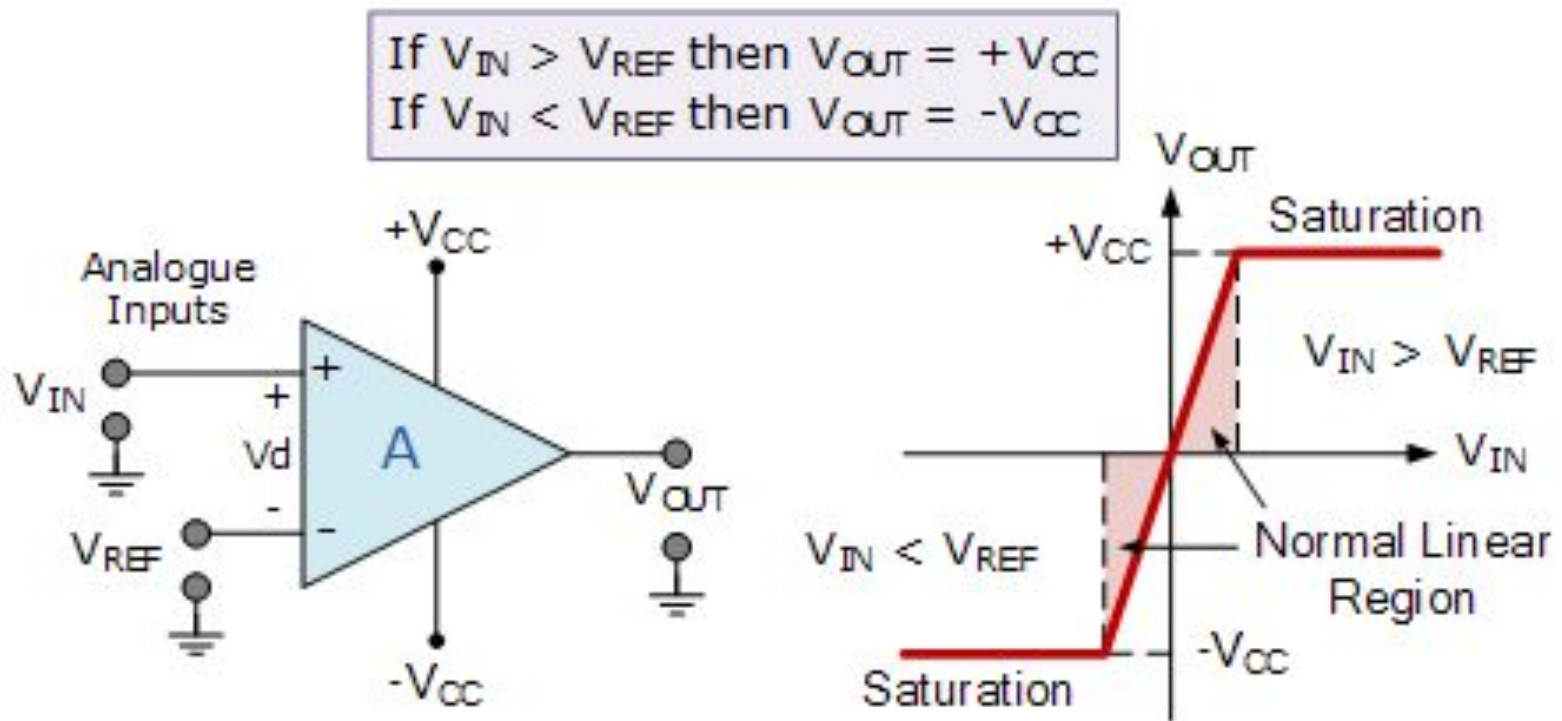
- Type of op-amp that compares two input voltage and produces an output in either of two states



Comparator Reference Voltage

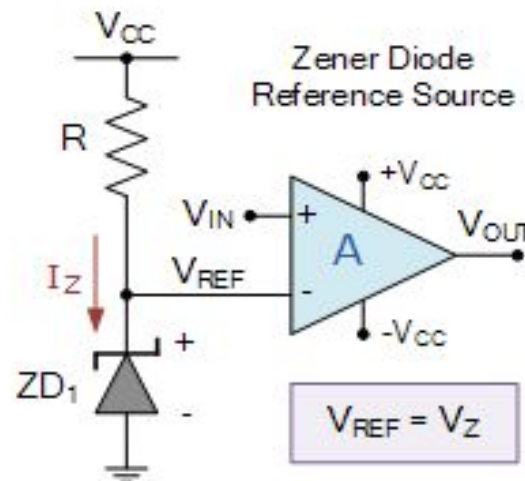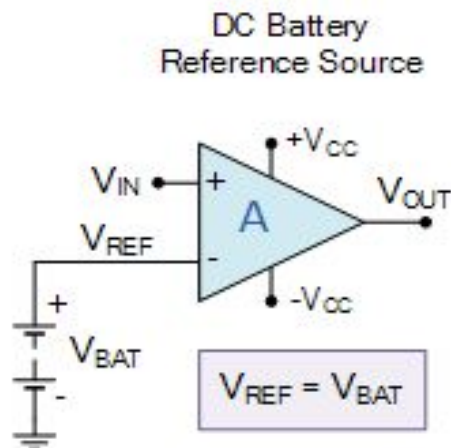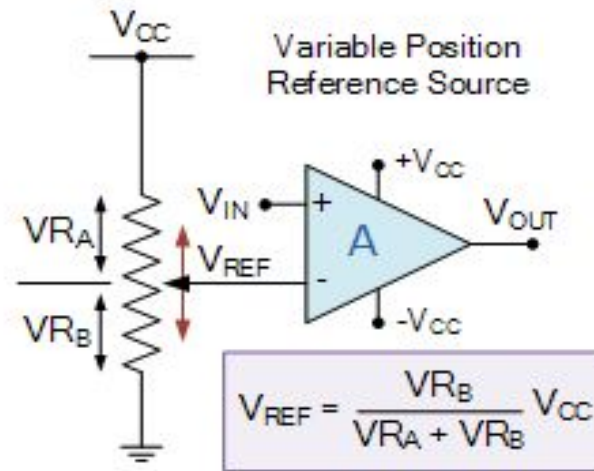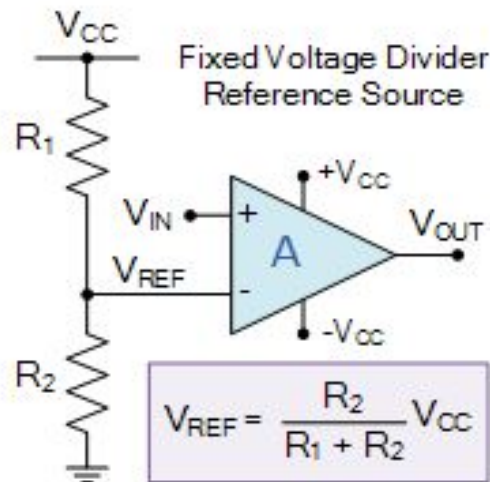

Non inverting Comparator Circuit

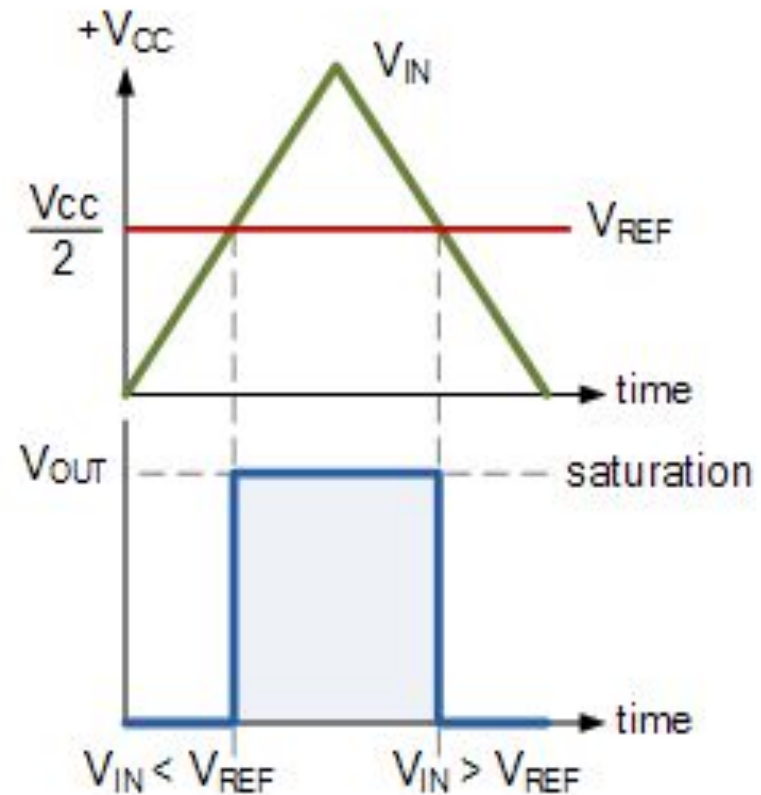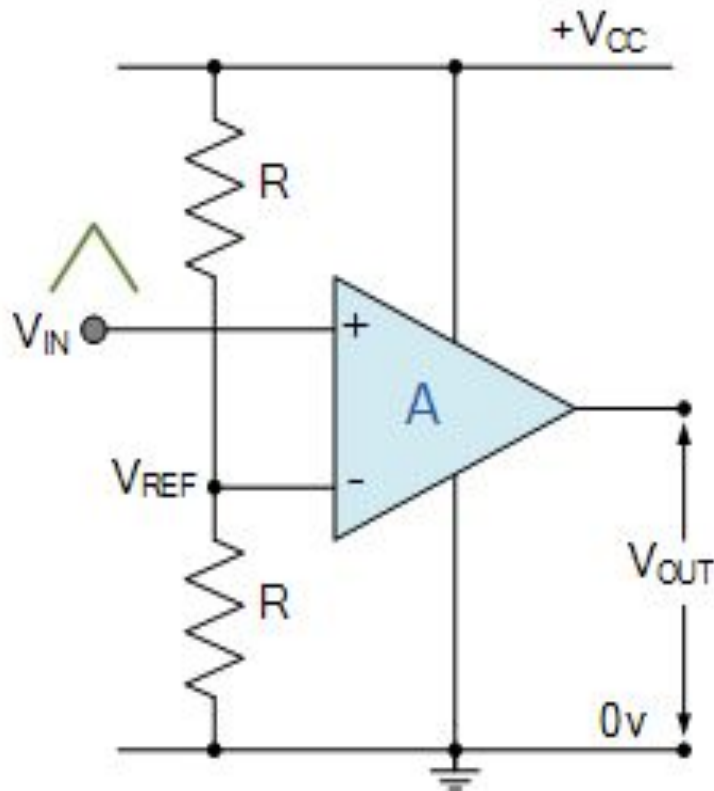

References

❖ For more details, refer to:

- *Boylestad R. L., Electronic Devices and Circuit Theory, Pearson Education*
- *Op-Amps and Linear Intergrated Circuits , Ramakant A. Gayakwad*
- <https://www.electronics-tutorials.ws/opamp>